

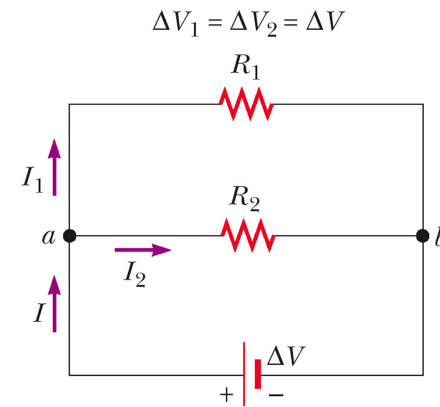
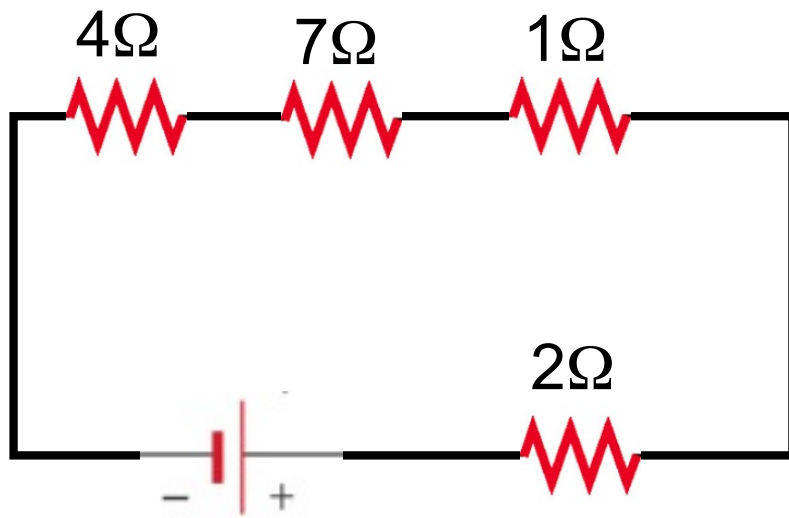
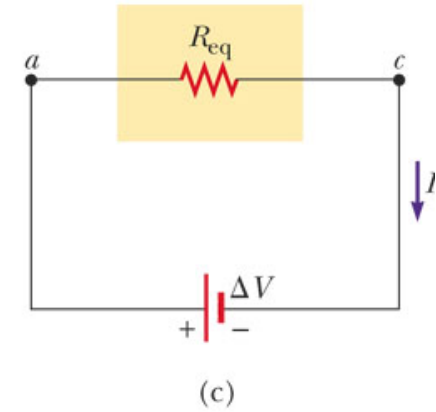


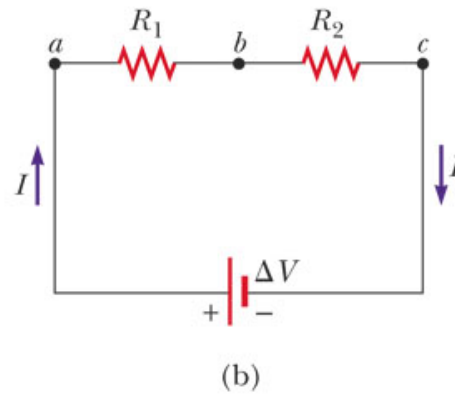21.7: Combinations of resistors: in series or in parallel



© 2008 Sinauer Associates, Inc.

Resistors connected in series

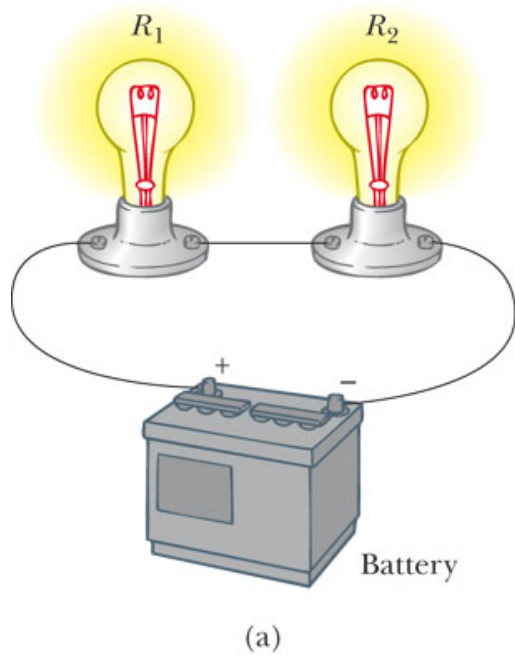

© 2006 Brooks/Cole - Thomson

What's R_{eq} in terms of R_1 and R_2 ?

$$\Delta V = IR_{eq}$$

Resistors connected in series

Note: Current is the same in R_1 and R_2 .

$$\Delta V_1 = IR_1$$


$$\Delta V_2 = IR_2$$

$$\Delta V = \Delta V_1 + \Delta V_2$$

$$\Delta V = IR_1 + IR_2 = I(R_1 + R_2)$$

$$\Delta V = IR_{\text{eq}}$$

$$R_{\text{eq}} = R_1 + R_2$$

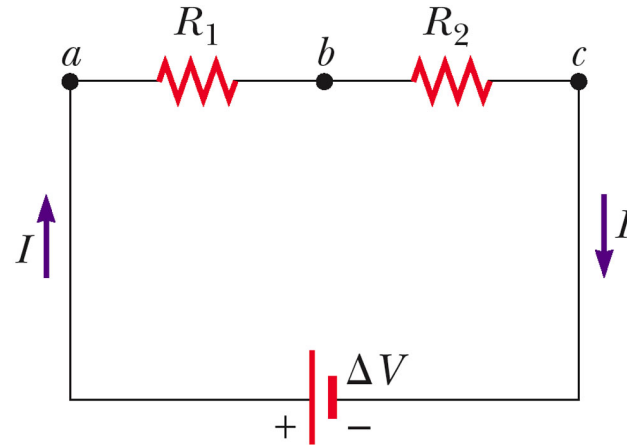


For N resistors in series:

$$R_{\text{eq}} = R_1 + R_2 + \dots + R_N$$

Note that R_{eq} is larger than any one individual R value

Resistors connected in series

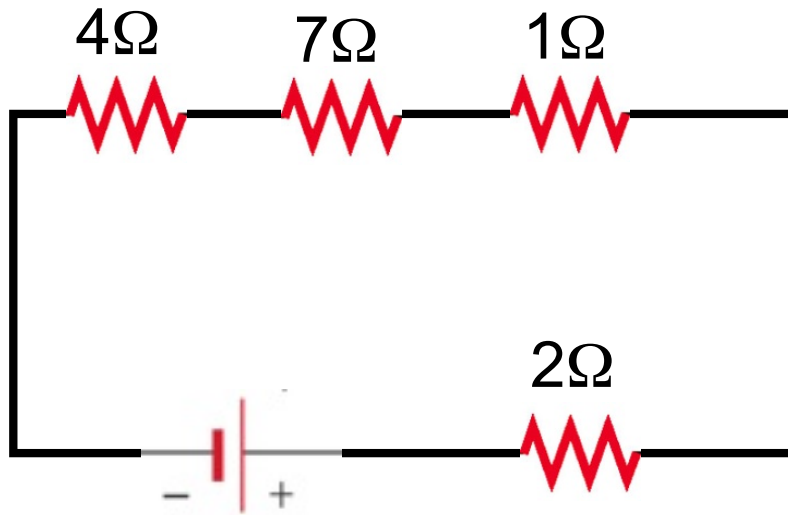

Find R_{eq} :

$$R_{eq} = 4\Omega + 7\Omega + 1\Omega + 2\Omega = 14\Omega$$




Understanding the Series Law



$$R = \rho \frac{L}{A} \text{ means } R \text{ is prop. to } L$$

Total R is prop. to $(L_1 + L_2)$

Resistors in Parallel

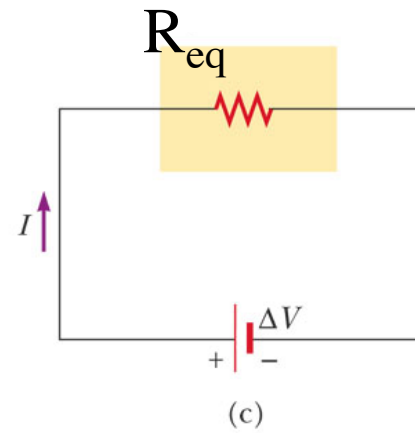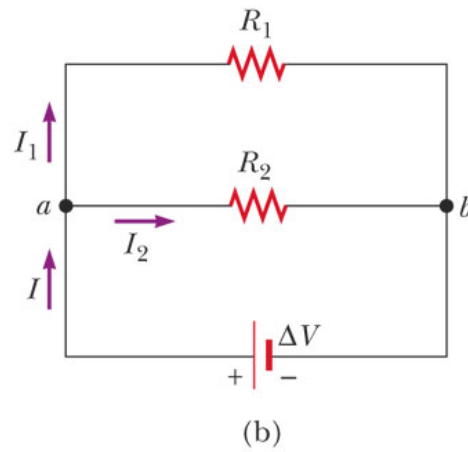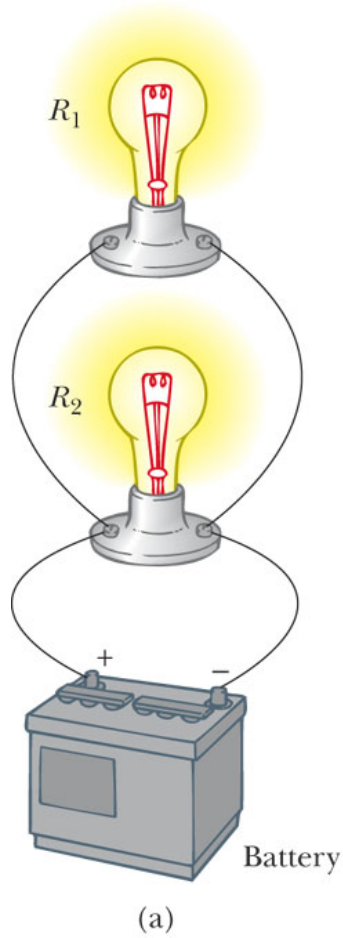


What happens at a junction?

Initial current I_{tot} splits up:
 I_1 through R_1 and I_2 through R_2

Charge is conserved: $I_{\text{tot}} = I_1 + I_2$

More charge will be able to travel
through the path of least resistance

If $R_1 > R_2$, then $I_2 > I_1$

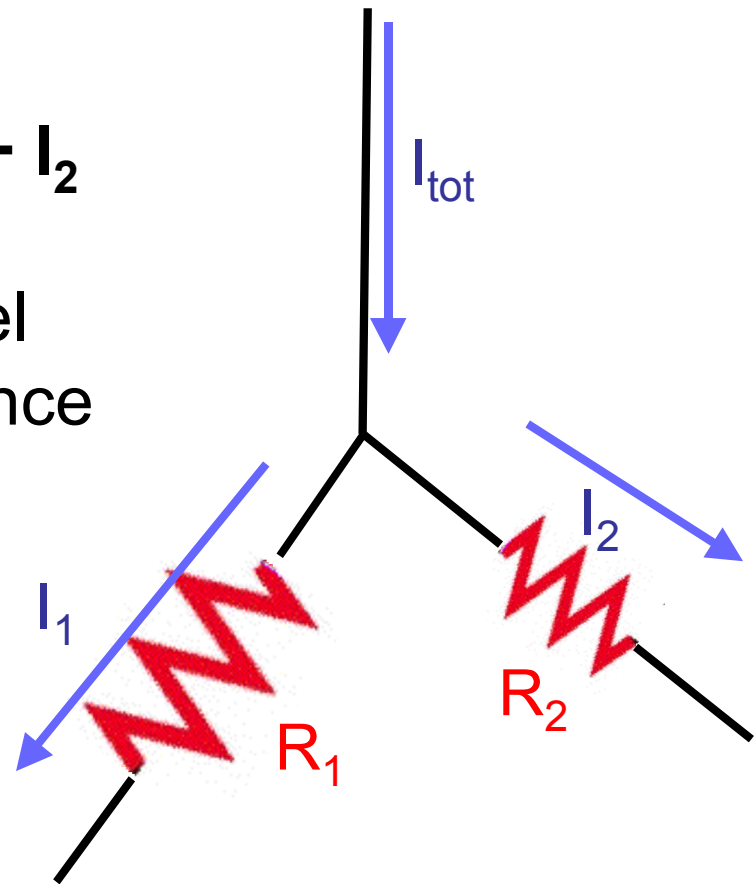

Resistors in Parallel

Note: ΔV across each resistor is the same


$$I = I_1 + I_2 = \Delta V / R_1 + \Delta V / R_2 = \Delta V(1/R_1 + 1/R_2)$$

$$\Delta V = I / (1/R_1 + 1/R_2)$$

$$\Delta V = I R_{eq}$$

$$R_{eq} = 1 / (1/R_1 + 1/R_2)$$

$$1/R_{eq} = (1/R_1 + 1/R_2)$$

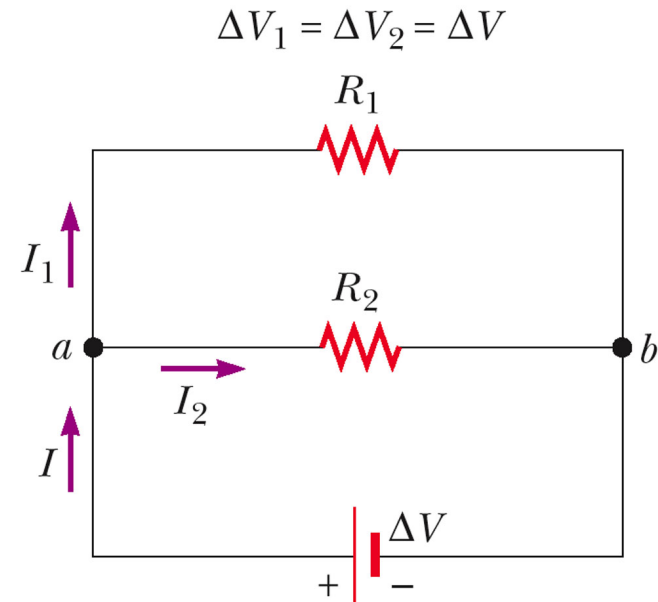


© 2006 Brooks/Cole - Thomson

For N resistors in parallel:

$$1/R_{eq} = 1/R_1 + 1/R_2 + \dots + 1/R_N$$

Understanding the parallel law

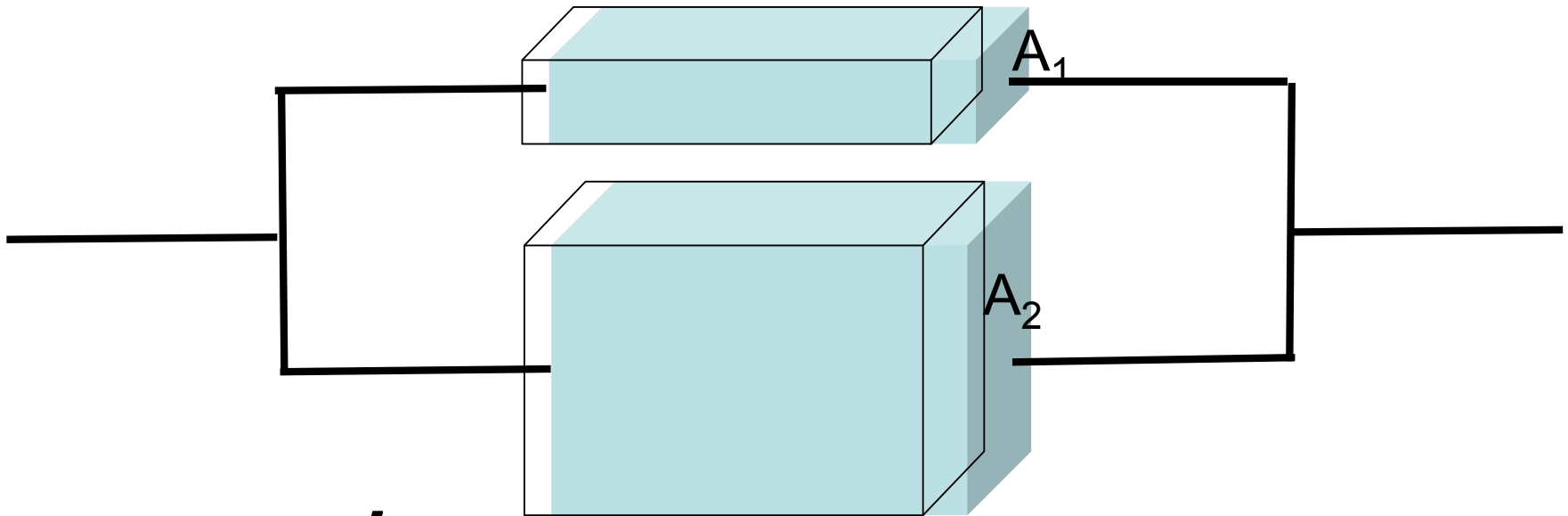

$$R = \rho \frac{L}{A}$$

R is prop.to $1/A$

$$A_{\text{tot}} = A_1 + A_2$$

A_{tot} prop.to $1/R_1 + 1/R_2$

R_{tot} prop.to $1/A_{\text{tot}}$

$1/R_{\text{tot}}$ prop.to $1/R_1 + 1/R_2$

Example:

Find the current in each resistor.

$$I_1 = \Delta V / R_1 = 18\text{V} / 3\Omega = 6\text{A}$$

$$I_2 = \Delta V / R_2 = 18\text{V} / 6\Omega = 3\text{A}$$

$$I_3 = \Delta V / R_3 = 18\text{V} / 9\Omega = 2\text{A}$$


(Total $I = 11\text{A}$)

Find the power dissipated in each resistor:

$$P_1 = I_1 \Delta V = 6\text{A} \times 18\text{V} = 108\text{ W}$$

$$P_2 = I_2 \Delta V = 3\text{A} \times 18\text{V} = 54\text{ W}$$
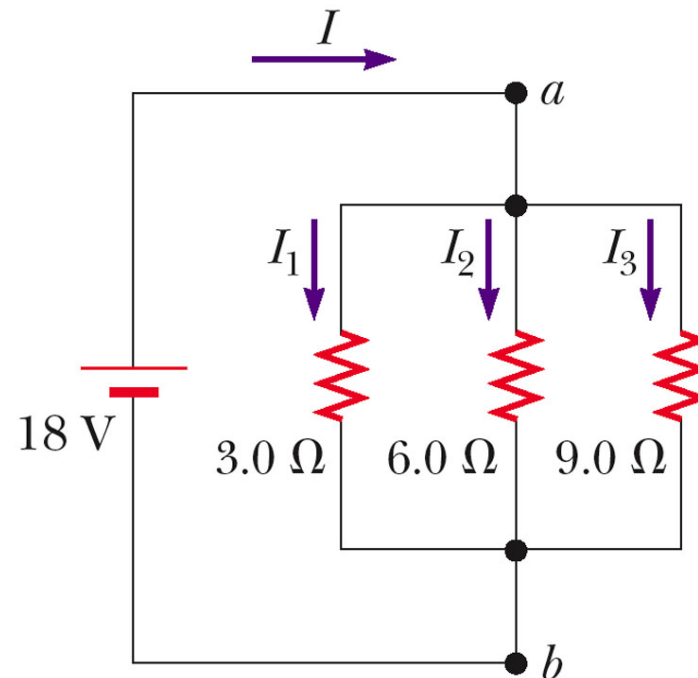
$$P_3 = I_3 \Delta V = 2\text{A} \times 18\text{V} = 36\text{ W}$$



$$\text{Total } P = 198\text{ W}$$

Example:

Find R_{eq} :


$$\begin{aligned} 1/R_{eq} &= 1/R_1 + 1/R_2 + 1/R_3 = \\ &1/(3\Omega) + 1/(6\Omega) + 1/(9\Omega) = \\ &11/(18\Omega) \end{aligned}$$

$$R_{eq} = (18/11)\Omega = 1.64 \Omega$$

Find the power dissipated in the equivalent resistor:

$$P = (\Delta V)^2/R_{eq} = (18V)^2/1.64\Omega = 198 \text{ W}$$
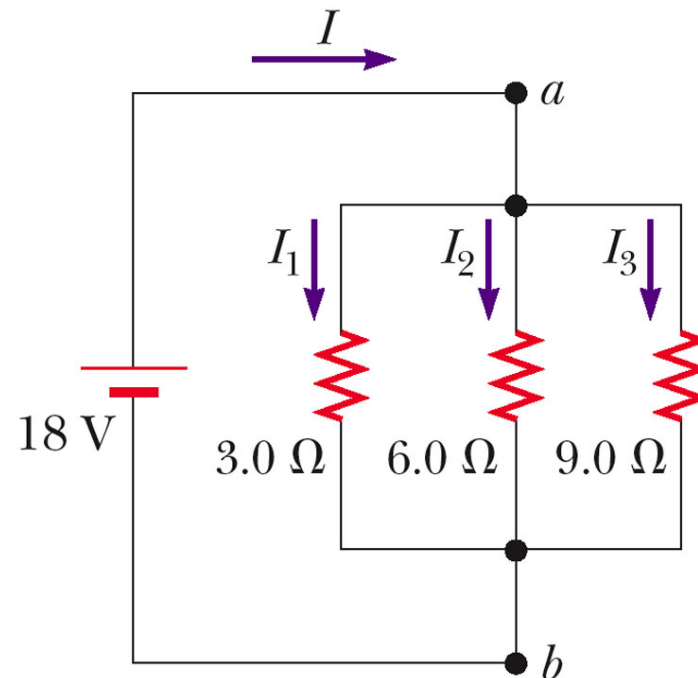
$$\text{Also, } P = I\Delta V = 11A \times 18V = 198W$$



© 2006 Brooks/Cole - Thomson

Comparing resistors and capacitors

Resistors in series are like capacitors in parallel. Resistors in parallel are like capacitors in series.


$$R \propto L \text{ and } C \propto 1/L$$

$$R \propto 1/A \text{ and } C \propto A$$

What happens when you have resistors in series AND in parallel?


Find R_{eq} through multiple steps:

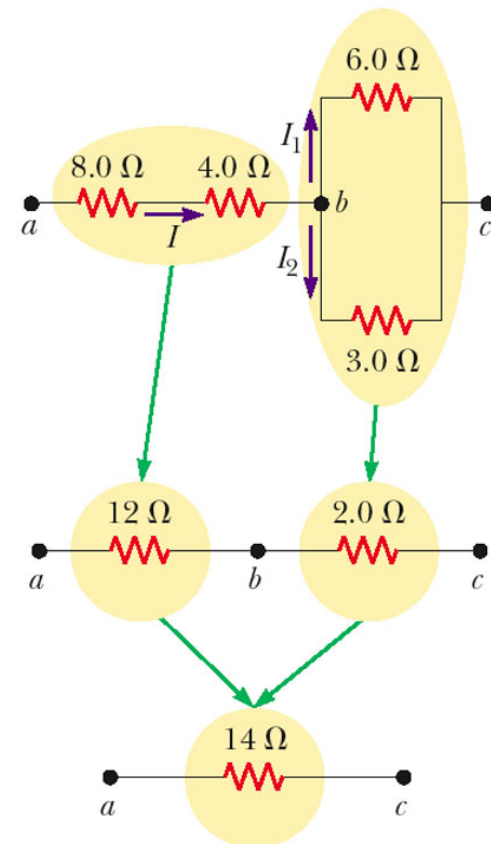1. Connect in series
2. Then connect in parallel
3. Repeat #1-2 as needed




The next 3 slides cover quick quizzes 21.5-21.7; I did not have time to review them in lecture Tuesday

Quick Quiz 21.5

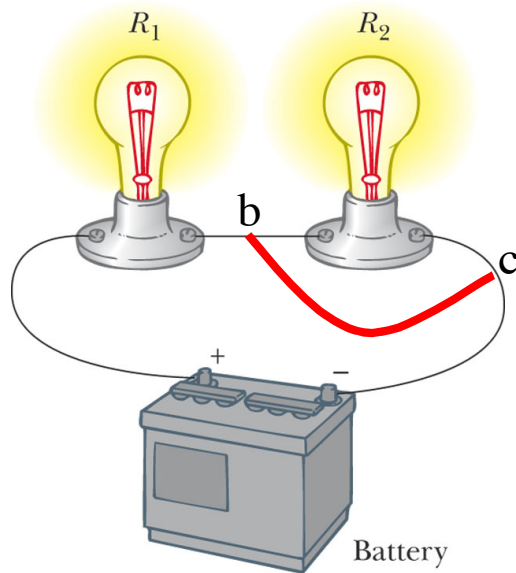

© 2005 Brooks/Cole - Thomson

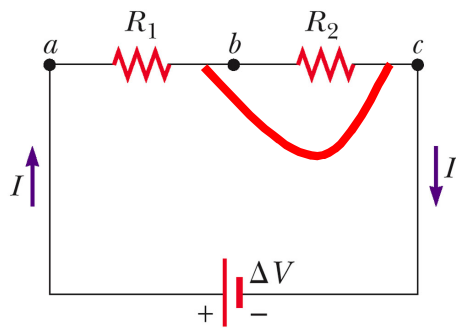

© 2005 Brooks/Cole - Thomson

Use a piece of conducting wire to connect points b & c, bypassing R_2 .

What happens to the brightness of Bulb 2?

It goes out.

What happens to the brightness of Bulb 1?

$$\Delta V = I_{\text{orig}}(R_1 + R_2)$$


$$\Delta V = I_{\text{new}}(R_1)$$

$$I_{\text{new}} > I_{\text{orig}}$$

Brightness of Bulb 1 increases due to increased power due to increased current.

Quick Quiz 21.6:

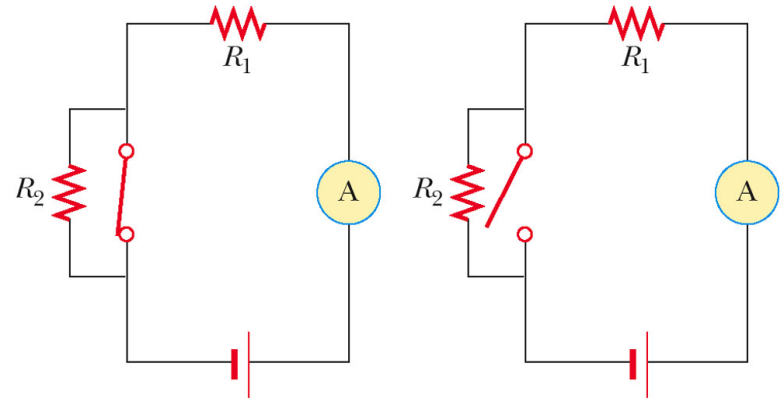Current I_{orig} is measured in the ammeter with the switch closed. When the switch is opened, what happens to the reading on the ammeter?



© 2006 Brooks/Cole - Thomson


Initially, all current flows through switch, bypassing R_2 .
 $\Delta V = I_{\text{orig}} R_1$

When switch is opened, all current is forced through R_2 ; we have a circuit with two resistors in series.

$$\Delta V = I_{\text{new}}(R_1 + R_2) = I_{\text{new}}(R_{\text{eq}})$$

$R_{\text{eq}} > R_1$ and ΔV remains fixed, so $I_{\text{new}} < I_{\text{orig}}$. (current decreases)

Quick Quiz 21.7

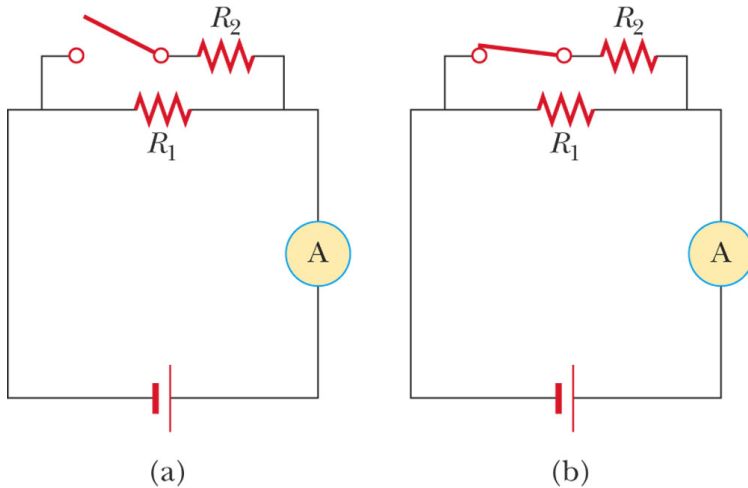

Initially: switch closed, no current through R_2 . Current in R_1 , measured with ammeter. When the switch is opened, current begins to flow through R_2 . What happens to the reading on the ammeter?

$$\text{Initially, } \Delta V = I_{\text{init}} R_1$$

$$\text{Then, } \Delta V = I_{\text{final}} R_{\text{eq}}$$

For R 's in parallel, R_{eq} is $<$ individual R 's.

$$\text{So } I_{\text{final}} > I_{\text{init}}$$