

# Physics 1B: Electricity & Magnetism, Fall 2010

## Quiz #3, Nov. 2, 2010

This is version **A!**

Useful coefficients:  $g = 9.8 \text{ m s}^{-2}$ ; Unit of elementary charge  $e = 1.6 \times 10^{-19} \text{ C}$   
Mass of proton,  $m_p =$  Mass of neutron,  $m_n = 1.67 \times 10^{-27} \text{ kg}$ ; Mass of electron,  $m_e = 9.11 \times 10^{-31} \text{ kg}$   
Coulomb's constant,  $k_e = 8.99 \times 10^9 \text{ N m}^2 \text{ C}^{-2}$   
Permittivity of free space  $\epsilon_0 = \frac{1}{4\pi k_e} = 8.85 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$   
Prefixes: milli (m) =  $10^{-3}$ ; micro ( $\mu$ ) =  $10^{-6}$ ; nano (n) =  $10^{-9}$ ; pico (p) =  $10^{-12}$ ; fempto (f) =  $10^{-15}$   
1 eV =  $1.6 \times 10^{-19} \text{ J}$

**Questions 1–3:** You are given a circuit consisting of 7 identical capacitors, each with capacitance 14 mF, connected IN SERIES with a 9-V battery.

1. What is the voltage drop across each individual capacitor?

- a. 0.78 V
- b. 1.29 V
- c. 2.0 V
- d. 7.0 V
- e. 9.0 V

2: Calculate the equivalent capacitance.

- a. 0.14 mF
- b. 0.5 mF
- c. 2 mF
- d. 49 mF
- e. 14 mF

3: While the capacitors are all kept connected to the battery, a dielectric material with a dielectric constant  $\kappa = 2$  is inserted into the gaps of each capacitor. What is the ratio of the equivalent capacitance now to that derived in problem 1, i.e., what is  $C_{\text{eq},2} / C_{\text{eq},1}$  ?

- a. 2
- b.  $2/7$
- c.  $1/2$
- d.  $7/2$
- e. 14

Solution for No. 1: The sum of the voltage drops across the capacitors must equal 9 V. With

each capacitor being equal,  $\Delta V = 9/7 = \mathbf{1.29 \text{ V}}$  for each.

Solution for No. 2: Let  $C$  denote the capacitance on each individual capacitor.

$$\frac{1}{C_{eq,1}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} = \frac{7}{C}$$

$$\frac{1}{C_{eq,1}} = \frac{1}{14mF} + \frac{1}{14mF} + \frac{1}{14mF} + \frac{1}{14mF} + \frac{1}{14mF} + \frac{1}{14mF} + \frac{1}{14mF} = \frac{7}{14mF} = \frac{1}{2mF}$$

$$\mathbf{C_{eq,1} = \frac{C}{7} = 2 \text{ mF.}}$$

Solution for No. 3: Let  $C$  denote the original capacitance, before the dielectrics are inserted. When the dielectrics are inserted, we have  $C \rightarrow \kappa C$  on each capacitor.

$$\frac{1}{C_{eq,2}} = \frac{1}{\kappa C} + \frac{1}{\kappa C} + \frac{1}{\kappa C} + \frac{1}{\kappa C} + \frac{1}{\kappa C} + \frac{1}{\kappa C} + \frac{1}{\kappa C} = \frac{1}{\kappa} \times \frac{7}{C}$$

Taking the reciprocal of both sides, we get  $C_{eq,2} = \kappa \frac{C}{7} = \kappa C_{eq,1}$

$$\mathbf{\text{So } C_{eq,2} / C_{eq,1} = \kappa = 2}$$

-----  
4. Consider an electron moving in a circuit which consists of five resistors connected in series with a battery. The five resistors,  $R_a$ ,  $R_b$ ,  $R_c$ ,  $R_d$ ,  $R_e$ , have resistances of  $19\Omega$ ,  $15\Omega$ ,  $10\Omega$ ,  $25\Omega$ , and  $1\Omega$  respectively, and the battery supplies an EMF of  $19 \text{ V}$ . The drop in potential energy is greatest when traversing which resistor?

- a.  $R_a$
- b.  $R_b$
- c.  $R_c$
- d.  $R_d$
- e.  $R_e$

Solution:  $\Delta PE$  is related to  $\Delta V$  as  $\Delta U = q\Delta V$ , so we need to identify the largest drop in  $\Delta V$ . This will occur for the resistor with the largest value of resistance,  $\mathbf{R_d}$ . Furthermore, the current is identical at all points in the circuit, so  $\Delta V = IR$  holds for each resistor separately, and the largest  $\Delta V$  occurs at the resistors with the largest value of  $R$ .

-----  
5. What is the maximum number of hair dryers (each consuming power at a rate of  $1000\text{W}$ ) you can connect in parallel in a  $120\text{-V}$  home circuit without tripping the home's  $45\text{-Amp}$  circuit breaker?

- a. 3
- b. 4
- c. 5
- d. 6
- e. 7

Solution: Each hair draw must draw a current of  $I = P/\Delta V = 1000\text{W}/120\text{V} = 8.33\text{ A}$ . The total current needed to operate  $N$  hair dryers is  $8.33N$  Amps. 5 hair dryers draws 41.67 Amps, but 6 hair dryers would draw 50 A and thus trip the circuit breaker. The answer is **5**.

-----

6. You have two cylindrical resistors, A and B. Both are made of platinum. Their lengths are identical. The radius of A is one half that of B. Resistor A is to be operated at  $20^\circ\text{C}$ . Resistor B is to be operated at  $120^\circ$ .  $\alpha$  for platinum is a constant in this temperature range:  $3.92 \times 10^{-3} (\text{ }^\circ\text{C})^{-1}$ . Find the ratio of their resistance values,  $R(A)/R(B)$ .

- a) 0.35
- b) 0.70
- c) 1.43
- d) 2.87
- e) 5.56

SOLUTION: We use  $R = \rho l / A$  for each resistor, and can form their ratio of resistance values  $\frac{R(A)}{R(B)} = \frac{\rho_A L_A / A_A}{\rho_B L_B / A_B} = \frac{\rho_A L_A A_B}{\rho_B L_B A_A}$ .

We are given that  $L_A = L_B$ .

When you halve the radius, you decrease the cross-sectional area by a factor of 4. So the area of A is one-fourth that of B:  $A_B = 4 A_A$

Now we must calculate  $\rho_A/\rho_B$ :

We can use  $\rho_B = \rho_A [1 + \alpha(T - T_0)]$

where  $T = 120^\circ\text{C}$  and  $T_0$  is  $20^\circ\text{C}$  (reference temperature).

$(T - T_0) = 100^\circ\text{C}$ .

$\alpha(T - T_0) = 0.392$

$\rho_B/\rho_A = [1 + \alpha(T - T_0)] = 1.392$

$\rho_A/\rho_B = 1 / 1.392$

Finally, we have  $\frac{R(A)}{R(B)} = \frac{1}{1.392} \times \frac{4}{1} = \mathbf{2.87}$

-----

7. You are given three samples of different metals, and you can determine the resistance  $R$  for each of them at temperatures of  $65^\circ\text{F}$  and at  $458^\circ\text{F}$  ( $R_0$  and  $R$ , respectively):

Sample	$R_0$ at $T=65^\circ\text{F}$	$R$ at $T=458^\circ\text{F}$
Palladium (Pd)	1.00 $\Omega$	1.81 $\Omega$
Nickel (Ni)	10.00 $\Omega$	16.00 $\Omega$
Brass	2.00 $\Omega$	2.44 $\Omega$
Tin (Sn)	2.00 $\Omega$	3.96 $\Omega$

Rank these metals in order from the highest temperature coefficient of resistivity  $\alpha$  to the lowest (assume  $\alpha$  is constant over this temperature range).

- a. Sn, Pd, Ni, Brass
- b. Brass, Pd, Ni, Sn

- c. Ni, Sn, Brass, Pd
- d. Ni, Brass, Sn, Pd
- e. Sn, Ni, Pd, Brass

Solution: Consider the equation for the dependence of resistance as a function of temperature,

$$R = R_0 [1 + \alpha(T - T_0)]: \text{ it can be re-written as}$$

$$R/R_0 = [1 + \alpha(T - T_0)]$$

We are given T and T<sub>0</sub>, which are the same for all three samples. Whichever metal has the highest ratio of R/R<sub>0</sub> must have the highest value of [1 + α(T - T<sub>0</sub>)] and thus the highest values of α.

R/R<sub>0</sub> for Pd is 1.81.

R/R<sub>0</sub> for Ni is 1.60.

R/R<sub>0</sub> for brass is 1.22.

R/R<sub>0</sub> for Sn is 1.98.

These are the values of [1 + α(T - T<sub>0</sub>)]. So,

αΔT for Pd is 0.81

αΔT for Ni is 0.60

αΔT for brass is 0.22

αΔT for Sn is 0.98

And (T - T<sub>0</sub>) is the same for all four samples. We conclude that **α is highest for Sn. Pd is second-highest. Ni is third-highest. α is lowest for brass.**

-----

8. The dielectric strength of “substance X” is  $4.0 \times 10^7$  N/C and its dielectric constant is 4. You are given a parallel plate capacitor whose plates are separated by 1 mm. When filled with substance X between its plates, this capacitor can hold a charge of 0.01 C before dielectric breakdown occurs. Find the maximum amount of energy that can be stored in the capacitor without dielectric breakdown occurring.

- a. 50 J
- b. 800 J
- c. 2 J
- d. 15 J
- e. 200 J

Solution: We can use Energy  $U = 1/2 Q (\Delta V_{\max})$  where  $\Delta V_{\max}$  is the maximum voltage difference which can be applied before dielectric breakdown occurs.

$$\Delta V_{\max} = E_{\max} d = (4.0 \times 10^7 \text{ V/m})(0.001\text{m}) = 4.0 \times 10^4 \text{ V}.$$

$$U = 1/2 Q (\Delta V_{\max}) = 1/2 (0.01 \text{ C}) (40000\text{V}) = \mathbf{200 \text{ J}}$$

An alternate solution would have been to calculate the capacitance:

$$C = Q/(\Delta V) = (0.01\text{C}) / 40000 \text{ V} = 2.5 \times 10^{-7} \text{ F} = 250 \text{ nF}.$$

$$\text{We can then use } U = 1/2 C (\Delta V_{\max})^2 = 1/2 (2.5 \times 10^{-7} \text{ F})(40000\text{V})^2 = \mathbf{200 \text{ J}}.$$

-----  
9. Two capacitors are connected in parallel with a battery: capacitor A has capacitance  $C_A$ ; capacitor B has capacitance  $C_B$ ;  $C_A$  is greater than  $C_B$ . Which of the following statements is true?

- a. There is a larger potential difference across capacitor A.
- b. There is a larger potential difference across capacitor B.
- c. There is the same quantity of charge stored on each capacitor.
- d. There exists the same potential difference across both capacitors.
- e. There is more charge stored on capacitor B.

Solution: For circuit elements connected in parallel with a battery, the voltage drop across them must be identical (**confirming choice D** and ruling out choices A and B). Because the values of capacitance are not equal, and using  $C = Q/\Delta V$ , there must be differing amounts of charge stored on each capacitor (ruling out C). Finally, because  $C_A > C_B$ , and because  $Q = C\Delta V$ , we have  $Q_A > Q_B$  (in contradiction to choice e).

-----  
10. If  $1.0 \times 10^{20}$  electrons enter a  $20\Omega$  resistor in a duration of one minute and four seconds, what is the potential difference  $\Delta V$  across the resistor?

- a) 0.31 V
- b) 5.0 V
- c) 32 V
- d) 50 V
- e) 80 V

Solution: We can calculate the current using  $I = \Delta Q/\Delta T$ .

$$\Delta Q = 1.0 \times 10^{20} \text{ electrons} \times (1.6 \times 10^{-19} \text{ C per electron}) = 1.6 \times 10^1 \text{ C} = 16 \text{ C}.$$

$$I = \Delta Q/\Delta T = 16\text{C} / 64 \text{ seconds} = 0.25 \text{ Amps}.$$

$$\Delta V = IR = (0.25\text{A})(20\Omega) = \mathbf{5.0 \text{ V}}.$$

-----

Please double-check that your intended choices are bubbled in correctly on the scantron form. Double-check that you've bubbled in the test version correctly – this is version A! And please double-check to make sure you have bubbled in your Exam Code Number on the scantron form correctly!