

$\mu = 4 \cdot \pi \cdot 10^{-7} = 1.26 \cdot 10^{-6} \text{ N/A}^2$

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question

Situation 31.1

An 18 mH solenoid inductor is wound on a form 0.80 m in length and 0.10 m in diameter. A coil is tightly wound around the solenoid at its center. The coil resistance is 5.0 ohms. The mutual inductance of the coil and solenoid is 60 μ H. At a given instant, the current in the solenoid is 300 mA, and is decreasing at the rate of 2.5 A/s.

1) In Situation 31.1, at the given instant, the magnetic energy of the solenoid, in μ J, is closest to


- A) 500 B) 800 C) 600 D) 400 E) 700

$$\frac{1}{2} LI^2 = \frac{1}{2} 18 \times 10^{-3} \cdot (.3)^2 = 8.1 \times 10^{-5} = 810 \mu\text{J}$$

2) In Situation 31.1, at the given instant, the induced current in the coil is closest to

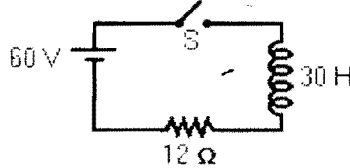- A) 40 μ A B) 25 μ A C) 30 μ A D) 35 μ A E) 45 μ A

$$\mathcal{E}_c = M \frac{dI_1}{dt} = 60 \times 10^{-6} \cdot 2.5$$



$$I = \frac{\mathcal{E}_c}{R} = \frac{60 \times 10^{-6} \cdot 2.5}{5} = 30 \times 10^{-6} \text{ Amps}$$

An R-L circuit has a 60 V battery, a 30 H inductor, a 12 ohm resistor, and a switch S, in series, as shown. Initially, the switch is open, and there is no magnetic flux in the inductor. At time $t = 0$ s, the switch is closed.

3) In Figure 31.1, when the resistor voltage is equal to the inductor voltage, the current in the circuit is closest to

- A) 2.5 A B) 1.5 A C) 1.0 A D) 2.0 A E) 3.0 A

$$V_R = I(t)R \quad V_L = I'(t)L$$

$$\frac{1}{2} = e^{-R/L t} \quad \ln 2 = R/L t \quad t = \frac{L}{R} \ln 2 = 1.73 \text{ sec}$$

$$I(t) = I(\infty) - (I(\infty) - I(0))e^{-R/L t} = \frac{\mathcal{E}}{R} - \frac{\mathcal{E}}{R}e^{-R/L t} \Rightarrow I(t) \approx 2.5$$

An R-L circuit is shown, with a 10 ohm resistor and an ideal 40 H inductor, that has zero resistance. At time $t = 0$ s, there is a 12A current in the circuit.

4) In Figure 31.2, when the current is decreasing at the rate of 2.0 A/s, the time t is closest to

- A) 2.8 s B) 1.2 s C) 2.4 s D) 6 s E) 2.0 s

$$I(t) = I_0 e^{-R/L t}$$

$$I'(t) = -\frac{R}{L} I_0 e^{-R/L t} = -2.0$$

$$e^{-R/L t} = \frac{2L}{RI_0} \Rightarrow \frac{R}{L} t = \ln\left(\frac{RI_0}{2L}\right)$$

$$t = \frac{L}{R} \ln\left(\frac{RI_0}{2L}\right) = 1.62$$