

Easy

1 $V = 9V$ The load resistor is in series
 $I = 117mA$ with the battery, so we have.
 $R_L = 72\Omega$ $R_{TOT} = R_L + R_i$ and using Ohm's
 $R_i = ?$ law, $R = V/I$

$$R_{TOT} = 9V / 117mA = 76.9\Omega = R_L + R_i = 72\Omega + R_i$$


Thus $R_i = 76.9\Omega - 72\Omega$

$$R_i = 4.9\Omega$$

2 $R_1 = 4\Omega$ (a) series connection, find R_{eq} .
 $R_2 = 8\Omega$ Def: $R_{eq}(\text{series}) = R_1 + R_2 + R_3 = 24\Omega = R_{series}$
 $R_3 = 12\Omega$

$V = 24V$ (b) current through each resistor: since they are in series, they all have the same current: $I = V/R_{eq} = 24V / 24\Omega$
 $I = 1.00 \text{ Amps}$

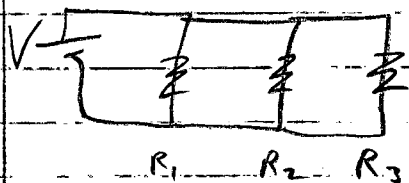(c) parallel connection \rightarrow Find R_{eq} : $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$



$$R_{eq} = \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{12} \right)^{-1} = 2.2\Omega$$

Find current in each resistor: Since each resistor is connected in parallel to the battery, we can use Ohm's law separately for each one.

$$I_1 = V/R_1 = 6A$$

$$I_2 = V/R_2 = 3A$$


$$I_3 = V/R_3 = 2A$$

Note $I_1 + I_2 + I_3 = 11 \text{ Amps}$

which is the total current that goes through the battery. We confirm it w/ $I_{TOT} = V/R_{eq} = 11 \text{ amps}$. ✓

Easy

4

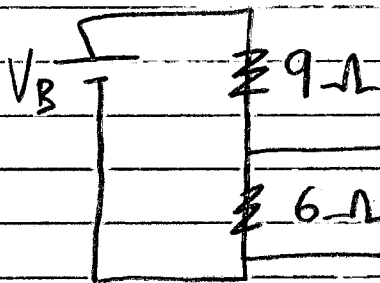

connect resistors in series

(a)

This tells us the current through the circuit is $I = V/R = 12V/6\Omega = 2A$

And therefore the total Voltage = $I R_{eq} = 2A (6+9)\Omega$

(b) now connect in parallel

$V_{Batt} = 30V$




$R_1 = 6\Omega$
 $R_2 = 9\Omega$

$I(9\Omega) = .25A$

Thus the voltage drop across the resistor is $V = IR = (9\Omega)(.25A)$
 $V(R_2) = 2.25V$

And since it is in parallel with the battery, this must also be the voltage drop across the battery. $V_B = 2.25V$


6

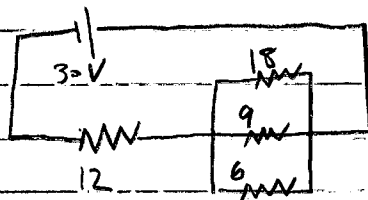

Find R_{eq}

First note the 18/9/6 Ω resistors are in parallel together with $R_{intermediate} = R_{int}$
 $R_{int} = \left(\frac{1}{18} + \frac{1}{9} + \frac{1}{6}\right)^{-1} = 3\Omega$

Now we have:

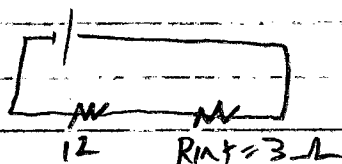


These two resistors are in series so we add them

$R_{eq} = 15\Omega$

Easy

7 Find R_{eq} between a & b

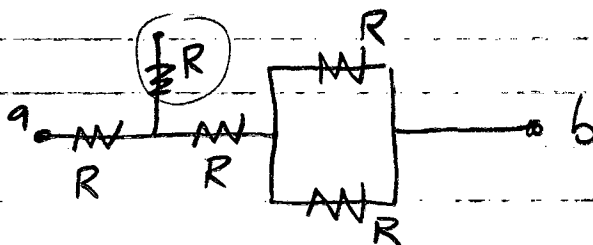


Note, since the circled resistor is not a part of any path from $a \rightarrow b$, it will not contribute to the R_{eq} .

Now, the two resistors closest to (b) are in parallel so $R_{part} = (1/R + 1/R)^{-1} = R/2$.

Finally, this R_{part} is in series with the first two resistors closer to (a). [remember to ignore the vertical circled resistor].

$$R_{eq} = R + R + R/2 = \boxed{5R/2 = R_{eq}}$$

17 Determine the current in each branch:

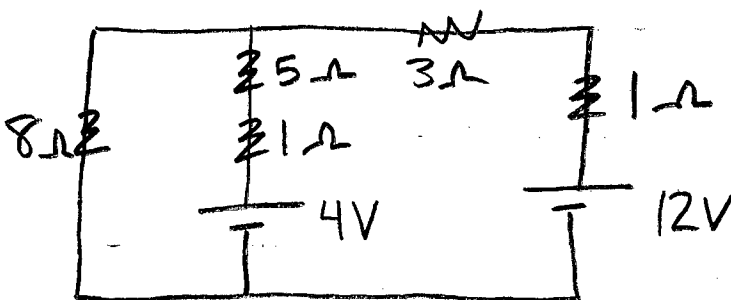


First define a current direction in each branch. Note, it does not matter if you pick correctly, so just choose the direction you think the current goes and don't worry. If you pick wrong, you will get a (-) sign in your answer.

- You can also redraw the circuit simpler by combining the resistors in series. \rightarrow

EASY

Continuing 17

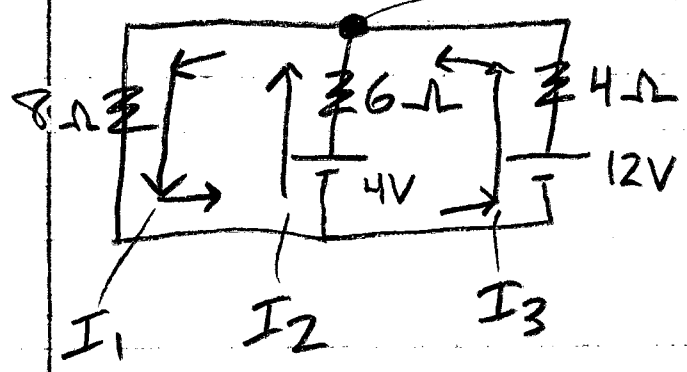

Apply the junction rule

① $I_2 + I_3 = I_1$

Now apply Kirchhoff's loop rule ($\sum \Delta V = 0$) to each:

Left loop

② $+4V - (6\Omega)I_2 - (8\Omega)I_1 = 0$

Right loop

③ $+12V - (4\Omega)I_3 + 6\Omega I_2 - 4V = 0$
 ↑ b/c opposing current ↑ b/c opposing battery

Now solve the equations

② $4 - 6I_2 - 8I_1 = 0 \rightarrow 4 - 6I_2 - 8I_2 - 8I_3 = 0$ (2')

③ $8 + 6I_2 - 4I_3 = 0$

① $I_1 = I_2 + I_3$ — sub into ②

rewrite ② $4 - 14I_2 - 8I_3 = 0$
 " [③ $8 + 6I_2 - 4I_3 = 0$] $\times (-2)$ and add

$[4 + (8)(-2)] + [-14 + (6)(-2)]I_2 + [-8 + (-4)(-2)]I_3 = 0$

$-12 - 26I_2 = 0 \rightarrow I_2 = -6/13 \text{ AMPS}$

from eq 2'


$I_3 = [4 - 14(-6/13)] / 8 = I_3 = +17/13 \text{ A}$

$I_1 = I_2 + I_3 = +11/13 \text{ A} = I_1$

(-) means true dir. is opposite to my arrow.

19

EASY

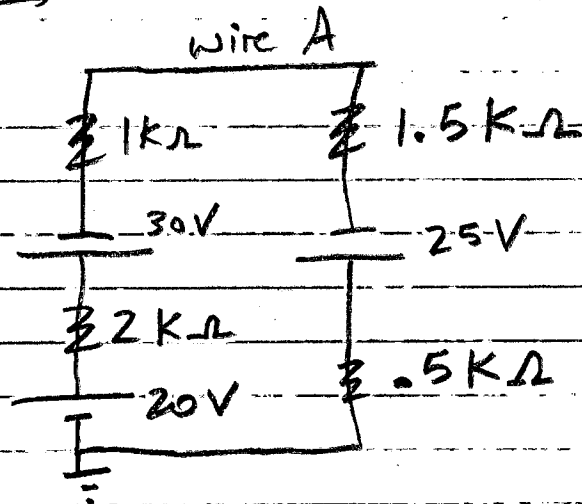

- (a) Find total current: define I as clockwise and apply loop rule.

$$+20V - 2k\Omega I - 30V - 1k\Omega I - 1.5k\Omega I + 25V - 0.5k\Omega I = 0$$

$$15V - (5k\Omega)I = 0 \rightarrow I = 15V / 5k\Omega = \boxed{3mA = I}$$

- (b) Find potential of wire A rel. to ground:

Work your way from ground up to wire A and add up all the ΔV as you go:

$$+20V - (2k\Omega)(3mA) - 30V - (1k\Omega)(3mA) = \text{Wire A voltage}$$

$$20 - 6 - 30 - 3 = \boxed{-19V = V_{\text{wire A}}}$$


- (c) Find ΔV across the 1500Ω resistor.

Using Ohm's law, $\Delta V = IR = (3mA)(1500\Omega)$

$$\boxed{\Delta V = 4.5V}$$

Easy

20

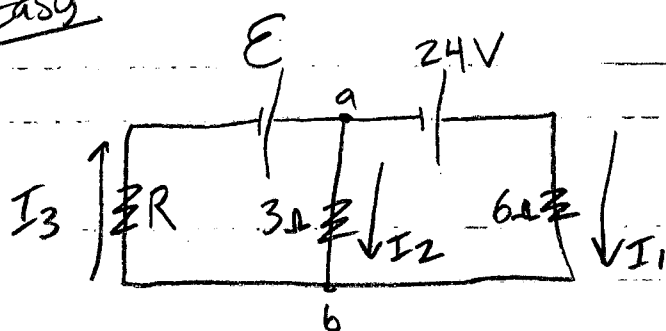Find I_2 & I_3 given

$$I_1 = 3A$$

Junction Rule at (a) $I_3 = I_2 + I_1$ Right hand loop Rule: $+24V - 6I_1 + 3I_2 = 0$
(clockwise)

$$\frac{24V - 6(3)}{-3} = I_2 = -2 \text{ Amps} \quad (\text{opp dir})$$

Note, since E & R are not given we cannot use that loop.

$$I_3 = -2A + 3A$$

$$I_3 = 1A$$

31

$C = 6 \mu F$
 $R = 2 M\Omega$
 $\mathcal{E} = 20V$
(in series)

(a) time constant?

$$\tau = RC = (6 \mu F)(2 M\Omega) = 12s = \tau$$

(b) max charge on capacitor?



When max charged, the capacitor contains the full voltage drop of the battery. $Q = CV \rightarrow Q_{max} = CV_{Batt}$

$$Q_{max} = (6 \mu F)(20V) = 120 \mu C = Q_{max}$$

32

$C = 20 \mu F$
 $R = 100 \Omega$
 $\mathcal{E} = 9V$
(series)

(a) $\tau = RC = 2ms = 2 \times 10^{-3}s = \tau$ (b) $Q_{max} = CV_{Batt} = 1.8 \times 10^{-4}C = Q_{max}$ (c) $Q(t = 1\tau = RC)$

$$Q = Q_{max} (1 - e^{-t/\tau}) = Q_{max} (1 - e^{-1})$$

$$= Q_{max} (1 - e^{-1}) = .632 Q_{max}$$

$$Q = 1.14 \times 10^{-4}C$$

Easy


37 $P = 1300\text{ W}$ heater
 $P = 1000\text{ W}$ toaster
 $P = 1500\text{ W}$ grill } parallel to 120V circuit

(a) current for each? $P = IV \rightarrow I = P/V$

$I_{\text{heater}} = 10.8\text{ A}$; $I_{\text{toaster}} = 8.3\text{ A}$; $I_{\text{grill}} = 12.5\text{ A}$

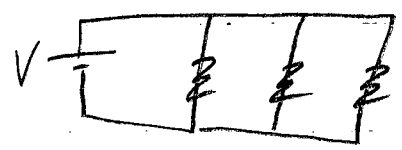(b) A 30A circuit breaker will cause the circuit to shut down b/c $I_{\text{TOT}} = 31.6\text{ A}$

38 lamp $R = 150$
 heater $R = 25$
 fan $R = 50$ } parallel
 120V



(a) $I_{\text{TOT}} = ?$ $I = V/R \rightarrow I_{\text{lamp}} = 0.8\text{ A}$
 $I_{\text{heat}} = 4.8\text{ A}$
 $I_{\text{fan}} = 2.4\text{ A}$

Since currents in parallel will all go through battery

$I_{\text{TOT}} = \Sigma I = 8\text{ Amps} = I_{\text{TOT}}$

(b) $\Delta V_{\text{fan}} = \Delta V_{\text{batt}}$ since it is in parallel: $\Delta V_{\text{fan}} = 120\text{ V}$


(c) current in lamp (from a) = $I_{\text{lamp}} = 0.8\text{ A}$

(d) Power out of heater? $P = IV = (4.8\text{ A})(120\text{ V})$

$P_{\text{heater}} = 576\text{ Watts}$

Medium

5

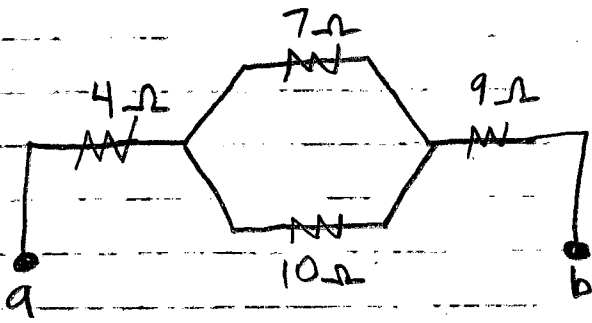

(a) Find R_{eq} ($a \rightarrow b$)

- Two middle resistors in parallel $\left(\frac{1}{7} + \frac{1}{10}\right)^{-1} = 4.1 \Omega$
- first, equivalent, third = series

(b) $V_{ab} = 34V$

find current everywhere

→ First, we know the equivalent current is $I_{eq} = V/R_{eq}$

$I_{eq} = 1.99 A$. This current flows through

The first and last (4Ω & 9Ω) resistors b/c there are no branches for current to split off.

For the two center resistors, the current will split between them, such that the voltage drop (IR) for each is the same.

$$I_7(7) = I_{10}(10) \quad \& \quad I_7 + I_{10} = I_{eq} = 1.99 A$$

$$I_7 = \frac{10}{7} I_{10} \quad \downarrow \quad \left(\frac{10}{7} + 1\right) I_{10} = 1.99 A$$


$$I_{10} = .819 A$$

$$I_7 = 1.17 A$$

$$I_4 = I_9 = 1.99 A$$

Medium

8

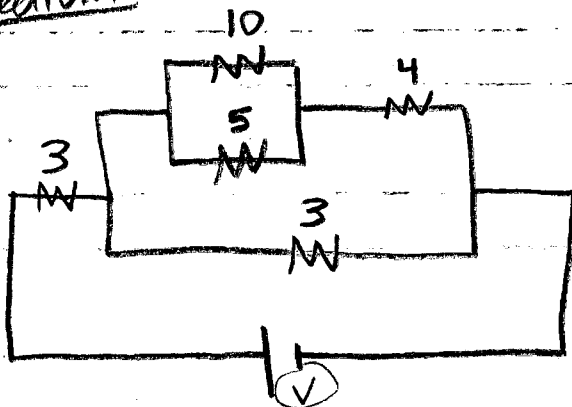


[all units are Ohms]

① Find R_{eq} : 1) combine 10 & 5 parallel:
 $(\frac{1}{10} + \frac{1}{5})^{-1} = 10/3$

2) combine $10/3$ & 4 in series: $10/3 + 4 = 22/3$

3) Redraw:

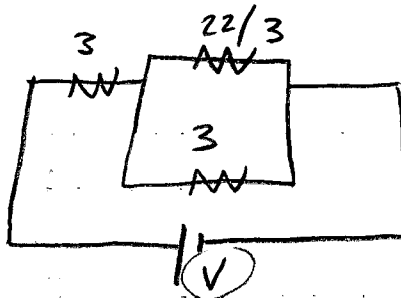

4) combine $22/3$ & 3 in parallel: $(\frac{3}{22} + \frac{1}{3})^{-1} = 2.13$

5) combine 2.13 & 3 in series: $2.13 + 3 = 5.13$

Thus $R_{eq} = 5.13 \Omega$


② $P = 4.00 \text{ W}$
find Voltage

We know $P = IV = V^2/R$ so $\sqrt{PR} = V$

$$V = \sqrt{(4 \text{ W})(5.13 \Omega)} = V = 4.53 \text{ Volts}$$

Med

9 Drawn slightly diff than book

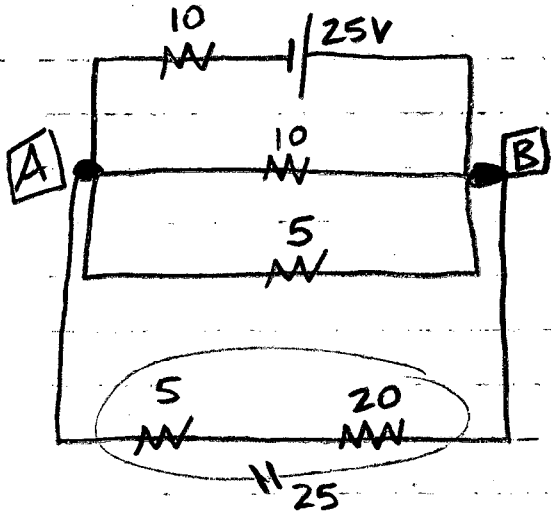


(a) Find current in 20Ω resistor

Notice that the bottom 3 branches are all in parallel so we combine them

$$\left(\frac{1}{10} + \frac{1}{5} + \frac{1}{25}\right)^{-1} = 2.94$$

Redraw:

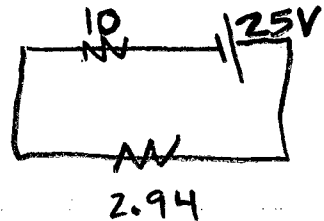

$$\begin{aligned} \text{Thus } R_{eq} &= 10 + 2.94 \\ &= 12.94 \Omega \end{aligned}$$

Now we can find the current out of the battery

$$I_T = V/R_{eq} = 1.93 \text{ A}$$

$$\text{Now lets find } V_{AB} = 25 \text{ V} - (10 \Omega) I_T = 5.7 \text{ V}$$

This potential difference (5.7V) is the voltage across all 3 parallel branches of the circuit.

$$\text{Thus, } I_{20} = \Delta V / R_{\text{Branch}} = 5.7 \text{ V} / 25 \Omega = \boxed{.23 \text{ A} = I_{20}}$$


(b) Find $V_{AB} = 5.7 \text{ V}$ (from above)

(The total resistance of the branch containing the 20Ω resistor is actually 25Ω.)

10

Med

R_A, R_B parallel 6V Battery:

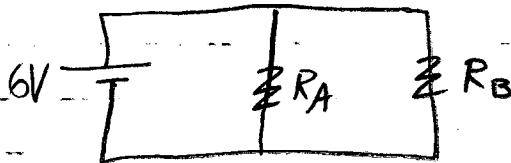


$I_B = 2A$

→ This tells us

$R_B = V/E_B = 6V/2A = \boxed{R_B = 3\Omega}$

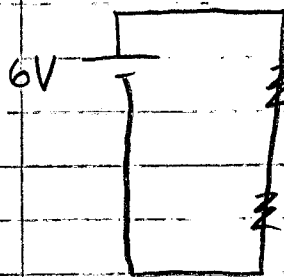R_A, R_B in series 6V bat we measure $V_A = 4V$



$R_A; V_A = I R_A = 4V$


Because $V_A + V_B = V_{total}$

$R_B; V_B = I R_B = 6V - 4V = 2V$

$I = \frac{V_B}{R_B} = \frac{2V}{3\Omega} = \frac{2}{3}A$

Thus $R_A = \frac{V_A}{I} = \frac{4V}{(2/3)A} = \boxed{6\Omega = R_A}$

13

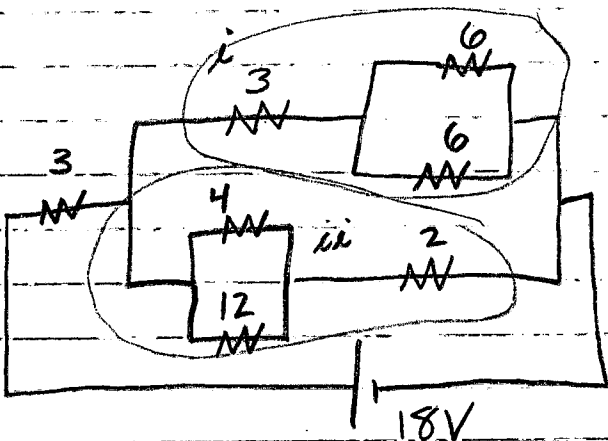

All resistances in Ohm's


a) Find I in 12Ω resistor:

First simplify i & ii

i) $3 + (\frac{1}{6} + \frac{1}{6})^{-1} = 6$

ii) $(\frac{1}{4} + \frac{1}{12})^{-1} + 2 = 5$

Now redraw

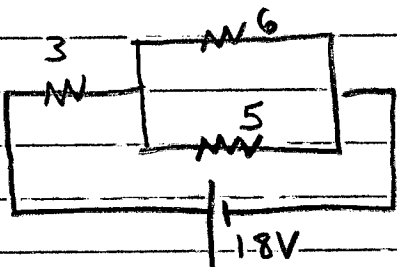

Find Req:


$Req = 3 + (\frac{1}{6} + \frac{1}{5})^{-1} = \boxed{5.73\Omega = Req}$

$I_{TOT} = V/Req = \boxed{3.14A = I_{TOT}}$

Med

13 - continued

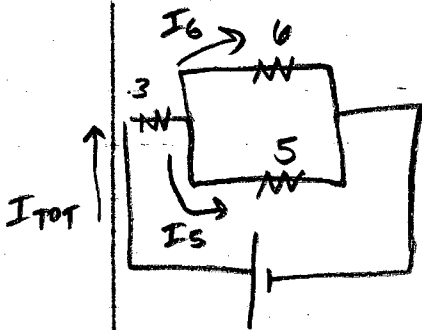$I_{TOT} = 3.14$ A will split up among the branches of the circuit. Since parallel, $\Delta V_6 = \Delta V_5$




$$I_{TOT} = I_6 + I_5$$

$$\Delta V_6 = \Delta V_5 \rightarrow I_6(6) = I_5(5)$$

$$I_6 = \frac{5}{6} I_5 \quad \text{sub into top}$$

$$I_{TOT} = 3.14 = \left(\frac{5}{6} I_5\right) + I_5 \rightarrow I_5 = 1.71 \text{ A}$$

Recall how we got (5)

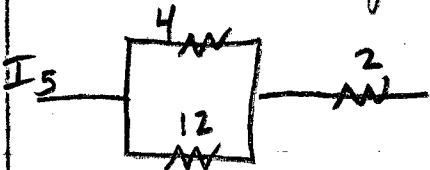

so I_5 will split again into I_4 and I_{12} where $V_4 = V_{12}$ because they are in parallel.

$$I_5 = I_4 + I_{12} \quad \& \quad V_4 = V_{12} \rightarrow 4I_4 = 12I_{12}$$

sub in here


$$I_4 = 3I_{12}$$

$$I_5 = 1.71 \text{ A} = 3I_{12} + I_{12}$$

$$I_{12} = .43 \text{ A}$$

(FINAL ANSWER)

22

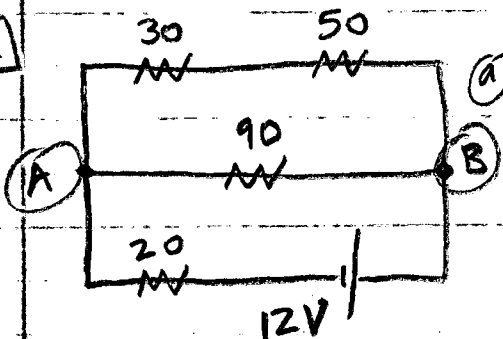

(a) Find power delivered to 50 Ω :

First find R_{eq} to get I_{TOT}

$R_{eq} = (30 + 50)$ in parallel with 90
Then in series with 20 Ω

$$R_q = \left(\frac{1}{80} + \frac{1}{90}\right)^{-1} + 20$$

$$\rightarrow R_q = 62.4 \Omega \rightarrow I_{TOT} = .1925 \text{ A}$$

Med

22 cont → Now find current through 50-Ω branch
I_{TOT} will split, but since the branches are in parallel,
The voltage across each will be a constant.

$$I_{TOT} = I_{80} + I_{90} \quad V_{80} = V_{90}$$

$$(80) I_{80} = (90) I_{90}$$

$$I_{TOT} = I_{80} + \frac{8}{9} I_{80}$$

$$I_{90} = \frac{8}{9} I_{80}$$


$$I_{80} = .102 A$$

→ Notice this is the current through the 50-Ω resistor.

Finally,

$$power = P = I^2 R = (I_{80})^2 (50 \Omega) = .52 \text{ Watts} = P_{50}$$

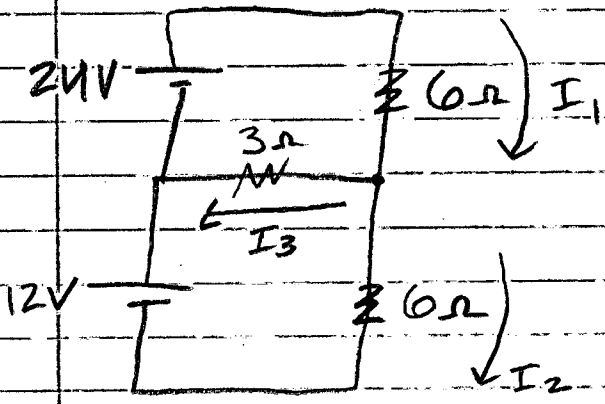25 Find all currents: (draw it with series resistors combined)



Junction rule: ① $I_1 = I_2 + I_3$

loop rules:

① top loop clockwise:

$$② 24V - 6I_1 - 3I_3 = 0$$

bottom loop clockwise

$$③ 12V + 3I_3 - 6I_2 = 0$$

Now we have 3 eq & 3 unk:

$I_1 = I_2 + I_3$ sub into 2nd eq.

$$24V - 6(I_2 + I_3) - 3I_3 = 0 \rightarrow 24V - 6I_2 - 9I_3 = 0$$

rewrite eq 3 $\rightarrow 12V - 6I_2 + 3I_3 = 0$ subtract

$$I_2 = (12 + 3I_3) / 6 = 2.5A = I_2$$

$$12V + 0I_2 - 12I_3 = 0$$


$$I_3 = 1A$$

$$I_1 = 3.5A$$

Med

27

Find all currents:

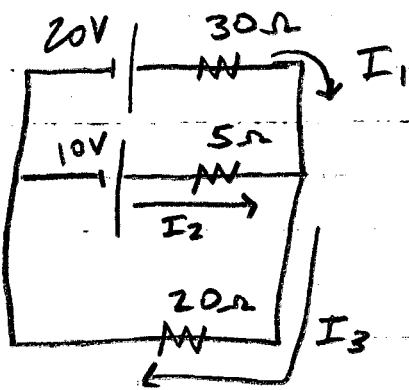

$$\textcircled{1} I_1 + I_2 = I_3$$

top loop $\textcircled{2} 20V - 30I_1 + 5I_2 - 10V = 0$
 bot loop $\textcircled{3} 10V - 5I_2 - 20I_3 = 0$

sub $\textcircled{1}$ into $\textcircled{3}$ & reduce

$$10V - 5I_2 - 20(I_1 + I_2) = 0$$

rewrite $\textcircled{2}$ $10V - 20I_1 - 25I_2 = 0$
 $(10V - 30I_1 + 5I_2 = 0) \times 5$ & add

$$60V - 170I_1 = 0 \quad \boxed{I_1 = 6/17 A}$$

$$I_2 = (10 - 20I_1) / 25 = \boxed{2/17 A = I_2} \quad (.353 A)$$

$$I_3 = I_1 + I_2 \rightarrow \boxed{I_3 = 8/17 A} \quad (.471 A)$$

33

Series RC

$$R = 1 M\Omega$$

$$C = 5 \mu F$$

$$E = 30V$$

Find $Q(10s)$ on the capacitors

$$\text{We have } Q(t) = Q_{max}(1 - e^{-t/RC})$$

$$\text{So we find } Q_{max} = CE = 150 \mu C = Q_{max}$$

$$\text{and we find } (1 - e^{-10/RC}) = (1 - e^{-10/5}) = .865$$

$$\text{Thus } Q(10) = (150 \mu C)(.865)$$

$$\boxed{Q(10) = 130 \mu C}$$

Med

35

Capacitor in RC has $Q = 0.6 Q_{\max}$ at $t = .95$
Find $RC = \tau$


$Q = Q_{\max} (1 - e^{-t/RC})$ is the equation to use
and solve for RC

$$\frac{Q}{Q_{\max}} = .6 = 1 - e^{-.9/RC}$$

$$\ln(1 - .6) = -.9/RC \rightarrow RC = \frac{-.9}{\ln(1 - .6)} = \boxed{.985 \tau}$$

48

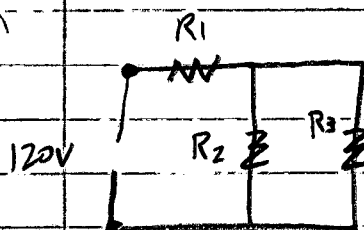60 W } $P = \Delta V^2 / R \rightarrow R = \frac{\Delta V^2}{P} = 240 \Omega$ per bulb
120 V }



(a) To get total power we need R_{eq}

$$R_{eq} = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 360 \Omega$$

The power dissipated is $P_{TOT} = V^2 / R_{eq}$

$$P_{TOT} = (120V)^2 / 360 \Omega = \boxed{40W}$$

(b) ΔV for each bulb?

$\Delta V = IR$ so we need current through R_1 ; This is I_{TOT}


$$I_{TOT} = V / R_{eq} = 1/3 A; \Delta V_1 = IR_1 = \boxed{\Delta V_1 = 80V}$$

$$\Delta V_2 = \Delta V_3 \text{ (b/c parallel)} = 120V - \Delta V_1 \text{ (b/c Kirchhoff loop rule)}$$

$$\boxed{\Delta V_2 = \Delta V_3 = 40V}$$

Med

49

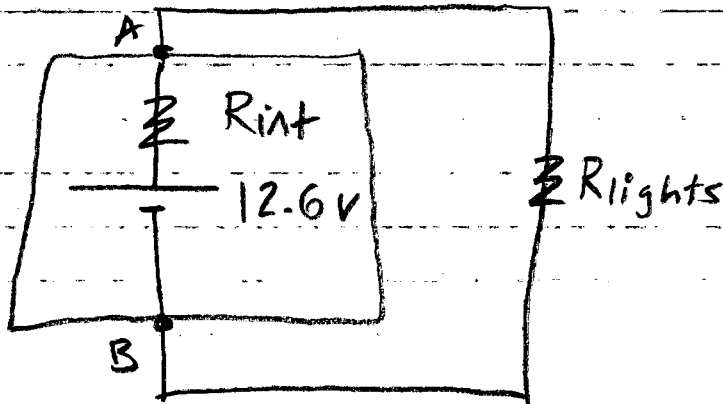

$$R_{int} = .08 \Omega$$

$$R_{lights} = 5 \Omega$$

(a) Find $\Delta V_{lights} : \Delta V_{light} = I R_{light} \rightarrow$ find I

$$I = V/R_{eq} = 12.6V / 5.08 \Omega = 2.48 A$$

$$\Delta V_{light} = 12.4 V$$

(b) Now starter motor draws an additional 35A from battery.

This lowers V_{AB} because the extra current passes R_{int} .

$$\Delta V_{light} = 12.6V - \Delta V_{int} = I_{light} R_{light}$$

$$\Delta V_{int} = I_{tot} R_{int} = (35 + I_{light} A)(.08 \Omega) = 2.8 + .08 I_{light}$$

Combine 2 boxed equations by eliminating V_{int} . (add)

$$12.6V = I_{light} R_{light} + (35A + I_{light})(.08 \Omega)$$

Solve for $I_{light} = \frac{12.6V - (35A)(.08 \Omega)}{5 \Omega + .08 \Omega} = 1.93 A$


$$\Delta V_{light} = I_{light} R_{light} = (1.93A)(5 \Omega)$$

$$\Delta V_{light} = 9.65 V$$


965

Hard

47

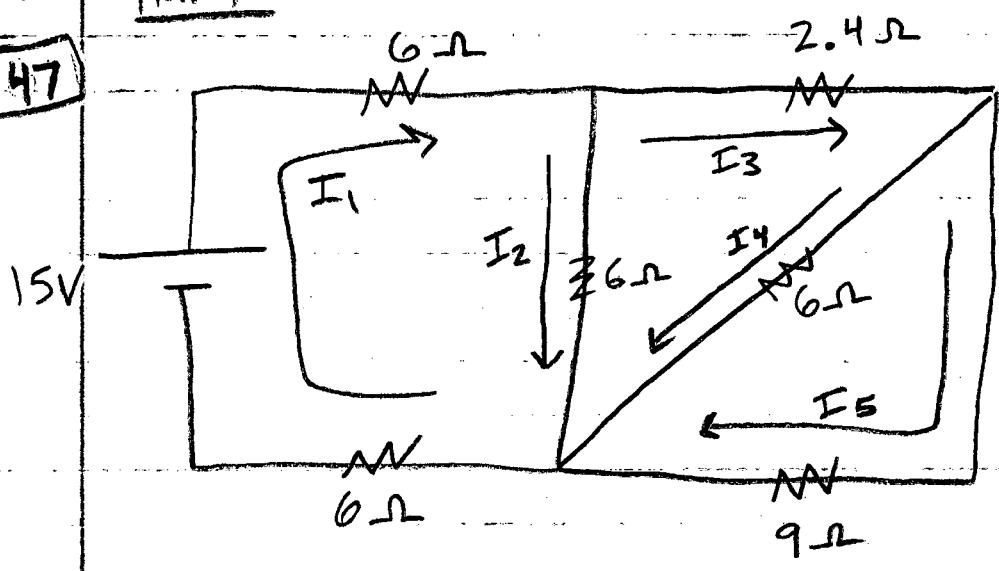

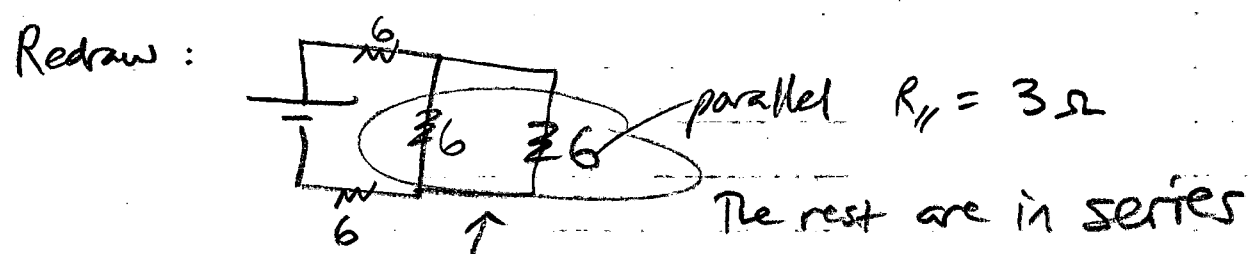- a) Find R_{eq}
 Right hand side $6\Omega \parallel 9\Omega$ are in parallel
 $(\frac{1}{6} + \frac{1}{9})^{-1} = 3.6\Omega \rightarrow$ This is series w/ 2.4
 Right side $R = 2.4 + 3.6 = 6\Omega$



$R_{eq} = 6 + 3 + 6 = 15\Omega$

- b) Find all currents.
 $I_1 = I_{TOT} = V/R_{eq} = \boxed{I_1 = 1A}$

Splits into $I_2 \parallel I_3$ evenly b/c the parallel branches have equal resistance.

$I_2 = I_3 = .5A$

I_3 splits into $I_4 \parallel I_5$ unevenly
 $\Delta V_{top} = \Delta V_{Bottom}$ (parallel)
 $6I_4 = 9I_5$

Hard

47-cont

$$.5 = I_4 + I_5$$

$$I_4 = \frac{3}{2} I_5$$

$$.5 = (1 + 3/2) I_5$$

$$I_5 = .2A$$

$$I_4 = .5 - .2 \rightarrow$$

$$I_4 = .3A$$

(c) ΔV on each resistor

$\Delta V = IR$ for each one


	ΔV	Power out
top left:	$\Delta V = (1A) 6\Omega = 6V$	6W
bot left:	$\Delta V = (1A) 6\Omega = 6V$	6W
center mid:	$\Delta V = (.5A) 6\Omega = 3V$	1.5W
top right:	$\Delta V = (.5A) (2.4\Omega) = 1.2V$.6W
center right:	$\Delta V = (.3A) (6\Omega) = 1.8V$.54W
bot right:	$\Delta V = (.2A) (9\Omega) = 1.8V$.36W

(d) power dissipated in each resistor = $I^2 R$

→ see above right for answers.

Hard

5.6

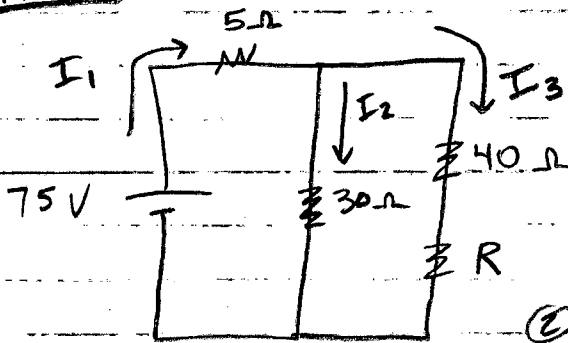

Given

$$P_R = 20\text{W} = I_3^2 R = I_3 V_R$$

$$\textcircled{1} I_1 = I_2 + I_3$$

$$\textcircled{2} \text{ right loop: } 30I_2 = (40 + R)I_3$$

$$\textcircled{3} \text{ left loop: } 75\text{V} - 5I_1 - 30I_2 = 0$$

Find R

sub $\textcircled{1}$ into $\textcircled{3}$: $75\text{V} - 35I_2 - 5I_3 = 0$
 solve $\textcircled{2}$ & the new eq for I_2

$$\textcircled{2} \frac{(40+R)I_3}{30} = I_2$$

$$\text{New} \frac{75\text{V} - 5I_3}{+35} = I_2$$

Next
Page \rightarrow

set equal to each other & sub $I_3 = \sqrt{\frac{20}{R}}$ (from top given)

$$\frac{(40+R)\sqrt{\frac{20}{R}}}{30} = \frac{75 - 1\sqrt{20/R}}{7 \cdot 35} \rightarrow \text{solve for R}$$

This is a tough equation, but since you have a square root, you should try values for R that give a whole number for $\sqrt{20/R}$ term. Possible values for this would be $R = 5, 20, 80$

Work out each side for these values & you find $R = 20\Omega$ is the solution.

$$\frac{(40+20)\sqrt{\frac{20}{20}}}{30} = 2 = \frac{75 - 1\sqrt{20/20}}{7} = 2$$

Thus $R = 20\Omega$

see next page for better solution!!

Col Same as #9.

Hard

56 - cont.

We can set the two equations for I_2 equal to each other and we get

$$\frac{40I_3 + RI_3}{30} = \frac{15V - 5I_3}{357}$$

reduce it and
using $P = I_3^2 R = 20$
we can plug $\left[\frac{IR = 20}{I_3} \right]$

$$7(40I_3 + 20/I_3) = 30(15V - I_3)$$

Now multiply by I_3 & combine terms

$$280I_3^2 + 140 = 450I_3 + 30I_3^2 = 0$$

$$310I_3^2 - 450I_3 + 140 = 0 \quad \text{apply quadratic formula}$$

$$I_3 = 1A \text{ or } 0.452A$$

Back to $P = I_3^2 R = 20W$ we have $R = \frac{20W}{I_3^2}$

$$R = \frac{20W}{(1A)^2} = 20\Omega$$

2 possible values

$$\text{OR } R = \frac{20W}{(0.452A)^2} = 98\Omega$$

Prob 61 This is the same as prob #9.