

# Physics 1B - Chap 21 HW Solutions

①

## Easy

1  $V_{rms} = 100V$   
 $R = 5\Omega$

(a)  $V_{max} = \sqrt{2} V_{rms} = \boxed{141V = V_{max}}$

(b)  $V_{rms} = I_{rms} R \rightarrow I_{rms} = \frac{100V}{5\Omega} = \boxed{20A}$

(c)  $I_{max} = \sqrt{2} I_{rms} = \boxed{28.3A}$

(d) Power dissipated (ave) =  $I_{rms}^2 R = (20A)^2 5\Omega = \boxed{2000W}$

2 (a)  $P_{ave} = 75W$   
 $f = 60Hz$   
 $V_{max} = 170V$

$$P_{ave} = \frac{V_{ave}^2}{R} = \left(\frac{V_{max}}{\sqrt{2}}\right)^2 \frac{1}{R}$$

$$R = \frac{V_{max}^2}{2 P_{ave}} = \frac{170^2}{2(75)} = \boxed{193\Omega}$$

(b)  $P_{ave} = 100W$

$$R = \frac{170^2}{2(100)} = \boxed{145\Omega}$$

8  $C = 2.2\mu F$

(a)  $\Delta V_{rms} = 120V$

$$f = 60Hz \rightarrow \omega = 2\pi f = 120\pi$$

$$\Delta V_{max} = I_{max} X_c \quad \text{and} \quad X_c = \frac{1}{2\pi f C}$$

$$I_{max} = \frac{\Delta V_{max}}{X_c} = (\sqrt{2} V_{rms}) 2\pi f C = \sqrt{2} (120) (120\pi) (2.2\mu F)$$

$$\boxed{I_{max} = 0.141A}$$

Easy

②

8- $\mu\text{F}$

$$\textcircled{b} \Delta V_{\text{rms}} = 240 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$I_{\text{max}} = \sqrt{2} (240) (100\pi) (2.2 \mu\text{F}) \rightarrow I_{\text{max}} = 0.235 \text{ A}$$

II

$$f = 60 \text{ Hz}$$

$$V_{\text{max}} = 170 \text{ V}$$

$$\Delta V_{\text{max}} = I_{\text{max}} X_C$$

$$I_{\text{rms}} = 0.75 \text{ A}$$

$$\Delta V_{\text{max}} = (\sqrt{2} I_{\text{rms}}) \left( \frac{1}{2\pi f C} \right)$$

find C

$$C = \frac{\sqrt{2} I_{\text{rms}}}{2\pi f} \frac{1}{V_{\text{max}}} = \frac{\sqrt{2} (0.75 \text{ A})}{2\pi (60) (170 \text{ V})}$$

$$C = 16.5 \mu\text{F}$$

15

$$X_L = 54 \Omega$$

$$f = 60 \text{ Hz}$$

$I_{\text{max}} = ?$  when connected to  $f = 50 \text{ Hz}$  &  $100 \text{ V}_{\text{rms}}$

step 1: find L:  $X_L = 2\pi f L \rightarrow L = \frac{X_L}{2\pi f} \rightarrow L = 0.143 \text{ H}$

$$I_{\text{max}} = \frac{V_{\text{max}}}{X_{L(\text{new})}} = \frac{\sqrt{2} V_{\text{rms}}}{2\pi f L} = \frac{\sqrt{2} (100 \text{ V})}{2\pi (50) (0.143)}$$

$$I_{\text{max}} = 3.15 \text{ A}$$

Easy

16

$f = 20 \text{ Hz}$   
 $V_{\text{rms}} = 50 \text{ V}$   
 $I_{\text{max}} = 80 \text{ mA}$   
 $L = ?$

$$I_{\text{max}} = \frac{V_{\text{max}}}{X_L} = \frac{\sqrt{2} V_{\text{rms}}}{2\pi f L}$$

solve for L

$$L = \frac{\sqrt{2} V_{\text{rms}}}{2\pi f I_{\text{max}}}$$

$$L = \frac{\sqrt{2} (50)}{2\pi (20)(80 \text{ mA})} \rightarrow \boxed{L = 7.0 \text{ H}}$$

19

$C = 40 \mu\text{F}$   
 $R = 50 \Omega$   
 $V_{\text{rms}} = 30 \text{ V}$   
 $f = 60 \text{ Hz}$

(a)  $I_{\text{rms}} = ? ; X_C = \frac{1}{2\pi(60)(40 \mu\text{F})} = 66.3 \Omega$

$$V_{\text{rms}} = I_{\text{rms}} \cdot Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{50^2 + (0 - 66.3 \Omega)^2}$$

$$Z = 83 \Omega$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \boxed{.36 \text{ A}}$$

(c)  $\Delta V_C = I X_C$   
 $= (.36 \text{ A})(66.3 \Omega)$   
 $\Delta V_{\text{rms}} = 23.9 \text{ V}$

(b)  $V_{\text{rms}}$  on Resistor

$$V_{\text{rms}} = I_{\text{rms}} R = .36 \text{ A} (50 \Omega) = \boxed{18 \text{ V}}$$

(d) phase angle =  $\phi = \tan^{-1} \frac{X_L - X_C}{R} = \frac{0 - 66.3}{50}$

$$\phi = -53^\circ$$

Easy

28  $R = 50 \Omega$       a) find power factor and  $P_{ave}$   
 $C = 30 \mu F$   
 $f = 60 \text{ Hz}$       first,  $X_C = \frac{1}{2\pi f C} = 88.4 \Omega$   
 $V_{rms} = 100V$

Thus  $\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) = \tan^{-1} \left( \frac{0 - 88.4}{50} \right)$

$\phi = -60.5^\circ$ , so  $\cos \phi = .492$

$P_{ave} = V_{rms} I_{rms} \cos \phi$ ; we need  $I_{rms}$  first

$P_{ave} = V_{rms} \frac{V_{rms}}{Z} \cos \phi$

$P_{ave} = \frac{(100V)^2 (.492)}{102 \Omega}$

$P_{ave} = 48.4 W$

$I_{rms} = \frac{V_{rms}}{Z}$  so we need  $Z$

$Z = \sqrt{R^2 + (X_L - X_C)^2}$

$Z = \sqrt{50^2 + (0 - 88.4)^2} = 102$

b) repeat w/  $L = 0.3 H$  instead of capacitor

Now  $X_C = 0$  and  $X_L = 2\pi f L = 113 \Omega$

and  $Z = \sqrt{50^2 + 113^2} = Z = 123.7 \Omega$

$\phi = \tan^{-1} \left( \frac{113}{50} \right) = 66.1^\circ$        $\cos \phi = .404$

$P_{ave} = \frac{V_{rms}^2}{Z} \cos \phi = \frac{100^2}{123.7} (.404) = 32.7 W = P_{ave}$

Easy

40) Need 6Vrms, have 120Vrms

$N_{primary} = 400 \text{ turns}, I_s = 500 \text{ mA}$

a)  $\Delta V_2 = \frac{N_2}{N_1} \Delta V_1$ , so since we start with 120 V and we only want to end with 6V, we want **less turns.**

b) Find  $I_{primary}$

We can get this using the fact that power in = power out so  $I_p V_p = I_s V_s$

or  $I_p = I_s \frac{V_s}{V_p} = 500 \text{ mA} \left( \frac{6V}{120V} \right) = \boxed{25 \text{ mA}}$

c) find  $N_{secondary}$  from  $\Delta V_2 = \frac{N_2}{N_1} \Delta V_1$ , we obtain

$N_2 = N_1 \frac{\Delta V_2}{\Delta V_1} = 400 \left( \frac{6V}{120V} \right) = \boxed{20 \text{ turns}}$

Medium

12

$\omega = 120\pi$

$\Delta V_{max} = 140V$

$C = 6 \mu F$

$L = 0 \Omega$  b/c it says "purely capacitive"

$R = 0 \Omega$

Find  $I_{rms} \rightarrow I_{rms} = \frac{V_{rms}}{X_c} = \frac{V_{max}/\sqrt{2}}{1/(2\pi f)C}$

$I_{rms} = \frac{140V/\sqrt{2}}{1/(120\pi)(6\mu F)} = \boxed{0.224A}$

18

$L = 400mH$

$C = 4.43\mu F$

$R = 500\Omega$

$f = 50Hz$

a) Find  $V_{max}$   $V_{max} = I_{max} Z$

$Z = \sqrt{R^2 + (X_L - X_C)^2}$ ; find  $X_L$  &  $X_C$

$X_L = 2\pi f L = 126\Omega$

$X_C = 1/(2\pi f C) = 719\Omega$

$I_{max} = 250mA$

$Z = \sqrt{500^2 + (126 - 719)^2} = 775\Omega$

$V_{max} = 250mA(775\Omega) = \boxed{194V}$

b) Find phase angle  $\phi$

$\phi = \tan^{-1} \frac{X_L - X_C}{R} = \tan^{-1} \left( \frac{126 - 719}{500} \right) = \boxed{-50^\circ = \phi}$

Note: The (-) sign means the voltage lags the current.

Medium

21

$R = 900 \Omega$

$X_L = 2\pi fL = 3770 \Omega$

$C = 0.25 \mu\text{F}$

$L = 2.5 \text{ H}$

$X_C = 1/2\pi fC = 2650 \Omega$

$f = 240 \text{ Hz}$

$\Delta V_{\text{max}} = 140 \text{ V}$

(a) Find  $Z$ ; need  $X_L$  &  $X_C$  first; see above

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{900^2 + 1120^2} = \boxed{1440 \Omega}$$

(b)  $I_{\text{max}} = \frac{V_{\text{max}}}{Z} = \frac{140 \text{ V}}{1440 \Omega} = \boxed{.097 \text{ A}}$

(c) phase angle:

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) = \tan^{-1} \left( \frac{1120}{900} \right) = \boxed{51.2^\circ}$$

(d) since  $\phi$  is (+), the voltage leads and the current lags.

30

$C = 200 \mu\text{F}$

$L = 100 \text{ mH}$

$R = 20 \Omega$

$V_{\text{max}} = 100 \text{ V} \rightarrow V_{\text{rms}} = 70.7 \text{ V}$

(a)  $f = 60 \text{ Hz}$  find  $P_{\text{ave}}$  and  $\cos \phi$

$$X_C = 1/2\pi fC = \underline{13.3 \Omega} \quad ; \quad X_L = 2\pi fL = \underline{37.7 \Omega}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{20^2 + 24.4^2} = \underline{\underline{31.5 \Omega}}$$

Medium

30-cont  $\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) = \tan^{-1} \left( \frac{24.4}{20} \right) = 50.7^\circ$

$\cos \phi = .634$

$P_{ave} = V_{rms} I_{rms} \cos \phi = V_{rms} \left( \frac{V_{rms}}{Z} \right) \cos \phi$

$= \frac{(70.7V)^2}{31.5 \Omega} (.634) = P_{ave} = 101W$

②  $f = 50 \text{ Hz} \rightarrow$  get new  $X_C, X_L, Z$  values

$X_C = 15.9 \Omega$   
 $X_L = 31.4 \Omega$   
 $Z = 25.3 \Omega$

$\phi = \tan^{-1} \left( \frac{31.4 - 15.9}{20} \right) = 37.8^\circ$

$\cos \phi = .79$

$P_{ave} = \frac{70.7}{25.3} (.79) = 156W = P_{ave}$

33

$R = 12 \Omega$   
 $C = 1.4 \text{ pF} = 1.4 \times 10^{-12} \text{ F}$   
 $f_0 = 88.9 \text{ MHz}$

$L = ? \quad f_0 = \frac{1}{2\pi \sqrt{LC}} \rightarrow L = \left( \frac{1}{2\pi f} \right)^2 \frac{1}{C}$

$L = \frac{1}{[2\pi (88.9 \times 10^6)]^2 (1.4 \times 10^{-12})} \rightarrow L = 2.3 \mu\text{H}$



Medium

41  $V_1 = 3600V$   
 $V_2 = 120V$

$P_2 = 1000 \text{ kW}$  @ 90% efficiency

a)  $P_1 = ?$  well  $\frac{P_2}{P_1} = 90\% = .9 \rightarrow P_1 = \frac{P_2}{.9}$

$$P_1 = \frac{1000 \text{ kW}}{.9} = \boxed{1111 \text{ kW} = P_1}$$

b) current  $I_1 = ?$

$$P_1 = I_1 V_1 \rightarrow I_1 = \frac{P_1}{V_1} = \frac{1111 \text{ kW}}{3600 \text{ V}} = \boxed{309 \text{ A}}$$

c) current  $I_2 = ?$

$$I_2 = \frac{P_2}{V_2} = \frac{1000 \text{ kW}}{120 \text{ V}} = \boxed{8.3 \text{ kA}}$$

Hard

32

① Get Reactance      ② Get Impedance

$$\begin{aligned}
 R &= 25 \Omega \\
 L &= 6 \text{ mH} \rightarrow X_L = 22.6 \Omega \\
 C &= 25 \mu\text{F} \rightarrow X_C = 10.6 \Omega
 \end{aligned}
 \left. \vphantom{\begin{aligned} R \\ L \\ C \end{aligned}} \right\} Z = \sqrt{25^2 + (22.6 - 10.6)^2}$$

$$Z = 27.7 \Omega$$

$$V_{\text{rms}} = 110 \text{ V}$$

$$f = 600 \text{ Hz}$$

③ Get  $I_{\text{rms}}$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = 0.36 \text{ A}$$

(a) get sum of voltages

$$\begin{aligned}
 \Delta V_R &= I_{\text{rms}} R = 9 \text{ V} \\
 \Delta V_C &= I_{\text{rms}} X_C = 3.82 \\
 \Delta V_L &= I_{\text{rms}} X_L = 8.14
 \end{aligned}
 \left. \vphantom{\begin{aligned} \Delta V_R \\ \Delta V_C \\ \Delta V_L \end{aligned}} \right\} \sum \Delta V = 21 \text{ Volts}$$

Thus the sum of the voltages does NOT equal the total voltage. This is because they are not in phase.

(b) Which is greatest:  $P_R, P_L, P_C$

Recall that a perfect capacitor and inductor store energy but do not lose energy. Thus the resistor is the only element with power dissipated  $P_R$

(c)  $P_{\text{ave}}(\text{total}) = I_{\text{rms}} V_{\text{rms}} \cos \phi$

but since we know only the resistor has power loss we can use

$$P = I_{\text{rms}}^2 R = (.36 \text{ A})^2 25 \Omega = \boxed{3.24 \text{ W}}$$