


Closed book. No work needs to be shown for multiple-choice questions.

1. Two charges $+Q$ and $-Q$ are separated by a distance d . What is the electric potential at the point exactly in the middle between these two charges?

- a. $+4k_e Q/d$
- b. $+2k_e Q/d$
- c. $+k_e Q/d$
- d. $-2k_e Q/d$
- e. zero.


2. Four capacitors are connected as shown below. What is the equivalent capacitance of the combination between points a and b ?

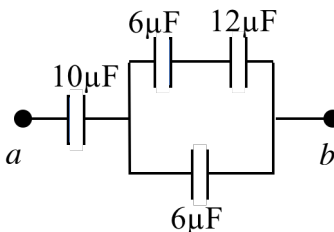- a. $12 \mu\text{F}$.
- b. $5.0 \mu\text{F}$.
- c. $20 \mu\text{F}$.
- d. $15 \mu\text{F}$.
- e. $34 \mu\text{F}$.



3. Four capacitors are connected as shown below. If a difference of potential of 18 V is applied between points a and b , what is the potential difference and the charge in the $12 \mu\text{F}$ capacitor?

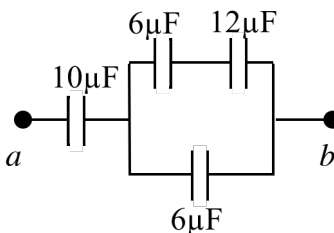- a. 18 V and $54 \mu\text{C}$.
- b. 3 V and $54 \mu\text{C}$.
- c. 6 V and $36 \mu\text{C}$.
- d. 3 V and $36 \mu\text{C}$.
- e. 6 V and $90 \mu\text{C}$.




4. Two capacitors with capacitances of $3.0 \mu\text{F}$ and $6.0 \mu\text{F}$, respectively, are connected in series. The system is connected to a 90 V battery. What electrical potential energy is stored in the $3.0 \mu\text{F}$ capacitor?

- a. $0.18 \times 10^{-3} \text{ J}$
- b. $5.4 \times 10^{-3} \text{ J}$
- c. $8.1 \times 10^{-3} \text{ J}$
- d. $2.7 \times 10^{-3} \text{ J}$
- e. $10.8 \times 10^{-3} \text{ J}$

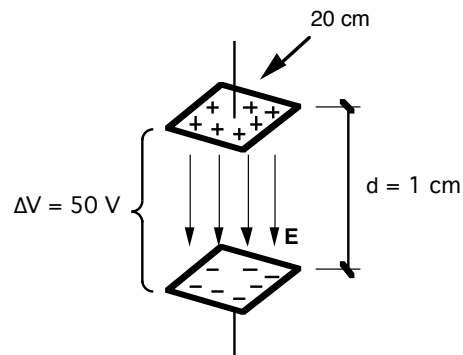5. A parallel plate capacitor is made from two square plates, 20 cm on a side. The plates are spaced 1.0 cm apart and connected to a 50 V battery. How much energy is stored in the capacitor?

- $8.9 \times 10^{-8} \text{ J}$.
- $2.2 \times 10^{-7} \text{ J}$.
- $3.5 \times 10^{-11} \text{ J}$.
- $8.9 \times 10^{-10} \text{ J}$.
- $4.4 \times 10^{-8} \text{ J}$.




6. If an electron is accelerated from rest through a potential difference of 4,800 V, find its approximate velocity at the end of this process.

- $2.0 \times 10^7 \text{ m/s}$.
- $2.8 \times 10^7 \text{ m/s}$.
- $4.2 \times 10^7 \text{ m/s}$.
- $5.6 \times 10^7 \text{ m/s}$.
- $4.6 \times 10^8 \text{ m/s}$.

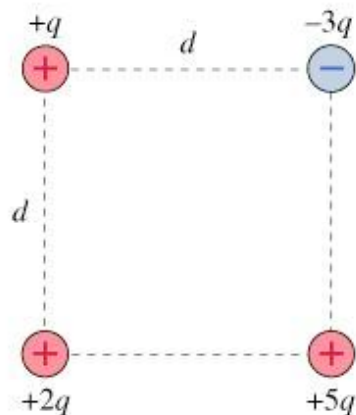
7. If the value of the charge q is 10 nC, what is the potential created by the charges $+q$, $+2q$ and $+5q$ at the point exactly where the charge $-3q$ is located? Use $d = 2\text{m}$.

- 167 V.
- 180 V.
- 225 V.
- 333 V.
- 360 V.



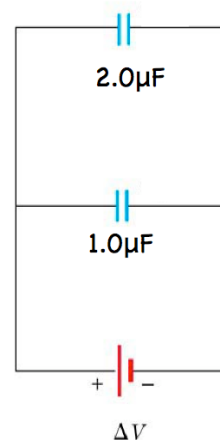8. A $2.0 \mu\text{F}$ and a $1.0 \mu\text{F}$ capacitor are connected in parallel and a potential difference, ΔV , is applied across the combination. The $2.0 \mu\text{F}$ capacitor has:

- twice the charge of the $1.0 \mu\text{F}$ capacitor.
- half the charge of the $1.0 \mu\text{F}$ capacitor.
- twice the potential difference of the $1.0 \mu\text{F}$ capacitor.
- half the potential difference of the $1.0 \mu\text{F}$ capacitor.
- none of the above.



Recall that

$$F = k_e \frac{|q_1||q_2|}{r^2}; \quad k_e = 8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2}; \quad e = 1.60 \times 10^{-19} \text{C}; \quad \epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}$$

$$m_e = 9.11 \times 10^{-31} \text{kg};$$

$$\vec{F} = q_o \vec{E}; \quad E = k_e \frac{|q|}{r^2}; \quad \Phi_E = EA \cos \theta; \quad \Phi_E = \frac{Q_{\text{inside}}}{\epsilon_0}; \quad PE_{\text{elec, point}} = k_e \frac{qq_0}{r}; \quad V_{\text{point charge}} = k_e \frac{q}{r};$$

$$\Delta PE_{\text{elec}} = q_o \Delta V; \quad C = \frac{Q}{\Delta V}; \quad C_{\text{parallel plate}} = \epsilon_0 \frac{A}{d}; \quad C_{\text{dielectric}} = \kappa \epsilon_0 \frac{A}{d}; \quad \frac{1}{C_{\text{series eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots;$$

$$C_{\text{parallel eq}} = C_1 + C_2 + C_3 + \dots; \quad \text{Energy}_{\text{capacitor}} = \frac{1}{2} Q(\Delta V) = \frac{1}{2} C(\Delta V)^2 = \frac{Q^2}{2C};$$