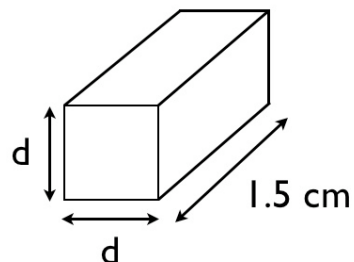


Closed book. No work needs to be shown for multiple-choice questions.

1. A $200.0\ \Omega$ resistor is constructed by forming a material of resistivity $2.5\ \Omega\cdot\text{m}$. The cross-section of this resistor is shaped like a square with side length d . The resistor is $1.5\ \text{cm}$ long. What is the value of the side length d ?

- a. 0.19 mm.
- b. 3.0 mm.
- c. 1.4 cm.
- d. 7.3 cm.
- e. 1.2 m.




2. Consider a series RC circuit for which $C = 6.0\ \mu\text{F}$, $R = 2.0 \times 10^6\ \Omega$, and $\mathcal{E} = 2.0\ \text{V}$. Find the time constant of this circuit.

- a. 6.0 s.
- b. 12 s.
- c. 24 s.
- d. $4.0\ \mu\text{s}$.
- e. 3.0 ms

3. For the circuit below the $\mathcal{E}_1 = 14\text{V}$, $\mathcal{E}_2 = 3\text{V}$ and $\mathcal{E}_3 = 20\text{V}$. What is the value of the difference of potential (voltage) in R_3 ?

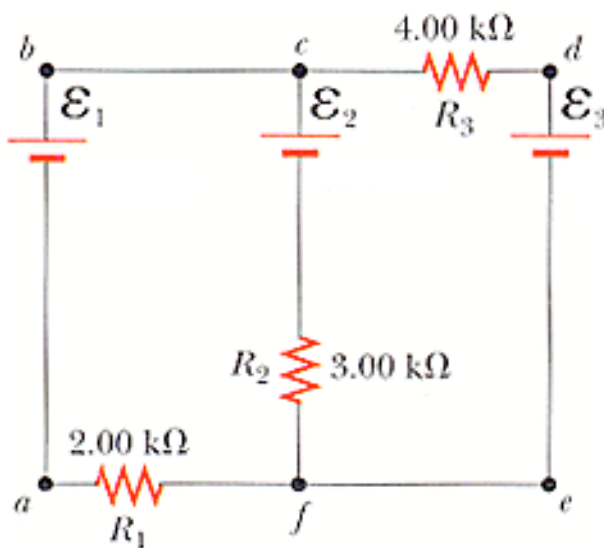- a. 4 V.
- b. 12 V.
- c. 8 V.
- d. 2 V.
- e. 16 V.




4. Two resistors have the same power dissipated by them. The potential difference measured across resistor A is twice that across resistor B . If the resistance of resistor B is R , what is the resistance of A ?

- a. $R/2$.
- b. $2R$.
- c. $R/4$.
- d. $4R$.
- e. $16R$.


5. In the circuit below, what is the power dissipated in the $12\ \Omega$ resistor?

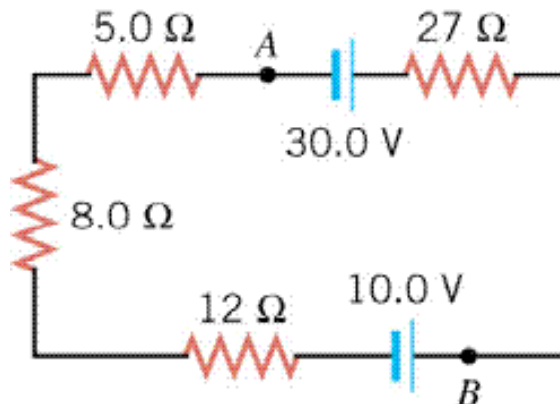- a. 1.78 W.
- b. 0.38 W.
- c. 4.62 W.
- d. 7.10 W.
- e. 0.77 W.




6. If $R_1 = R_5 = R_6 = 2\ \Omega$, $R_4 = 5\ \Omega$ and $R_2 = R_3 = 6\ \Omega$, the equivalent resistor connected to the battery is:

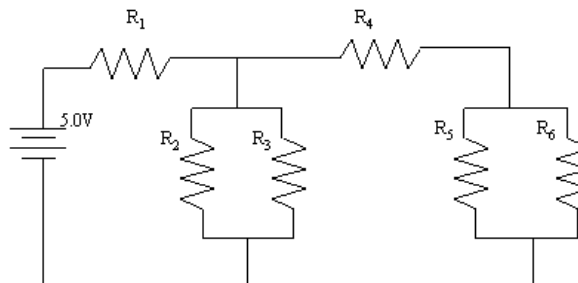- a. $4\ \Omega$
- b. $7\ \Omega$.
- c. $8\ \Omega$.
- d. $6\ \Omega$.
- e. $2\ \Omega$.



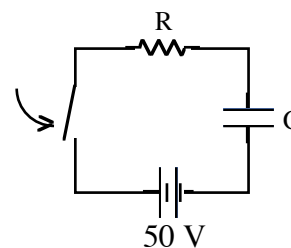
7. A series RC circuit has a time constant of 1.0 s. The battery has a voltage of 50 V and the maximum current just after closing the switch is 500 mA. The capacitor is initially uncharged. What is the charge on the capacitor 2.0 s after the switch is closed?



- a. 0.43 C
- b. 0.66 C
- c. 0.86 C
- d. 0.29 C
- e. 0.17 C

8. In the picture below, the current through the $3.0\ \Omega$ resistor is 2.0 A. What is the potential difference of the battery marked \mathcal{E} ?

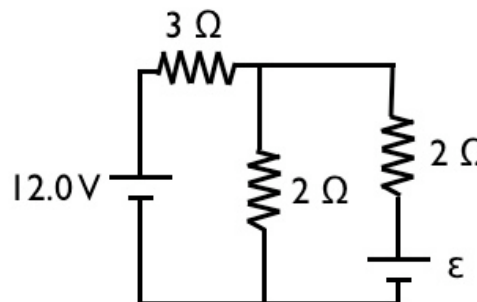- a. 2.0 V.
- b. 4.0 V.
- c. 5.0 V.
- d. 6.0 V.
- e. 8.0 V.



Recall that

$$F = k_e \frac{|q_1||q_2|}{r^2}; \quad k_e = 8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2}; \quad e = 1.60 \times 10^{-19} \text{C}; \quad \epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2};$$

$$m_e = 9.11 \times 10^{-31} \text{kg}; \quad m_p = 1.673 \times 10^{-27} \text{kg}; \quad m_n = 1.675 \times 10^{-27} \text{kg}; \quad 1 \text{eV} = 1.602 \times 10^{-19} \text{J};$$

$$1 \text{kWh} = 3.60 \times 10^6 \text{J}; \quad \vec{F} = q_o \vec{E}; \quad E = k_e \frac{|q|}{r^2}; \quad \Phi_E = EA \cos \theta; \quad \Phi_E = \frac{Q_{\text{inside}}}{\epsilon_0}; \quad PE_{\text{elec.point}} = k_e \frac{qq_0}{r};$$

$$V_{\text{point charge}} = k_e \frac{q}{r}; \quad \Delta PE_{\text{elec}} = q_o \Delta V; \quad C = \frac{Q}{\Delta V}; \quad C_{\text{parallel plate}} = \epsilon_0 \frac{A}{d}; \quad C_{\text{dielectric}} = \kappa \epsilon_0 \frac{A}{d};$$

$$\frac{1}{C_{\text{series eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots; \quad C_{\text{parallel eq}} = C_1 + C_2 + C_3 + \dots;$$

$$\text{Energy}_{\text{capacitor}} = \frac{1}{2} Q(\Delta V) = \frac{1}{2} C(\Delta V)^2 = \frac{Q^2}{2C}; \quad I = \frac{\Delta Q}{\Delta t};$$

$$R = \frac{\Delta V}{I} = \rho \frac{L}{A}; \quad \rho = \rho_o [1 + \alpha(T - T_o)]; \quad R = R_o [1 + \alpha(T - T_o)]; \quad \text{Power} = I(\Delta V) = I^2 R = \frac{(\Delta V)^2}{R};$$

$$\rho_{\text{Silver}} = 1.59 \times 10^{-8} \Omega \cdot \text{m}; \quad \rho_{\text{Copper}} = 1.7 \times 10^{-8} \Omega \cdot \text{m}$$

$$I_{\text{in}} = I_{\text{out}}; \quad \frac{1}{R_{\text{parallel eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots; \quad R_{\text{series eq}} = R_1 + R_2 + R_3 + \dots; \quad \sum \Delta V_{\text{loop}} = 0;$$

$$\tau = RC; \quad q_{\text{charge}} = Q_{\text{final}} (1 - e^{-t/RC}); \quad q_{\text{discharge}} = Q_0 e^{-t/RC};$$

$$A_{\text{circle}} = \pi r^2; \quad A_{\text{cyl.side}} = 2\pi r h; \quad A_{\text{sphere}} = 4\pi r^2; \quad g = 9.80 \text{ m/s}^2; \quad x = \frac{b \pm \sqrt{b^2 - 4ac}}{2a};$$

$$100 \text{ cm} = 1 \text{ m}; \quad 1 \mu\text{F} = 1.0 \times 10^{-6} \text{F}; \quad 1 \text{ MW} = 1.0 \times 10^6 \text{W}; \quad 1,000 \text{ W} = 1 \text{ kW}; \quad 60 \text{ s} = 1 \text{ min};$$

$$60 \text{ min} = 1 \text{ hr}; \quad 2.54 \text{ cm} = 1 \text{ in}; \quad 12 \text{ in} = 1 \text{ ft}; \quad 5,280 \text{ ft} = 1 \text{ mi}; \quad 1,609 \text{ m} = 1 \text{ mi}; \quad 0.3048 \text{ m} = 1 \text{ ft}.$$