

Physics 1B Spring 2010

Quiz 2 version A

Solution

1.(e)

The electric potential in the middle by charge $+Q$ is :

$$V_+ = \frac{k(+Q)}{\left(\frac{d}{2}\right)} \quad (1)$$

For charge $-Q$, it's

$$V_- = \frac{k(-Q)}{\left(\frac{d}{2}\right)} \quad (2)$$

So the total is $V = V_+ + V_- = 0$.

2.(b)

We can solve this problem separately. Please refer to Figure 1. In this figure, $C_1 = 10\mu F$, $C_2 = 6\mu F$, $C_3 = 12\mu F$, $C_4 = 6\mu F$.

(1) Calculate C_{eq1} . C_2 and C_3 are connected in series.

$$\frac{1}{C_{eq1}} = \frac{1}{C_2} + \frac{1}{C_3} \quad (3)$$

This gives $C_{eq1} = 4\mu F$.

(2) Calculate C_{eq2} . C_{eq1} and C_4 are connected in parallel.

$$C_{eq2} = C_{eq1} + C_4 \quad (4)$$

So we get $C_{eq2} = 10\mu F$.

(3) Calculate C_{tot} . C_1 and C_{eq2} are connected in series.

$$\frac{1}{C_{tot}} = \frac{1}{C_1} + \frac{1}{C_{eq2}} \quad (5)$$

So, the entire capacitance is $C_{tot} = 5\mu F$.

3.(d)

Problem 2 and 3 have the same combination of capacitors. Please refer to Figure 1. We'll use this figure from the right to the left.

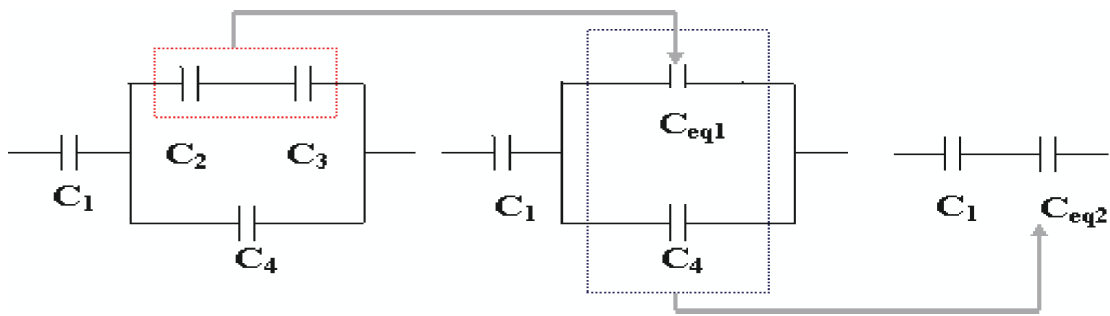


Figure 1: Problem 2 and 3.

C_1 and C_{eq2} are connected in series, thus they have the same charges.

$$\begin{aligned} \frac{U_1}{U_{eq2}} &= \frac{\frac{Q_1}{C_1}}{\frac{Q_{eq2}}{C_{eq2}}} \\ &= \frac{C_{eq2}}{C_1} \\ &= \frac{10\mu F}{10\mu F} \\ &= 1 \end{aligned}$$

$$U_1 + U_{eq2} = 18V \quad (6)$$

From these 2 equations we get $U_1 = U_{eq2} = 9V$.

As we can see, C_{eq1} and C_4 are connected in parallel. The potential difference between them is $9V$.

C_2 and C_3 are connected in series. Then $Q_2 = Q_3$.

$$\begin{aligned} \frac{U_2}{U_3} &= \frac{\frac{Q_2}{C_2}}{\frac{Q_3}{C_3}} \\ &= \frac{C_3}{C_2} \\ &= \frac{12\mu F}{6\mu F} \\ &= 2 \end{aligned}$$

$$U_2 + U_3 = 9V \quad (7)$$

We get $U_2=6V$, $U_3=3V$.

The charge in C_3 is given by $Q_3 = C_3 U_3 = 12 \times 10^{-6} F \times 3V = 36 \times 10^{-6} C = 36\mu C$.

4.(b)

These 2 capacitors are connected in series, and it means $Q_1 = Q_2$. Here $C_1 = 3.0\mu F$, $C_2 = 6.0\mu F$.

$$\begin{aligned}\frac{U_1}{U_2} &= \frac{\frac{Q_1}{C_1}}{\frac{Q_2}{C_2}} \\ &= \frac{C_2}{C_1} \\ &= \frac{6\mu F}{3\mu F} \\ &= 2 \\ U_1 + U_2 &= 90V\end{aligned}\tag{8}$$

We can get $U_1 = 60V$, $U_2 = 30V$. So,

$$\begin{aligned}\text{Energy stored} &= \frac{1}{2}C\Delta V^2 \\ &= \frac{1}{2} \times 3 \times 10^{-6} F \times 60^2 V^2 \\ &= 5.4 \times 10^{-3} J\end{aligned}\tag{9}$$

5.(e)

The capacitance of a parallel-plate capacitor is

$$\begin{aligned}C &= \epsilon_0 \frac{A}{d} \\ &= 8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2} \times \frac{(20 \times 10^{-2} m)^2}{1.0 \times 10^{-2} m} \\ &= 3.54 \times 10^{-11} F\end{aligned}\tag{10}$$

$$\begin{aligned}\text{Energy stored} &= \frac{1}{2}C\Delta V^2 \\ &= \frac{1}{2} \times 3.54 \times 10^{-11} F \times 50^2 V^2 \\ &= 4.4 \times 10^{-8} J\end{aligned}\tag{11}$$

6.(c)

The electric potential energy is converted into electron's kinetic energy. $|\Delta PE| = \frac{1}{2}m_e v_{final}^2 - \frac{1}{2}m_e v_0^2$. Here v_0 is 0 since electron is initially at rest. The change of PE is $|\Delta PE| = eU$. From

these 2 equations, the v_{final} is expressed as

$$\begin{aligned}v_{final} &= \sqrt{\frac{2eU}{m_e}} \\ &= \sqrt{\frac{2 \times 1.6 \times 10^{-19}C \times 4800V}{9.11 \times 10^{-31}kg}} \\ &= 4.2 \times 10^7 m/s\end{aligned}\tag{12}$$

7.(d)

The $+q$ charge creates a potential $V_1 = \frac{k(+q)}{d}$. The $+2q$ charge creates a potential $V_2 = \frac{k(+2q)}{\sqrt{2}d}$. The $+5q$ charge creates a potential $V_5 = \frac{k(+5q)}{d}$. The total potential at site of $-3q$ is $V_1 + V_2 + V_5$,

$$\begin{aligned}V_1 + V_2 + V_5 &= \frac{k(+q)}{d} + \frac{k(+2q)}{\sqrt{2}d} + \frac{k(+5q)}{d} \\ &= \frac{kq}{d}(1 + \sqrt{2} + 5) \\ &= \frac{899 \times 10^9 \frac{N \cdot m^2}{C^2} \times 10 \times 10^{-9}C}{2m} \times 7.414 \\ &= 333V\end{aligned}\tag{13}$$

8.(a)

These 2 capacitors are connected in parallel. They have the same potential difference. This gives $U_1 = U_2$. Here $C_1 = 2.0\mu F$, $C_2 = 1.0\mu F$.

$$\frac{Q_1}{Q_2} = \frac{C_1 U_1}{C_2 U_2} = \frac{C_1}{C_2} = \frac{2.0\mu F}{1.0\mu F} = 2\tag{14}$$