Physics 2B

Lecture 27A

"Success is the ability to go from one failure to another with no loss of enthusiasm." --Winston Churchill

Capacitors are usually used in circuits.

- A circuit is a collection of objects usually containing a source of electrical energy (like a battery).
- This energy source is connected to elements (like capacitors) that convert the electrical energy to other forms.
- We usually create a circuit diagram to represent all of the elements at work in the real circuit.

For example, let's say that we had two capacitors connected in parallel to a battery.

- In the circuit diagram we would represent a capacitor with a parallel line symbol: ||
- Also, in the circuit diagram we would represent a battery with a short line and a long line: 1
- The short line representing the negative terminal and the long line representing the positive terminal.



The previous real circuit can then be drawn as a circuit diagram as follows:
In this circuit, both capacitors would have the same potential difference as the battery.

 $\Delta V_{\text{bat}} = \Delta V_1 = \Delta V_2$

 $Q_{Tot} = Q_1 + Q_2$

Plus, we can say that the charges on either plate are equal to the total that passes through the battery.

0



We can essentially replace the two capacitors in parallel with one equivalent capacitor (this may make our life easier).

The equivalent capacitor must have exactly the same external effect on the circuit as the original capacitors.

The battery sees Q_{Tot} passing through it and believes that the one equivalent capacitor has a potential difference of ΔV .





We can also have two capacitors hooked up in series to a battery.

In this case the potential difference across the battery is no longer equivalent to the potential difference across either capacitor.



The charge on either capacitor must be the same.

ne

This means that the charge passing through the battery is equivalent to the charge on either capacitor.

Q_{Tot} = Q₁ = Q₂
 Also, the potential difference across either capacitor will sum to be the potential difference across the battery.

$$\Delta V_{bat} = \Delta V_1 + \Delta V_2$$

We can essentially replace the two capacitors in series with

one equivalent capacitor.

0

6



The battery sees Q_{Tot} passing through it and believes that the one equivalent capacitor has a potential difference of ΔV_{bat} .

So, to the battery the equivalent capacitance is:



Remember when you have multiple capacitors in a circuit that:

- Capacitors in parallel all have the same potential differences.
- The equivalent capacitance of the parallel capacitors also will have the same potential difference.
- Capacitors in series all have the same charge.
- The equivalent capacitor of the series capacitors also will have the same charge.

Capacitance

Find the equivalent capacitance between points a and b in the group of capacitors connected in series as shown in the figure to the right (take C₁=5.00µF, C₂=10.0µF, and C₃=2.00µF). If the potential between points a and b is 60.0V, what is the charge stored on C₃?



Answer

- Reduce the circuit by equivalent capacitance to find Q₃.
- The Start with the C_1 and C_2 in series on the top.



$$Capacitance$$
• Answer
• Next, combine the bottom two that are in parallel:

$$C_{P2} = C_2 + C_2$$

$$C_{P2} = 10.0 \,\mu\text{F} + 10.0 \,\mu\text{F} = 20.0 \,\mu\text{F}$$
• Finally, combine the remaining two
capacitors that are in series:

$$\frac{1}{C_{eq}} = \frac{1}{C_{P1}} + \frac{1}{C_{P2}} = \frac{1}{8.66 \,\mu\text{F}} + \frac{1}{20 \,\mu\text{F}}$$

$$\frac{1}{C_{eq}} = (0.1155) \,\frac{1}{\mu} + (0.0500) \,\frac{1}{\mu} = (0.1655) \,\frac{1}{\mu} + \frac{1}{b} = \frac{1}{b}$$

Capacitance

<u>Answer</u>
 Next, we need to find the total charge stored on the equivalent capacitor:

$$Q_{eq} = C_{eq}(\Delta V_{ab})$$

 ΔV_{P1}

$$Q_{eq} = 6.04 \,\mu \text{F}(60\text{V}) = 362 \,\mu \text{C}$$

Looking back at the two equivalent capacitors in series (C_{p1} and C_{p2}), we see that they must have the same amount of charge:

$$Q_{eq} = Q_{P1} = Q_{P2} = 362 \mu C$$

This means that they potential difference across C_{p1} is:

$$\Delta V_{P1} = \frac{362\,\mu\text{C}}{8.66\,\mu\text{F}} = 41.8\,\text{V}$$

 C_{n1}

 C_{p2}

Capacitanc<u>e</u>

Answer
We turn back to the three top capacitors in parallel (C_S, C₃, and C_S).
We note that all three of these capacitors must have the same potential difference as each other (and C_{p1}).

$$\Delta V_{C3} = 41.8 \mathrm{V}$$

This means that the charge on
 C₃ is:

$$Q_3 = C_3 \left(\Delta V_{C3} \right)$$

$$Q_3 = 2.00 \,\mu \text{F}(41.8\text{V}) = 83.6 \,\mu \text{C}$$



- The problem with capacitors is that they need to have huge dimensions to carry a significant amount of charge.
- Cost of material and manufacturing become a problem.
- The solution is to substitute an electrically insulating material between the parallel-plates instead of air or a vacuum.
- This is known as a dielectric.
- When inserted into the capacitor the dielectric will increase the overall capacitance.

The dielectric constant, κ, is the ratio of the new capacitance to the capacitance in a vacuum:



(b)

Dielectric



Capacitance C_0 in vacuum

Capacitance $C > C_0$

Easily polarized materials have larger dielectric constants than materials not easily polarized.



- Filling a capacitor with a dielectric increases the capacitance by a factor equal to the dielectric constant.
- The capacitance for a parallel-plate capacitor changes to:

$$C = \kappa \varepsilon_o \frac{A}{d}$$

- Common dielectric values:
- \oslash K_{vacuum} = 1
- $\odot K_{air} = 1.0006$
- \odot K_{glass} \approx 7

Note that the dielectric constant is a unitless variable.

For Next Time (FNT)

Start reading Chapter 27

Keep working on the homework for Chapter 26