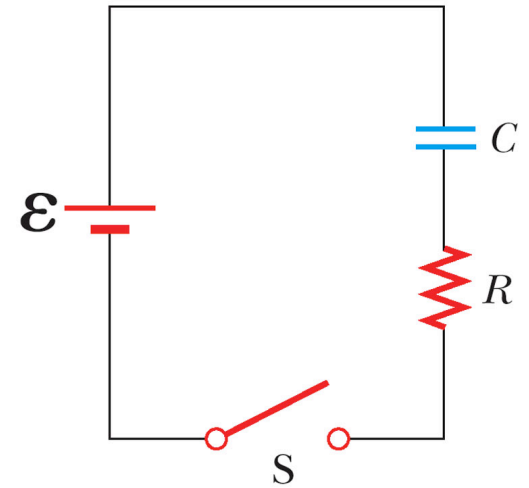


18.5 RC Circuits

Introduction to time-dependent currents and voltages.

Applications: timing circuits, clocks, computers, charging + discharging capacitors


An RC circuit



© 2006 Brooks/Cole - Thomson

RC circuit: charging

At time $t=0$, close Switch

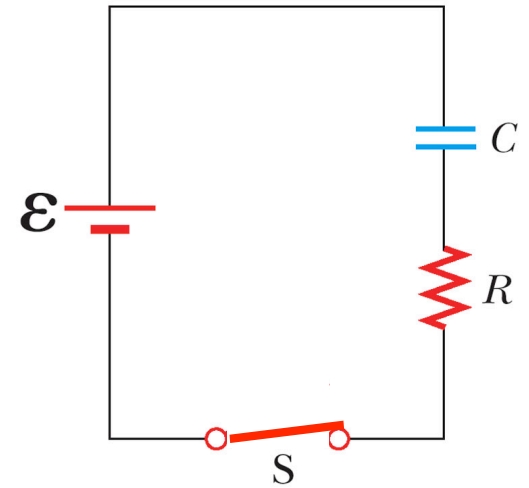

© 2006 Brooks/Cole - Thomson

An RC circuit

At time $t=0$, close switch

Initially (at $t=0$), $Q = 0$.

$$\Delta V_C \text{ (at } t=0) = Q(t=0) / C = 0$$


$$\text{Loop Rule: } \Sigma \Delta V = 0 = +\varepsilon - \Delta V_R - \Delta V_C$$

$$+\varepsilon - IR - \Delta V_C = 0$$

So when charge = 0 (which occurs at $t=0$),

$$\varepsilon = IR \text{ and so } I = \varepsilon / R$$

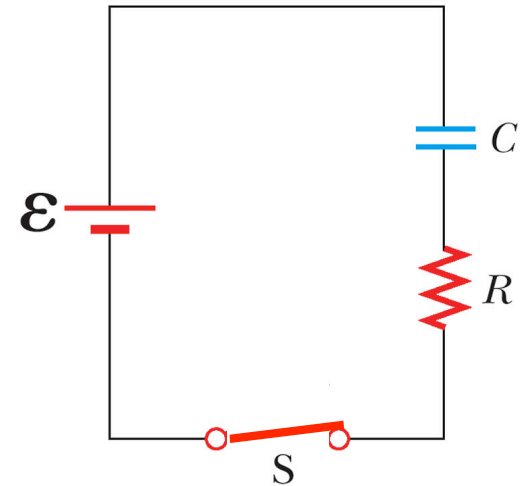(at this instant, capacitor has no effect)



© 2006 Brooks/Cole - Thomson

RC circuit: charging


Immediately after time $t=0$: Current starts to flow. Charge starts to accumulate on Capacitor (at a rate $I=dQ/dt$).

As Q increases over time, $\Delta V_C = Q/C$ also increases.

But remember $\Delta V_C + \Delta V_R = \mathcal{E}$.

So ΔV_R is decreasing over time.

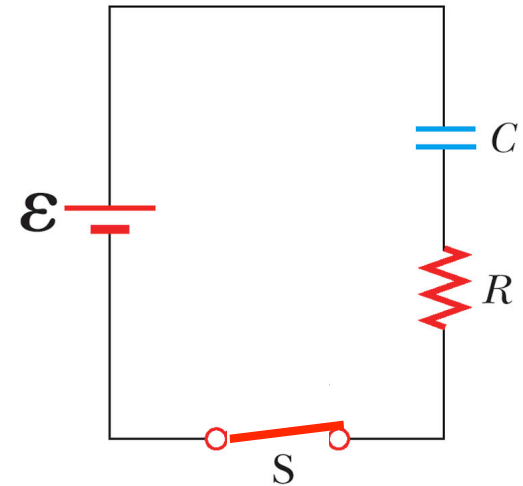And I through the resistor $= \Delta V_R/R$ is also decreasing.



© 2006 Brooks/Cole - Thomson

RC circuit: charging


After a very long time:

Charge accumulates until Q reaches its maximum:

ΔV_C goes to ε . Total Q on the capacitor goes to $C\varepsilon$.



$$+\varepsilon = \Delta V_C + \Delta V_R$$

ΔV_R goes to zero. And I goes to zero.

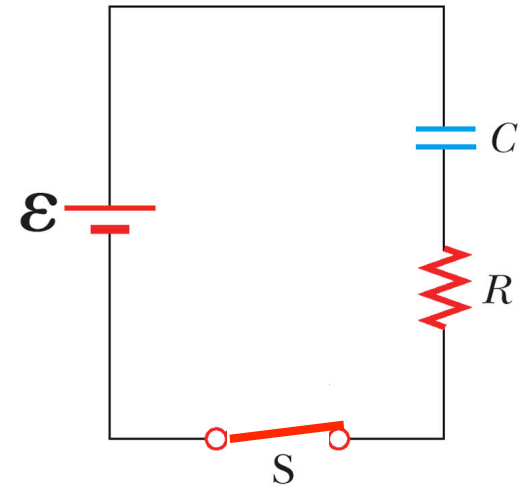

© 2006 Brooks/Cole - Thomson

RC circuit: charging

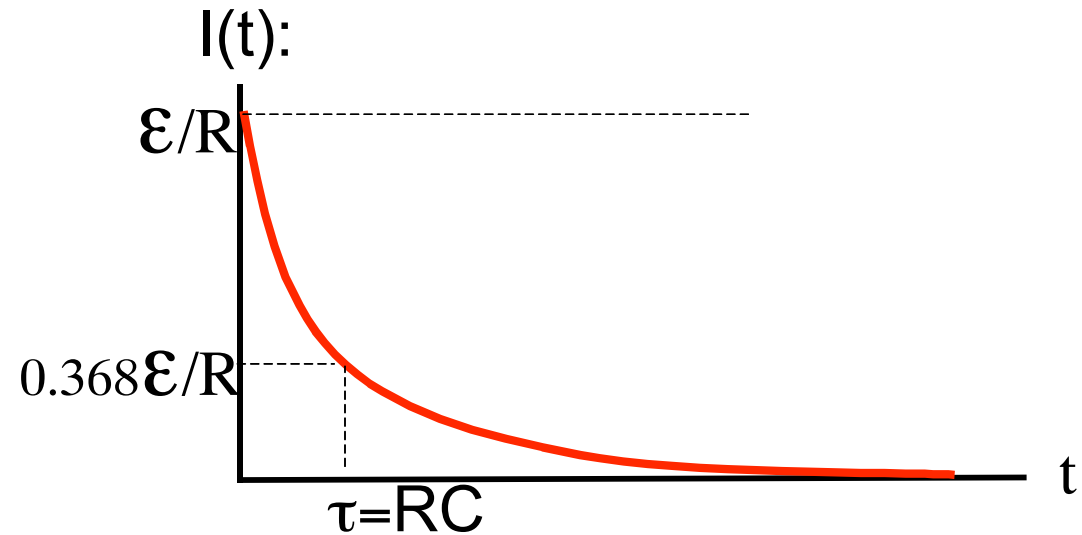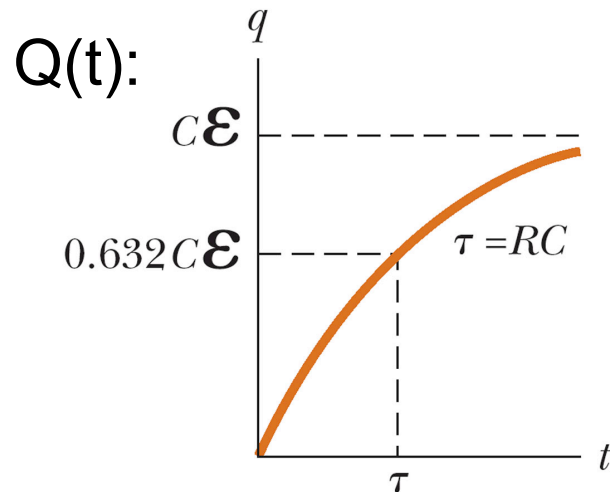

© 2008 Brooks/Cole - Thomson

$t=0$

$t \rightarrow \infty$

	$t=0$		$t \rightarrow \infty$
ΔV_C	0	$\epsilon(1-e^{-(t/\tau)})$	ϵ
Q	0	$C\epsilon(1-e^{-(t/\tau)})$	$C\epsilon$
ΔV_R	ϵ	$\epsilon(e^{-(t/\tau)})$	0
I	ϵ/R	$(\epsilon/R)(e^{-(t/\tau)})$	0

Exponential decay

Rate of decay is proportional to amount of species.

Other applications: Nuclear decay, some chemical reactions

Atmospheric pressure decreases exponentially with height

If an object of one temperature is exposed to a medium of another temperature, then the temperature difference between the object and the medium undergoes exponential decay.

Absorption of electromagnetic radiation by a medium (intensity decreases exponentially with distance into medium)



Time constant $\tau = RC$

RC is called the time constant: it's a measure of how fast the capacitor is charged up.

It has units of time:

$$RC = (V/I)(q/V) = q/I = q / (q/t) = t$$

At $t = RC$, $Q(t)$ and $\Delta V_C(t)$ go to $1 - 1/e = 0.63$ of the final values

At $t = RC$, $I(t)$ and $\Delta V_R(t)$ go to $1/e$ of the initial values

Time constant $\tau = RC$


Think about why increasing R and/or C would increase the time to charge up the capacitor:

When charging up: τ will increase with C because the capacitor can store more charge.


Increases with R because the flow of current is lower.

Time constant $\tau = RC$

RC: charging

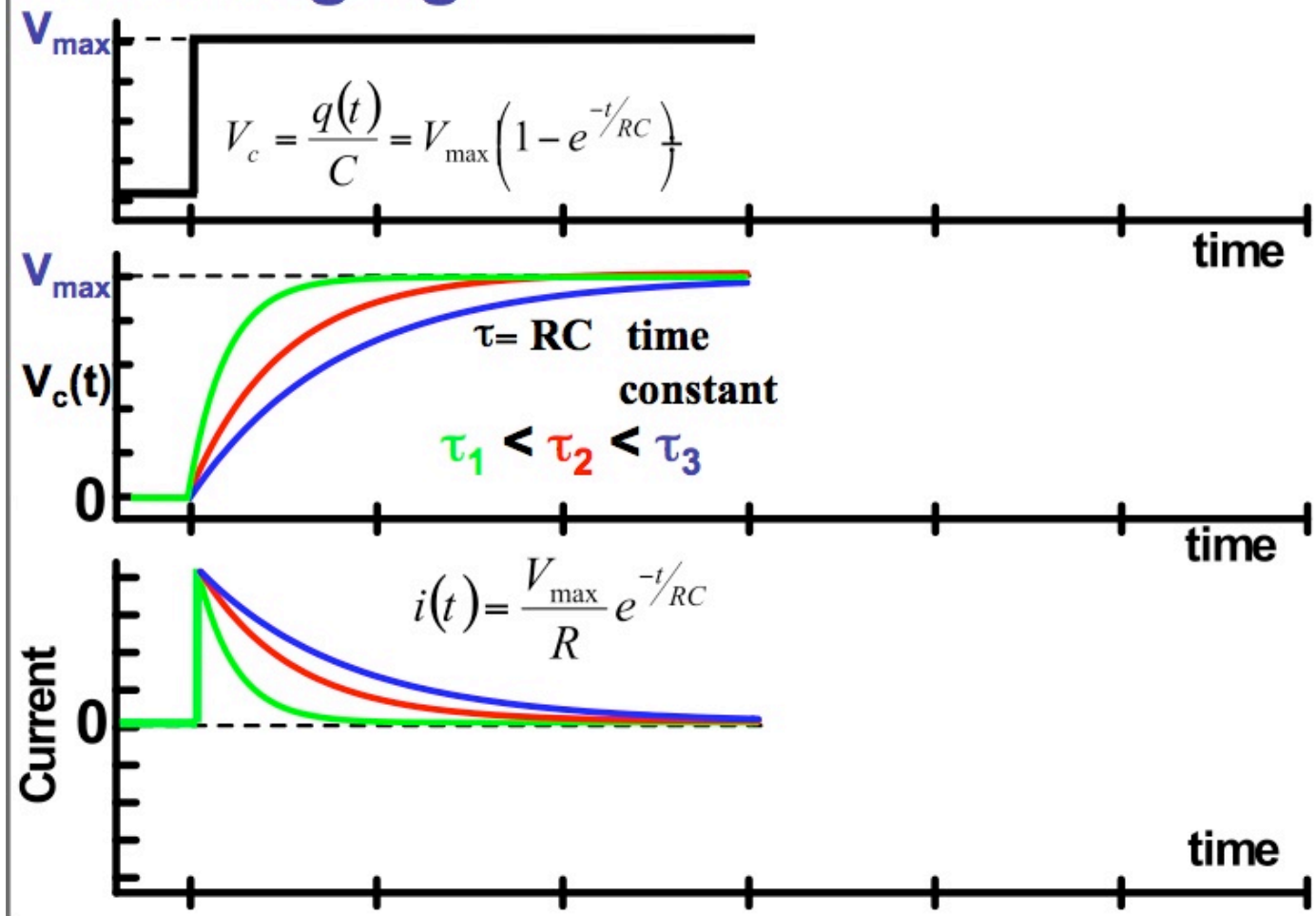

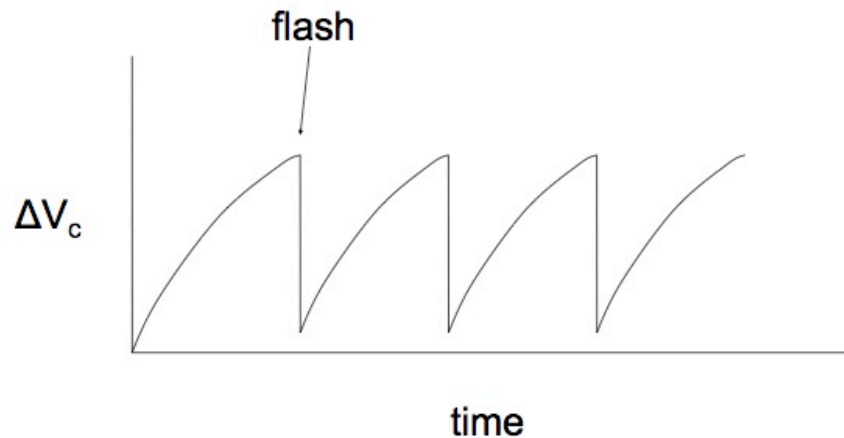You want to make a so-called flasher circuit that charges a capacitor through a resistor up to a voltage at which a neon bulb discharges once every 5.0 sec. If you have a 10 microfarad capacitor what resistor do you need?




Solution: Have the flash point be equal to $0.63 \Delta V_{C,\max}$

$$\tau = RC \rightarrow R = \tau/C = 5\text{s}/10^{-6}\text{F} = 5 \times 10^5 \text{ Ohms}$$

This is a very big resistance, but 5 seconds is pretty long in "circuit" time

Discharging an RC circuit:

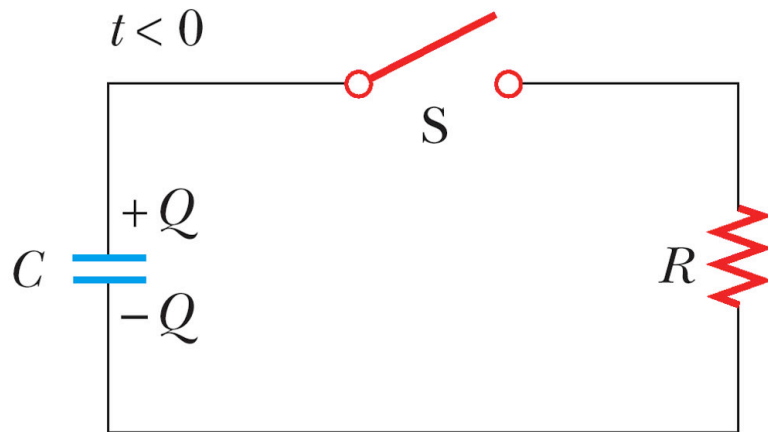


First, disconnect
from EMF source.

Q is at maximum value, $Q_{\max} = C\varepsilon$

ΔV_C is at maximum value of $\Delta V_{C,\max} = \varepsilon$


Discharging an RC circuit:

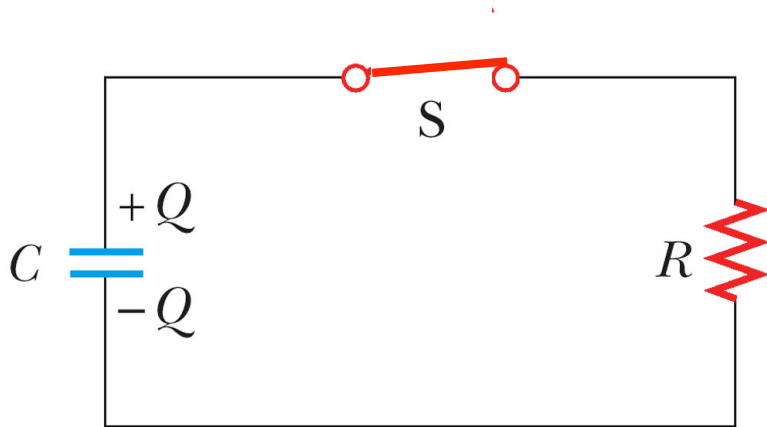

Then close switch
at time $t=0$.

Discharging an RC circuit:

Circuit now has only R and C.

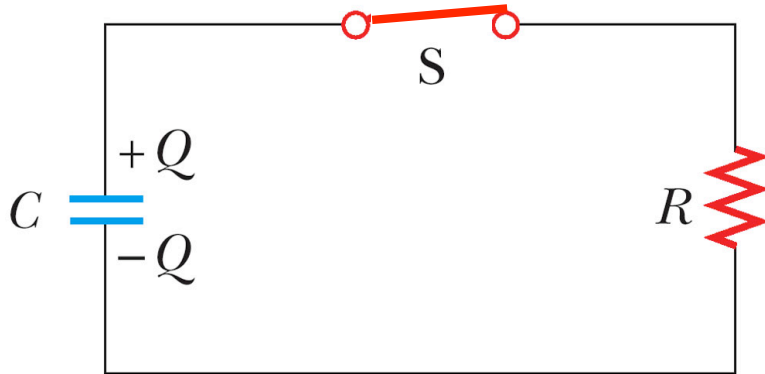


© 2006 Brooks/Cole - Thomson

From loop rule: $-\Delta V_C - \Delta V_R = 0$


As capacitor discharges, Q and ΔV_C decrease with time.

ΔV_R will track ΔV_C

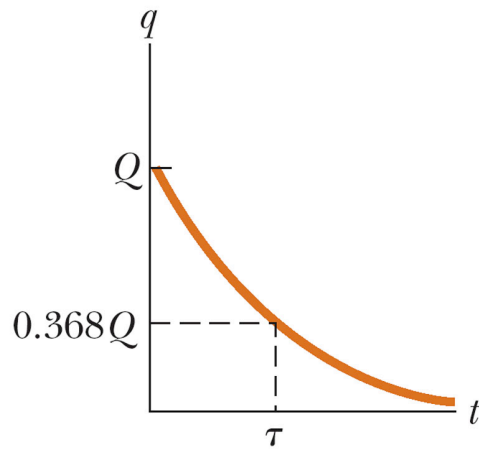So $I = \Delta V_R / R$ will jump from 0 to ε / R at $t=0$, then exponentially decay



© 2008 Brooks/Cole - Thomson

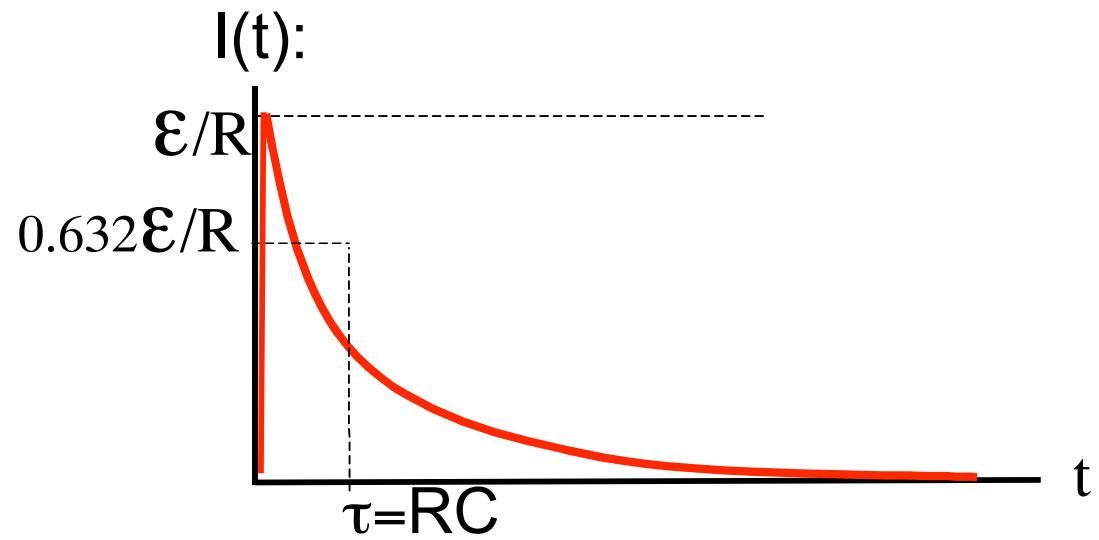

	$t=0$		$t \rightarrow \infty$
ΔV_C	ϵ	$\epsilon(e^{-(t/\tau)})$	0
Q	$Q_{\max} = C\epsilon$	$C\epsilon(e^{-(t/\tau)})$	0
ΔV_R	ϵ	$\epsilon(e^{-(t/\tau)})$	0
I	ϵ/R	$\epsilon/R(e^{-(t/\tau)})$	0

Think about why increasing R and/or C would increase the time to discharge the capacitor:

τ will increase with C because there is more stored charge in the capacitor to unload. τ increases with R because the flow of current is lower.

Given a 12 μF capacitor being discharged through a 2000 Ω resistor. How long does it take for the voltage drop across the resistor to reach 5% of the initial voltage?

Solution:

First, calculate τ : $\tau = 2000\Omega * 12 \times 10^{-6} \text{ F} = 24 \text{ ms}$

Then: $V = V_0 \exp(-t/\tau)$

$V / V_0 = \exp(-t/\tau)$

Take ln of both sides: $\ln(V/V_0) = -t/\tau$

Solve for t: $t = -\tau * \ln(V/V_0) = -0.024 \text{ s} (\ln(0.05)) = 0.072 \text{ sec}$