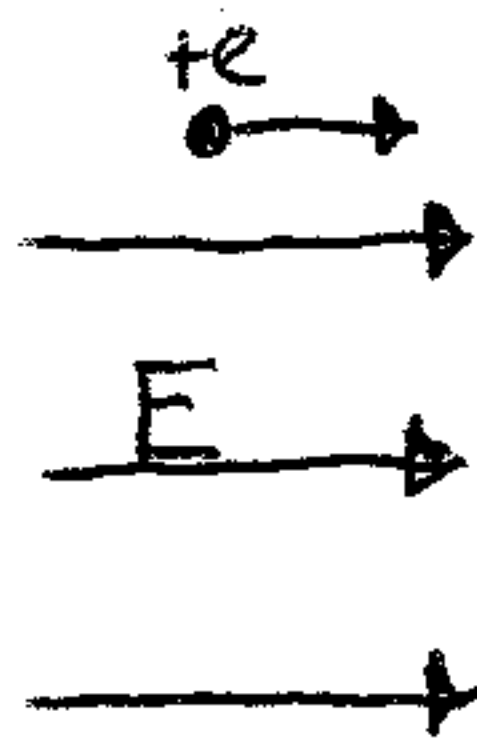
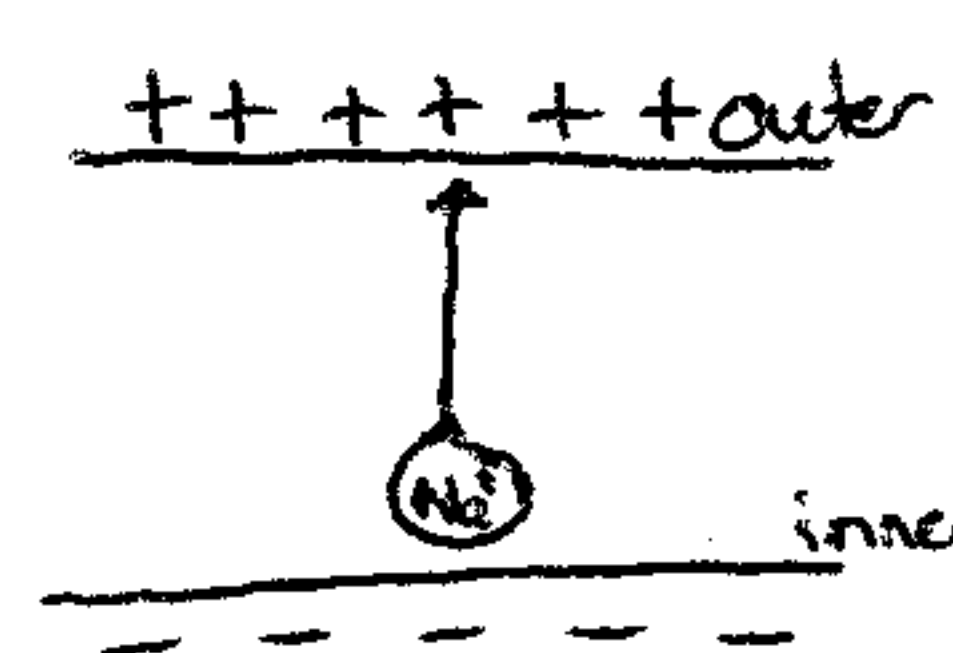


1 a)   $E = 200 \text{ N/C}$   
 $q = 1.602 \cdot 10^{-19} \text{ C}$   
 $\Delta x = 2.00 \text{ cm} = 2 \cdot 10^{-2} \text{ m}$  }  $W = qE\Delta x = 6.41 \cdot 10^{-19} \text{ J}$

b)  $W = -\Delta PE \Rightarrow \Delta PE = -6.41 \cdot 10^{-19} \text{ J}$

c)  $\Delta V = \Delta PE / q = -4.00 \text{ V}$

note: An electron would ~~lose~~ <sup>lose</sup> 4 V if it did the same motion. The proton loses potential energy going along the electric field lines, therefore  $\Delta PE$  is negative and  $\Delta V$  is positive. Hence  $\Delta V$  is negative. The electron would gain potential energy but  $q$  is negative; hence  $\Delta V$  is still negative.

3)   $\Delta PE = -W$   
 $\Delta PE = q\Delta V$  }  $W = -q\Delta V$

$q = 1.602 \cdot 10^{-19} \text{ C}$   
 $\Delta V = -90 \text{ mV}$  }  $1.4 \cdot 10^{-20} \text{ J}$

note:  $q = 1.602 \cdot 10^{-19} \text{ C}$ , because the net charge of a sodium ion is  $+1e$ .

$\Delta V$  is negative, because the ion moves from negative to positive, against the field lines.



$$\begin{aligned}
 6) \quad W &= -q \Delta V \\
 q &= 3.6 \cdot 10^5 \text{ C} \\
 \Delta V &= -12 \text{ V}
 \end{aligned}
 \left. \vphantom{\begin{aligned} W &= -q \Delta V \\ q &= 3.6 \cdot 10^5 \text{ C} \\ \Delta V &= -12 \text{ V} \end{aligned}} \right\} \begin{aligned} W &= 4.3 \cdot 10^6 \text{ J} \\ \text{see problem 3 for why } \Delta V &\text{ is negative} \end{aligned}$$

$$\begin{aligned}
 8a) \quad W &= -q \Delta V \\
 q &= 1.602 \cdot 10^{-19} \text{ C} \\
 \Delta V &= 120 \text{ V}
 \end{aligned}
 \left. \vphantom{\begin{aligned} W &= -q \Delta V \\ q &= 1.602 \cdot 10^{-19} \text{ C} \\ \Delta V &= 120 \text{ V} \end{aligned}} \right\} \begin{aligned} W &= 1.92 \cdot 10^{-17} \text{ J} \end{aligned}$$

By the work/energy theorem  
 $W = -\Delta KE$  Hence

$$\Delta KE = 1.92 \cdot 10^{-17} \text{ J} \quad \Delta KE = \frac{1}{2} m v_f^2 - \frac{1}{2} m v_0^2 \text{ but } v_0 = 0 \text{ thus}$$

$$\begin{aligned}
 m &= 1.607 \cdot 10^{-27} \text{ kg} \\
 \Delta KE &= 1.92 \cdot 10^{-17} \text{ J}
 \end{aligned}
 \left. \vphantom{\begin{aligned} m &= 1.607 \cdot 10^{-27} \text{ kg} \\ \Delta KE &= 1.92 \cdot 10^{-17} \text{ J} \end{aligned}} \right\} \begin{aligned} \Delta KE &= \frac{1}{2} m v_f^2 \\ v_f &= \sqrt{\frac{2 \Delta KE}{m}} = 1.52 \cdot 10^5 \text{ m/s} \end{aligned}$$

b) to be precise, the electron will accelerate in the opposite direction and  $\Delta V$  should be  $-120 \text{ V}$ , but this is still considered a difference of  $120 \text{ V}$ .

$q$  and  $\Delta V$  are equal and thus  $\Delta KE$  stays the same:  $\Delta KE = 1.92 \cdot 10^{-17} \text{ J}$

The only thing that changes is  $m$   $m = 9.1 \cdot 10^{-31} \text{ kg}$  Hence


$$v_f = \sqrt{\frac{2 \Delta KE}{m}} = 6.49 \cdot 10^6 \text{ m/s}$$

$$5) \quad \Delta V = -E \Delta x$$

$$\begin{aligned}
 \Delta V &= 2.5 \cdot 10^4 \text{ V} \\
 \Delta x &= 1.5 \cdot 10^{-2} \text{ m}
 \end{aligned}
 \left. \vphantom{\begin{aligned} \Delta V &= 2.5 \cdot 10^4 \text{ V} \\ \Delta x &= 1.5 \cdot 10^{-2} \text{ m} \end{aligned}} \right\} E = \frac{-\Delta V}{\Delta x} = -1.67 \cdot 10^6 \text{ V/m} \text{ since we only need the magnitude:}$$

$$|E| = 1.7 \cdot 10^6 \text{ V/m} = 1.7 \cdot 10^6 \text{ N/C} \text{ (note the two units are the same).}$$



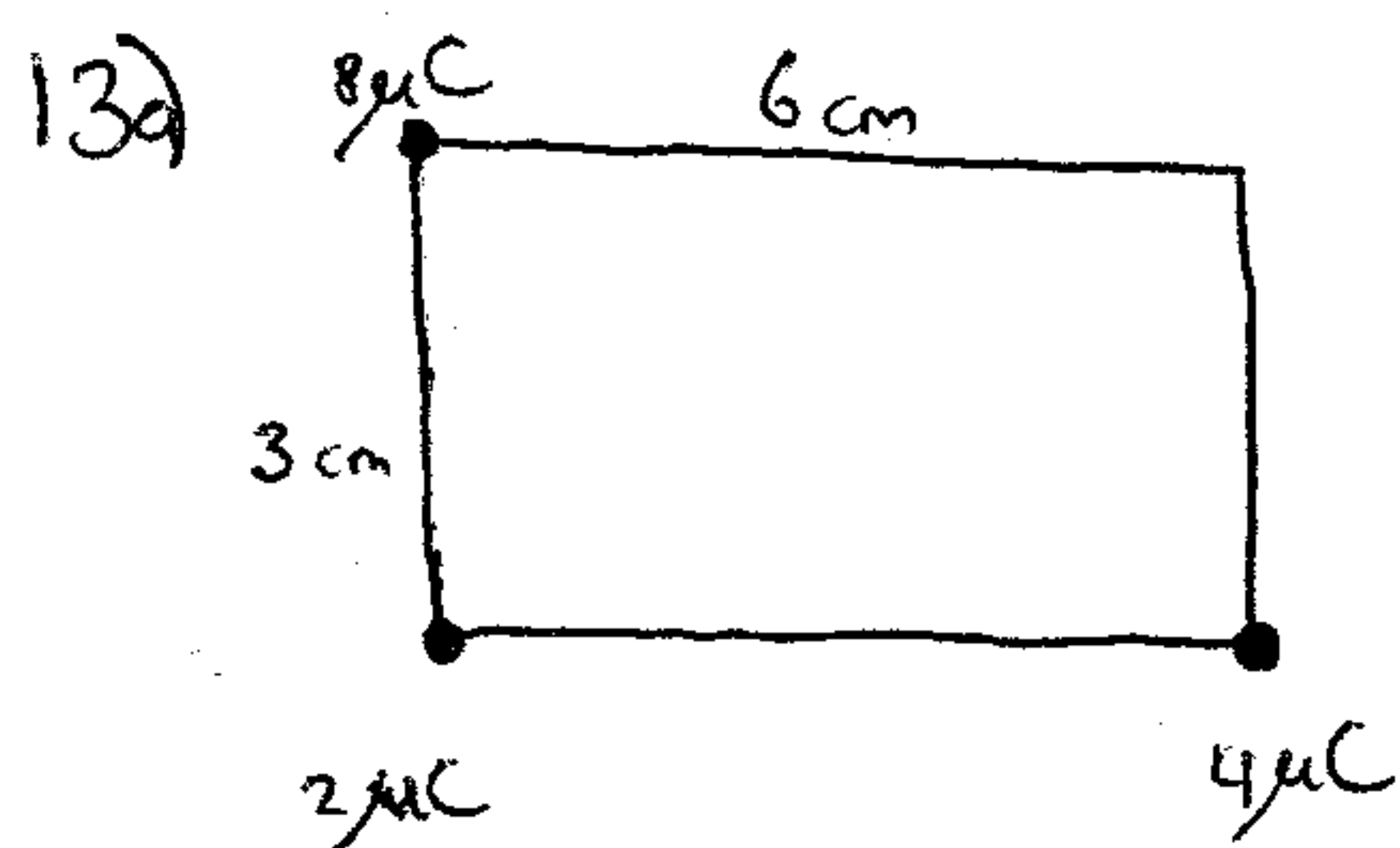

$V_p = k_e \frac{q}{r}$  since  $V$  is a scalar, the three individual voltages can just be added:

$$\begin{aligned} V_1: q_1 = 8 \cdot 10^{-6} \text{C} \quad r = 0.06 \text{m} \quad \left. \vphantom{\begin{matrix} V_1 \\ q_1 \\ r \end{matrix}} \right\} V_1 = 1.20 \cdot 10^6 \text{V} & \quad V_2: q_2 = 4 \cdot 10^{-6} \text{C} \quad r = 0.03 \text{m} \quad \left. \vphantom{\begin{matrix} V_2 \\ q_2 \\ r \end{matrix}} \right\} V_2 = 1.20 \cdot 10^6 \text{V} & \quad V_3: q_3 = 2 \cdot 10^{-6} \text{C} \quad r = \sqrt{3^2 + 6^2} = 0.0671 \text{m} \quad \left. \vphantom{\begin{matrix} V_3 \\ q_3 \\ r \end{matrix}} \right\} V_3 = 2.68 \cdot 10^5 \text{V} \end{aligned}$$

$$V = V_1 + V_2 + V_3 = 2.67 \cdot 10^6 \text{V}$$

b) If  $2\mu\text{C}$  is replaced with  $-2\mu\text{C}$  then  $V_3 = -2.68 \cdot 10^5 \text{V}$  Hence

$$V = V_1 + V_2 + V_3 = 1.20 \cdot 10^6 \text{V} + 1.20 \cdot 10^6 \text{V} + (-2.68 \cdot 10^5 \text{V}) = 2.13 \cdot 10^6 \text{V}$$



Halfway in between,  $r = 17.5\text{cm}$ . Hence,

$$\begin{aligned} V_1 = k_e \frac{q}{r} & \quad V_2 = k_e \frac{q}{r} \\ q = 5 \cdot 10^{-9} \text{C} & \quad q = -3 \cdot 10^{-9} \text{C} \\ r = 0.175 \text{m} & \quad r = 0.175 \text{m} \end{aligned} \quad \left. \vphantom{\begin{matrix} V_1 \\ q \\ r \end{matrix}} \right\} V_1 = 257 \text{V} \quad \left. \vphantom{\begin{matrix} V_2 \\ q \\ r \end{matrix}} \right\} V_2 = -154 \text{V}$$

$$V = V_1 + V_2 = 257 + (-154) = 103 \text{V}.$$

b)

$$\begin{aligned} \Delta PE &= k_e \frac{q_1 q_2}{r} \\ q_1 &= 5 \cdot 10^{-9} \text{C} \\ q_2 &= -3 \cdot 10^{-9} \text{C} \\ r &= 0.35 \text{m} \end{aligned} \quad \left. \vphantom{\begin{matrix} \Delta PE \\ q_1 \\ q_2 \\ r \end{matrix}} \right\} \Delta PE = -3.85 \cdot 10^{-7} \text{J}$$

Since  $PE$  is  $-$   $W = -\Delta PE$  is positive. Hence, work needs to be done to separate the two charges. If the charges had the same sign, then no work needs to be done (the two charges would repel).



$$16) \quad \left. \begin{array}{l} V = k_e q/r \quad k_e = 8.99 \cdot 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2 \\ q = 9 \cdot 10^{-9} \text{ C} \quad r = 0.3 \text{ m} \end{array} \right\} V = 270 \text{ V}$$

The voltage at  $x=30\text{cm}$  from the origin due to the charge there is  $270\text{V}$   
at infinity the voltage is  $0\text{V}$ . Therefore:

$$\Delta PE = -W \Rightarrow W = -q(V_{30\text{cm}} - V_{\infty}) =$$

$$\left. \begin{array}{l} q = 9 \cdot 10^{-9} \text{ C} \\ V_{30\text{cm}} = 270 \text{ V} \end{array} \right\} W = 9 \cdot 10^{-9} \text{ C} \cdot (270 - 0) = 2.43 \cdot 10^{-6} \text{ J}$$

The work is positive, you need to do work to bring two positive charges together because they repel each other.

$$21) \quad V = k_e q/r \quad r = k_e q/V$$

$$\left. \begin{array}{l} q = 8 \cdot 10^{-9} \text{ C} \\ V = 100 \text{ V} \end{array} \right\} r = 0.719 \text{ m} \quad \text{similarly for } V=50 \text{ V } r=1.44 \text{ m} \quad V=25 \text{ V } r=2.88 \text{ m}$$

In a table:

| $V(\text{V})$ | $r(\text{m})$ |
|---------------|---------------|
| 100           | 0.719 m       |
| 50            | 1.44 m        |
| 25            | 2.88 m        |

Clearly when  $V$  halves,  $r$  doubles,  $V$  and  $r$  are inversely proportional  
as can be seen from the equation  $r = k_e q/V$ .



$$22a) \left. \begin{array}{l} C = Q/\Delta V \\ \Delta V = 12.0V \\ C = 4.00 \mu F \end{array} \right\} Q = C\Delta V = 4.80 \cdot 10^{-5} C$$

$$b) \text{ Now } \Delta V = 1.50V \Rightarrow Q = C\Delta V = 6.00 \cdot 10^{-6} C$$

$$23a) \left. \begin{array}{l} C = \epsilon_0 A/d \\ A = 1 \cdot 10^6 m^2 \\ d = 800 m \\ \epsilon_0 = 8.85 \cdot 10^{-12} C^2/N \cdot m^2 \end{array} \right\} C = 1.1 \cdot 10^{-8} F$$

$$b) \text{ First find } \Delta V \text{ from } \Delta V = E \cdot \Delta x$$

$$\left. \begin{array}{l} E = 3 \cdot 10^6 N/C \\ \Delta x = 800 m \end{array} \right\} \Delta V = 2.4 \cdot 10^9 V \text{ therefore}$$

$$C = Q/\Delta V \Rightarrow Q = C\Delta V$$

$$\left. \begin{array}{l} C = 1.1 \cdot 10^{-8} F \\ \Delta V = 2.4 \cdot 10^9 V \end{array} \right\} Q = 26 C$$

$$25a) \left. \begin{array}{l} \Delta V = -E \cdot \Delta x \\ \Delta V = 20.0V \\ \Delta x = 1.80 \cdot 10^{-3} m \end{array} \right\} E = \frac{-\Delta V}{\Delta x} = 1.11 \cdot 10^4 V/m \text{ E always points from positive to negative}$$

$$b) \left. \begin{array}{l} C = \epsilon_0 A/d \\ A = 7.6 \cdot 10^{-4} m^2 \\ d = 1.8 \cdot 10^{-3} m \end{array} \right\} C = 3.74 \cdot 10^{-12} F$$

$$c) C = Q/\Delta V \Rightarrow Q = C\Delta V$$

$$\left. \begin{array}{l} C = 3.74 \cdot 10^{-12} F \\ \Delta V = 20.0V \end{array} \right\} Q = 7.48 \cdot 10^{-11} C \text{ note that this is the charge on one plate}$$

the other plate will have an equal but opposite charge  $Q = -7.48 \cdot 10^{-11} C$



30a) for parallel:  $C_{eq} = C_1 + C_2 + C_3$


$$C_1 = 5\mu F \quad C_2 = 4\mu F \quad C_3 = 9\mu F \quad C_{eq} = 5 + 4 + 9 = 18\mu F$$

b) for series:  $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

$$C_{eq} = \left( \frac{1}{5\mu F} + \frac{1}{4\mu F} + \frac{1}{9\mu F} \right)^{-1} = 1.78\mu F$$

31a) Note that the  $2\mu F$  and  $4\mu F$  are in parallel Hence  $C_{eq} = 2\mu F + 4\mu F = 6\mu F$




Redraw the new circuit will be:

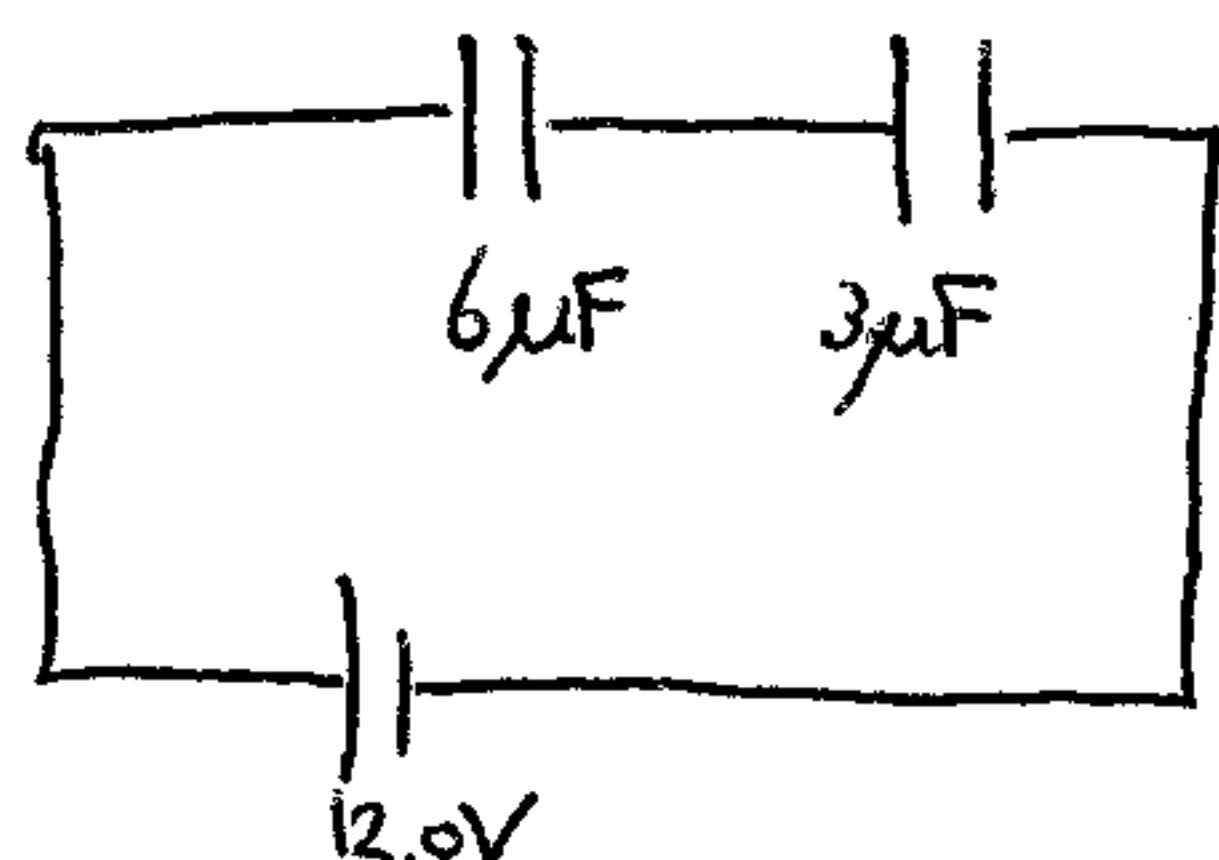

These are of course in series therefore

$$C_{eq} = \left( \frac{1}{6\mu F} + \frac{1}{3\mu F} \right)^{-1} = 2\mu F$$

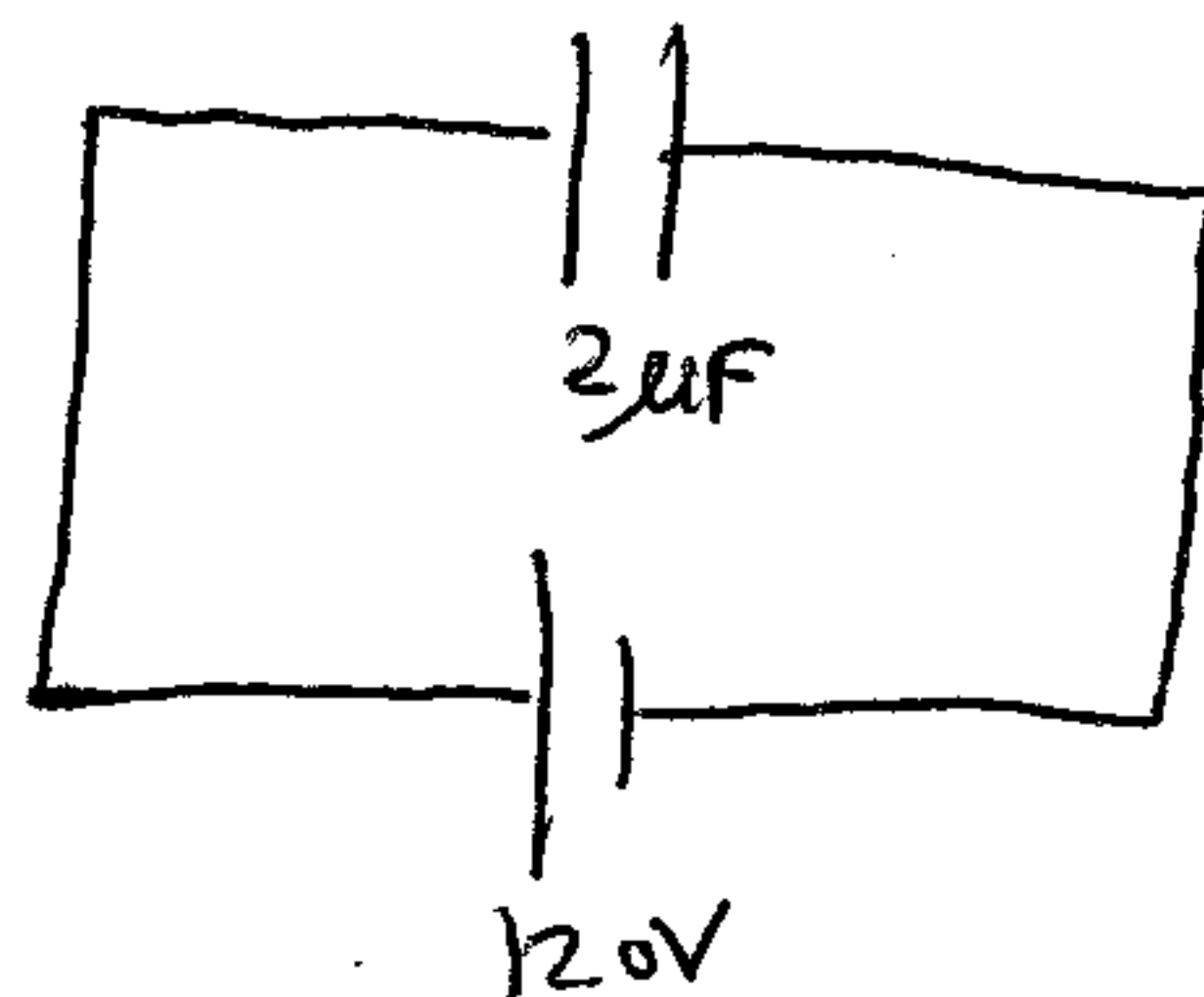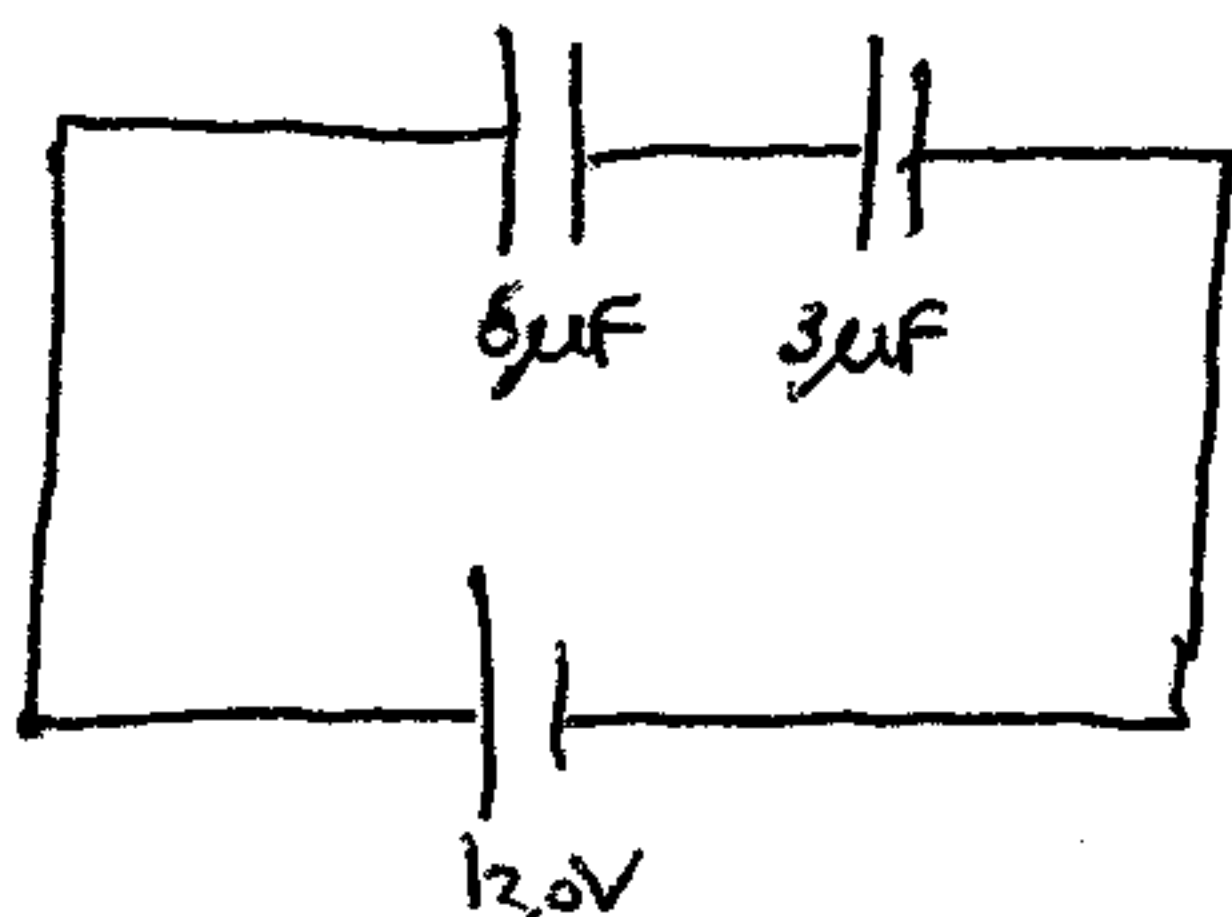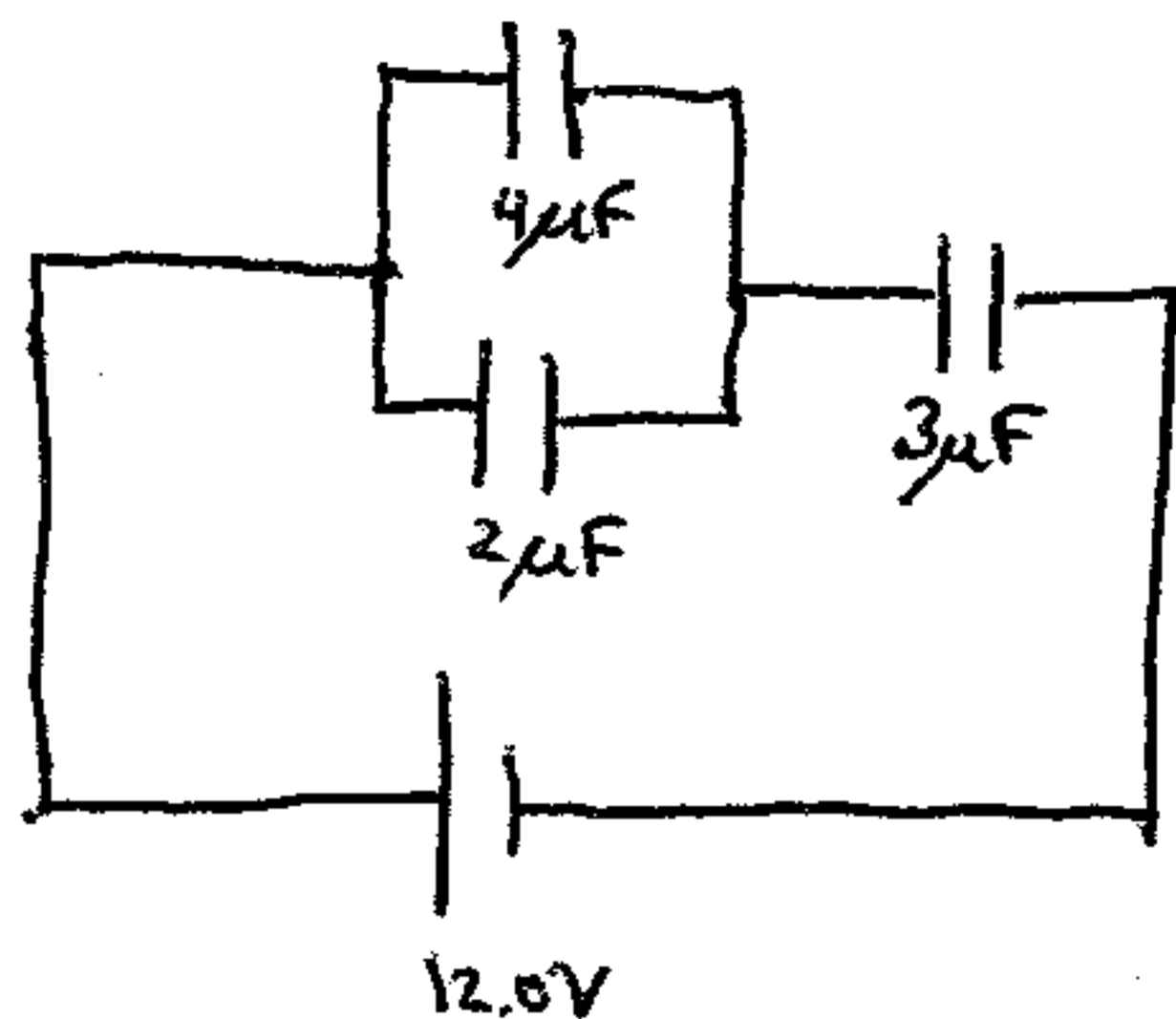b) The best strategy is redrawing each step and work backwards:



From the last picture  $C = \frac{Q}{\Delta V}$   $\Delta V = 12.0V$   $C = 2\mu F \Rightarrow Q = 2.4 \cdot 10^{-5} C$

going to the previous picture: the two capacitors are in series and must have the same charge on them  $Q = 2.4 \cdot 10^{-5} C$  on each. Therefore


$$\Delta V = \frac{Q}{C} = 8V \text{ for } 3\mu F \text{ and } \Delta V = \frac{Q}{C} = 4V \text{ for } 6\mu F.$$

going to the first picture: the two capacitors in parallel must have the same voltage:  $\Delta V = 4V$  for both the  $2\mu F$  and  $4\mu F$  capacitor

$$Q = C\Delta V = 8 \cdot 10^{-6} C \text{ for } 2\mu F \text{ and } Q = C\Delta V = 1.6 \cdot 10^{-5} C \text{ for } 4\mu F \text{ results:}$$

|                         |                         |                         |                           |                         |                           |
|-------------------------|-------------------------|-------------------------|---------------------------|-------------------------|---------------------------|
| $2\mu F: \Delta V = 4V$ | $Q = 8 \cdot 10^{-6} C$ | $4\mu F: \Delta V = 4V$ | $Q = 1.6 \cdot 10^{-5} C$ | $3\mu F: \Delta V = 8V$ | $Q = 2.4 \cdot 10^{-5} C$ |
|-------------------------|-------------------------|-------------------------|---------------------------|-------------------------|---------------------------|



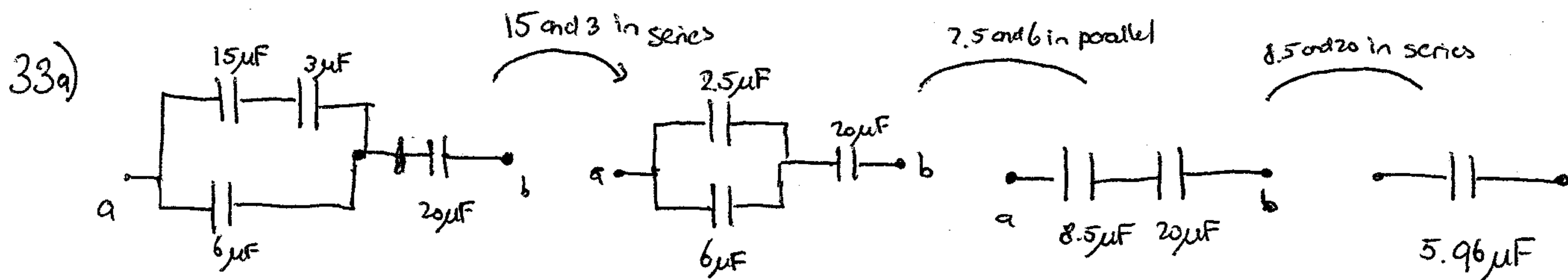


$C_{eq} = 5.96 \mu F$  for this circuit

b) Working backwards again: Using  $C = Q/\Delta V$  over and over again:

with two facts: 1) Capacitors in parallel have equal voltage  
2) Capacitors in series have equal charge

|                                    |                            |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                            |
|------------------------------------|----------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| $Q_{5.96} = 8.964 \cdot 10^{-5} C$ | $\Delta V_{5.96} = 15.0 V$ | <div style="border: 1px solid black; padding: 5px; display: inline-block;"> <math>Q_6 = 6.30 \cdot 10^{-5} C \quad \Delta V_6 = 10.5 V</math> </div><br><div style="border: 1px solid black; padding: 5px; display: inline-block;"> <math>Q_3 = 2.63 \cdot 10^{-5} C \quad \Delta V_3 = 8.77 V</math> </div><br><div style="border: 1px solid black; padding: 5px; display: inline-block;"> <math>Q_{20} = 8.94 \cdot 10^{-5} C \quad \Delta V_{20} = 4.47 V</math> </div><br><div style="border: 1px solid black; padding: 5px; display: inline-block;"> <math>Q_{2.5} = 2.63 \cdot 10^{-5} C \quad \Delta V_{2.5} = 10.5 V</math> </div> |
| $Q_{8.5} = 8.94 \cdot 10^{-5} C$   | $\Delta V_{8.5} = 10.5 V$  |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                            |
| $Q_{20} = 8.94 \cdot 10^{-5} C$    | $\Delta V_{20} = 4.47 V$   |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                            |
| $Q_{2.5} = 2.63 \cdot 10^{-5} C$   | $\Delta V_{2.5} = 10.5 V$  |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                            |
|                                    |                            |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                            |

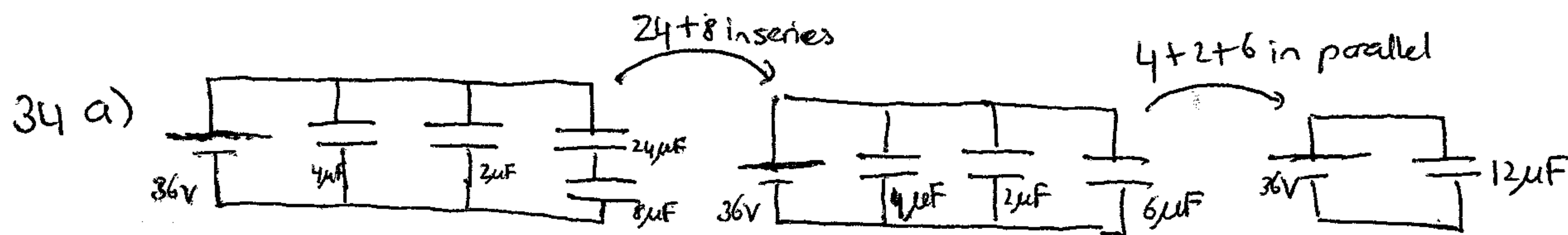

$C_{eq} = 12 \mu F$  for this circuit.

b)  $Q_{12} = 4.32 \cdot 10^{-4} C \quad \Delta V_{12} = 36.0 V$

$Q_4 = 1.44 \cdot 10^{-4} C \quad \Delta V_4 = 36.0 V$

$Q_2 = 7.20 \cdot 10^{-5} C \quad \Delta V_2 = 36.0 V$

$Q_6 = 2.16 \cdot 10^{-4} C \quad \Delta V_6 = 36.0 V$

$Q_{24} = 2.16 \cdot 10^{-4} C \quad \Delta V_{24} = 9.00 V$

$Q_8 = 2.16 \cdot 10^{-4} C \quad \Delta V_8 = 27.0 V$

7



$$37a) Q = C \Delta V$$

$$C = 25 \cdot 10^{-6} \text{ F}$$

$$\Delta V = 50 \text{ V}$$

$$Q_{25} = 1.25 \cdot 10^{-3} \text{ C}$$


$$Q = C \Delta V$$

$$C = 40 \mu\text{F}$$

$$\Delta V = 50 \text{ V}$$

$$Q_{40} = 2.00 \cdot 10^{-3} \text{ C}$$

b)

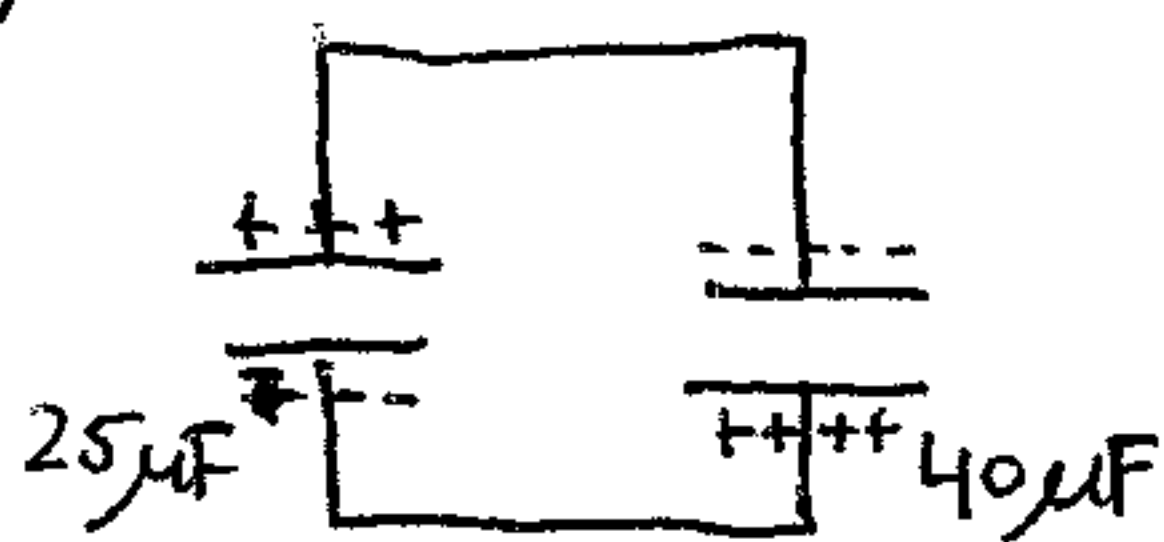

The first thing that happens is that the charge on the 25 μF capacitor gets cancelled. this leaves:

$$2 \cdot 10^{-3} - 1.25 \cdot 10^{-3} = 7.5 \cdot 10^{-4} \text{ C of charge in the system}$$

This charge gets divided over the two capacitors until the voltage across the two ~~plate~~ capacitors is the same.

$$\frac{Q_{25}}{C_{25}} = V = \frac{Q_{40}}{C_{40}}$$

$$\frac{Q_{25}}{Q_{40}} = \frac{25 \mu\text{F}}{40 \mu\text{F}} = \frac{5}{8}$$

$$Q_{25} = \frac{5}{8} Q_{40}$$

$$Q_{25} + Q_{40} = 7.5 \cdot 10^{-4} \text{ C}$$


$$\Rightarrow \frac{5}{8} Q_{40} + Q_{40} = 7.5 \cdot 10^{-4} \Rightarrow \frac{13}{8} Q_{40} = 7.5 \cdot 10^{-4}$$

$$Q_{40} = 4.62 \cdot 10^{-4} \text{ C}$$

$$Q_{25} = 7.5 \cdot 10^{-4} - 4.62 \cdot 10^{-4} = 2.88 \cdot 10^{-4} \text{ C}$$

$$\Delta V_{40} = Q_{40} / C_{40} = 11.6 \text{ V}$$

40)

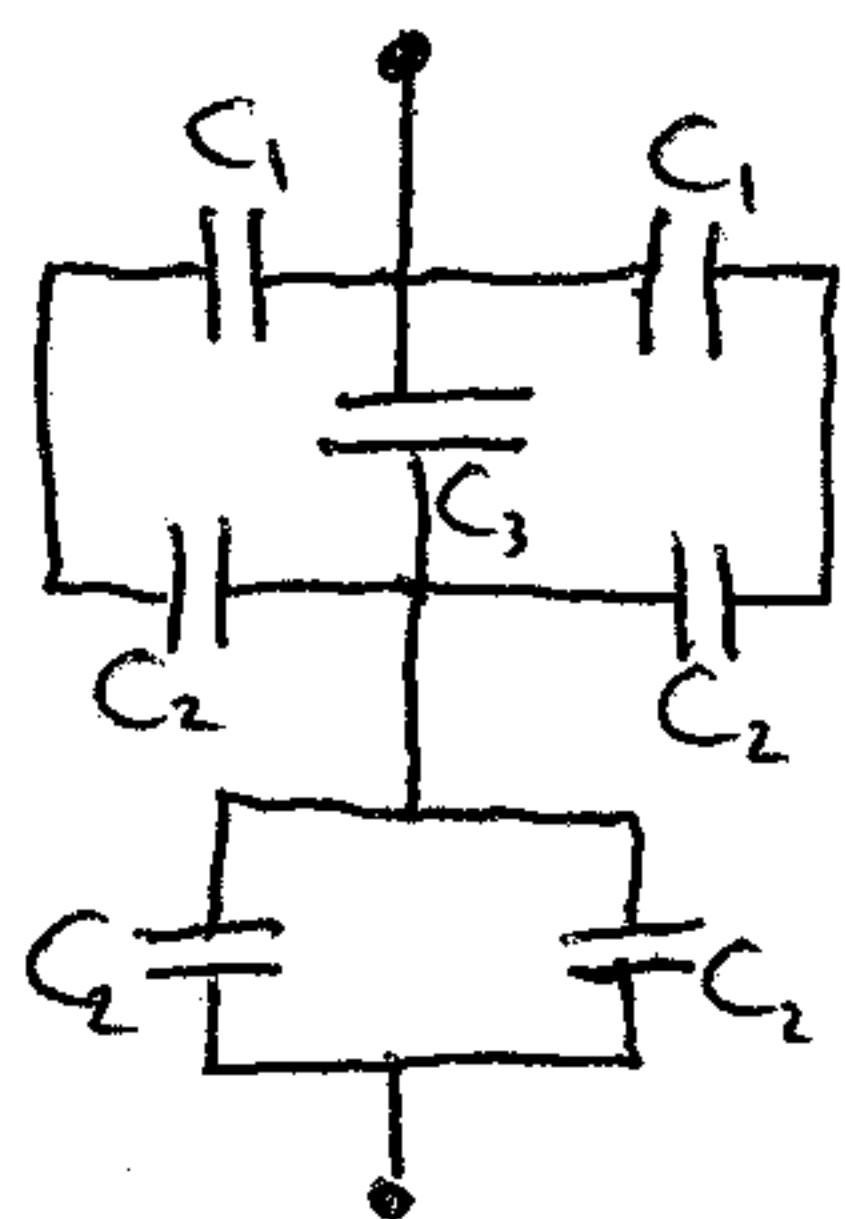


~~not shown~~  $C_1$  and  $C_2$  are in series

and  $C_2$  and  $C_2$


at the bottom are

in parallel -

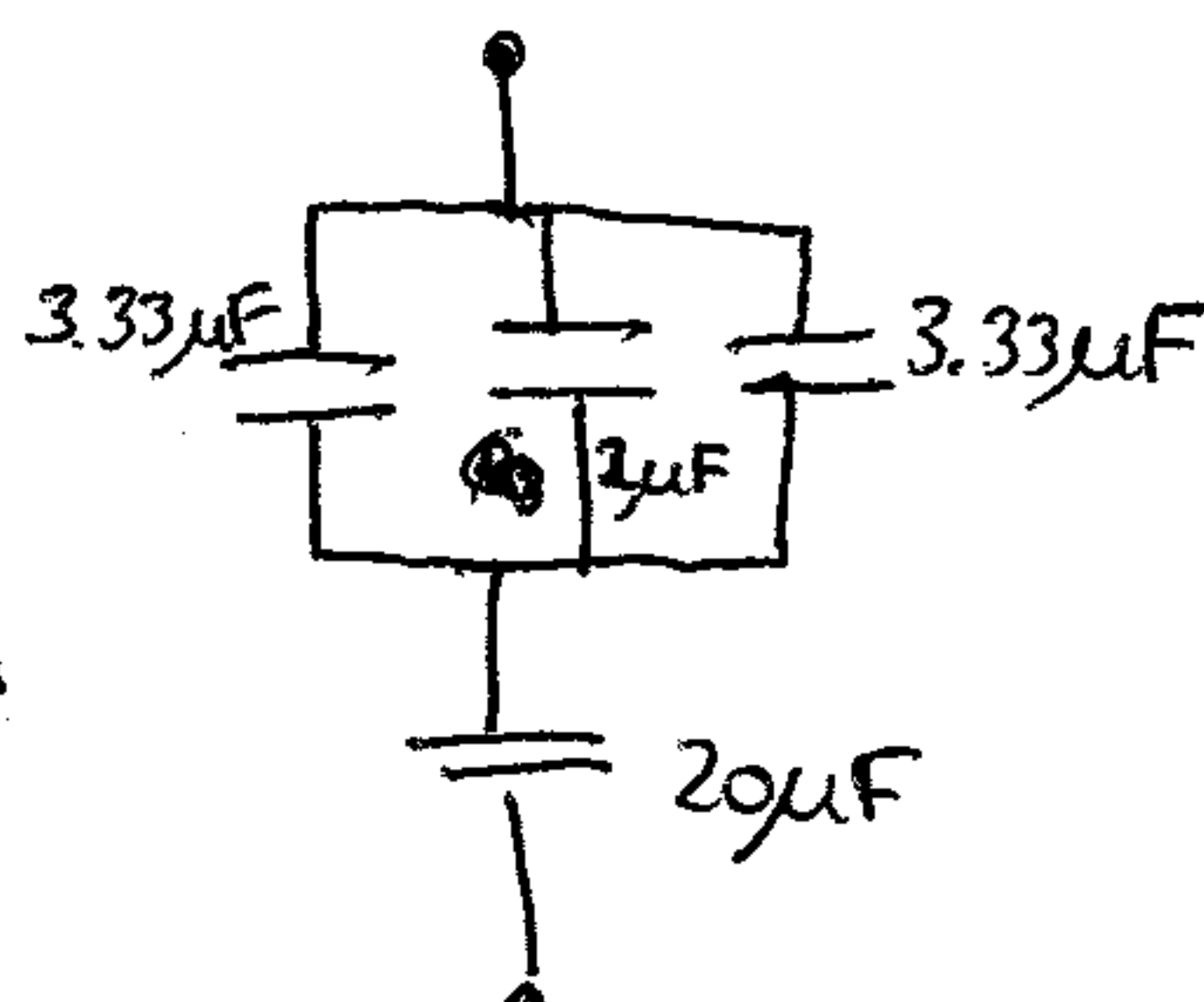
$$C_1 = 5 \mu\text{F} \quad C_2 = 10 \mu\text{F} \quad C_3 = 2 \mu\text{F}$$



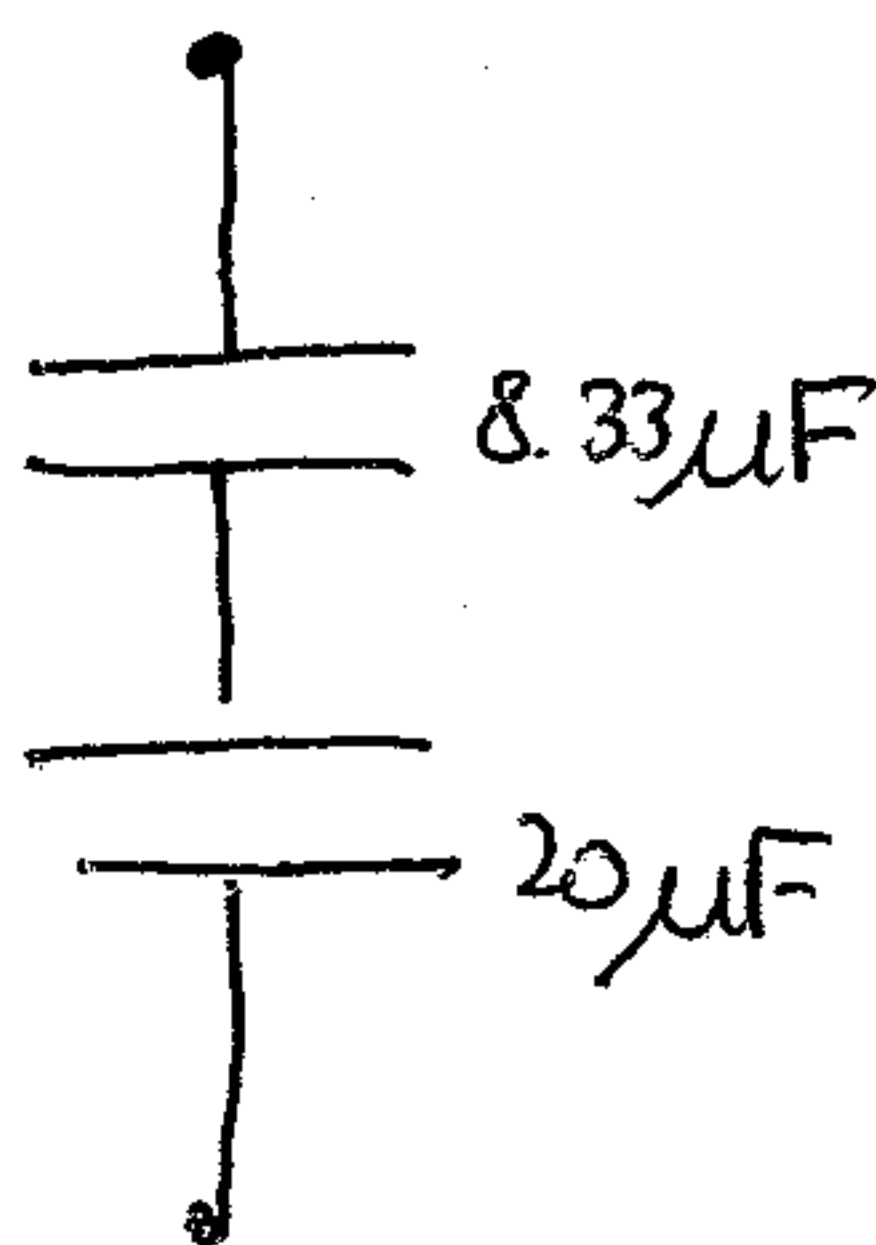the three capacitors on the top are in parallel



these are obviously in series

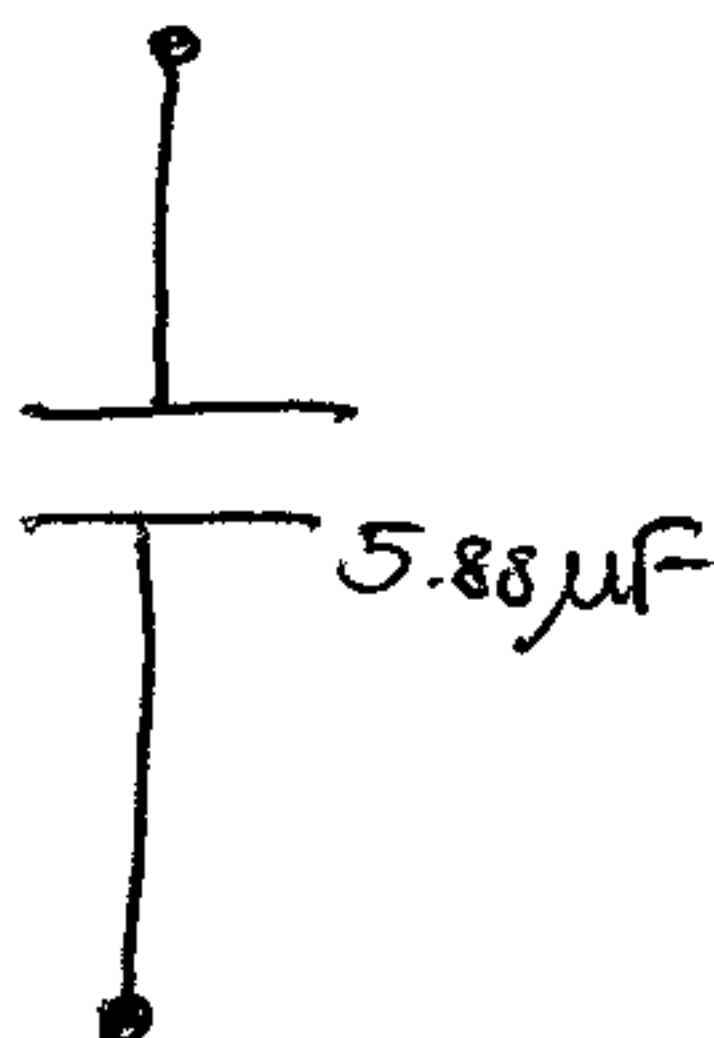

$$C_{eq} = 5.88 \mu\text{F}$$

8



43) first find  $C = \epsilon_0 A/d$

$$\left. \begin{array}{l} \epsilon_0 = 8.85 \cdot 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2 \\ A = 2.00 \cdot 10^{-4} \text{ m}^2 \\ d = 5 \cdot 10^{-3} \text{ m} \end{array} \right\} C = 3.54 \cdot 10^{-13} \text{ F}$$

$$\left. \begin{array}{l} E = \frac{1}{2} C (\Delta V)^2 \\ C = 3.54 \cdot 10^{-13} \text{ F} \\ \Delta V = 12.0 \text{ V} \end{array} \right\} E = 2.55 \cdot 10^{-11} \text{ J}$$

45) See problem 23)  $C = 1.1 \cdot 10^{-8} \text{ F}$

$$\Delta V = 2.4 \cdot 10^9 \text{ V}$$

$$E = \frac{1}{2} C (\Delta V)^2 = 3.2 \cdot 10^{10} \text{ J}$$

59)  $E = \frac{1}{2} C (\Delta V)^2$

$$\left. \begin{array}{l} E = 300 \text{ W} \cdot \text{s} = 300 \text{ J} \\ C = 3 \cdot 10^{-5} \text{ F} \end{array} \right\} \Delta V = \sqrt{\frac{2E}{C}} = 4.47 \cdot 10^3 \text{ V}$$

47)  $\Delta V = \frac{\Delta V_0}{K}$

$$\left. \begin{array}{l} \Delta V_0 = 100 \text{ V} \\ \Delta V = 25 \text{ V} \end{array} \right\} K = \frac{\Delta V_0}{\Delta V} = 4.0$$



$$49a) C = K\epsilon_0 A/d$$

$$\epsilon_0 = 8.85 \cdot 10^{-12} \text{ C}^2/\text{Nm}^2$$

$$K = 2.1$$

$$A = 175 \text{ cm}^2 = 1.75 \cdot 10^{-2} \text{ m}^2$$

$$d = 4.00 \cdot 10^{-5} \text{ m}$$

$$\left. \begin{array}{l} \epsilon_0 = 8.85 \cdot 10^{-12} \text{ C}^2/\text{Nm}^2 \\ K = 2.1 \\ A = 175 \text{ cm}^2 = 1.75 \cdot 10^{-2} \text{ m}^2 \\ d = 4.00 \cdot 10^{-5} \text{ m} \end{array} \right\} C = 8.1 \cdot 10^{-9} \text{ F}$$

$$b) E_{\text{max}} = 60 \cdot 10^6 \text{ V/m}$$

$$\Delta V_{\text{max}} = E_{\text{max}} \cdot d$$

$$d = 4.00 \cdot 10^{-5} \text{ m}$$

$$\left. \begin{array}{l} E_{\text{max}} = 60 \cdot 10^6 \text{ V/m} \\ \Delta V_{\text{max}} = E_{\text{max}} \cdot d \\ d = 4.00 \cdot 10^{-5} \text{ m} \end{array} \right\} \Delta V_{\text{max}} = 2400 \text{ V}$$

51a)

$$\rho = m/V$$

$$\rho = \text{density} = 1100 \text{ kg/m}^3$$

$$m = 1 \cdot 10^{-12} \text{ kg}$$

$$\left. \begin{array}{l} \rho = \text{density} = 1100 \text{ kg/m}^3 \\ m = 1 \cdot 10^{-12} \text{ kg} \end{array} \right\} V = \frac{m}{\rho} = 9.09 \cdot 10^{-16} \text{ m}^3$$

a sphere has volume formula:  $V = \frac{4}{3}\pi r^3$

$$r = \sqrt[3]{\frac{3V}{4\pi}} = 6.01 \cdot 10^{-6} \text{ m} \text{ is the radius of the blood cell.}$$

$$A = 4\pi r^2 = 4.54 \cdot 10^{-10} \text{ m}^2$$

$$b) C = K\epsilon_0 A/d$$

$$K = 5.00$$

$$\epsilon_0 = 8.85 \cdot 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$$

$$A = 4.54 \cdot 10^{-10} \text{ m}^2$$

$$d = 1.00 \cdot 10^{-7} \text{ m}$$

$$\left. \begin{array}{l} K = 5.00 \\ \epsilon_0 = 8.85 \cdot 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2 \\ A = 4.54 \cdot 10^{-10} \text{ m}^2 \\ d = 1.00 \cdot 10^{-7} \text{ m} \end{array} \right\} C = 2.01 \cdot 10^{-13} \text{ F}$$

$$c) C = Q/\Delta V$$

$$C = 2.01 \cdot 10^{-13} \text{ F}$$

$$\Delta V = 0.1 \text{ V}$$

$$\left. \begin{array}{l} C = 2.01 \cdot 10^{-13} \text{ F} \\ \Delta V = 0.1 \text{ V} \end{array} \right\} Q = C\Delta V = 2.01 \cdot 10^{-14} \text{ C} \Rightarrow 2.01 \cdot 10^{-14} \text{ C} \times \frac{1 \text{ e}}{1.602 \cdot 10^{-19} \text{ C}} = 1.25 \cdot 10^5 \text{ e}$$