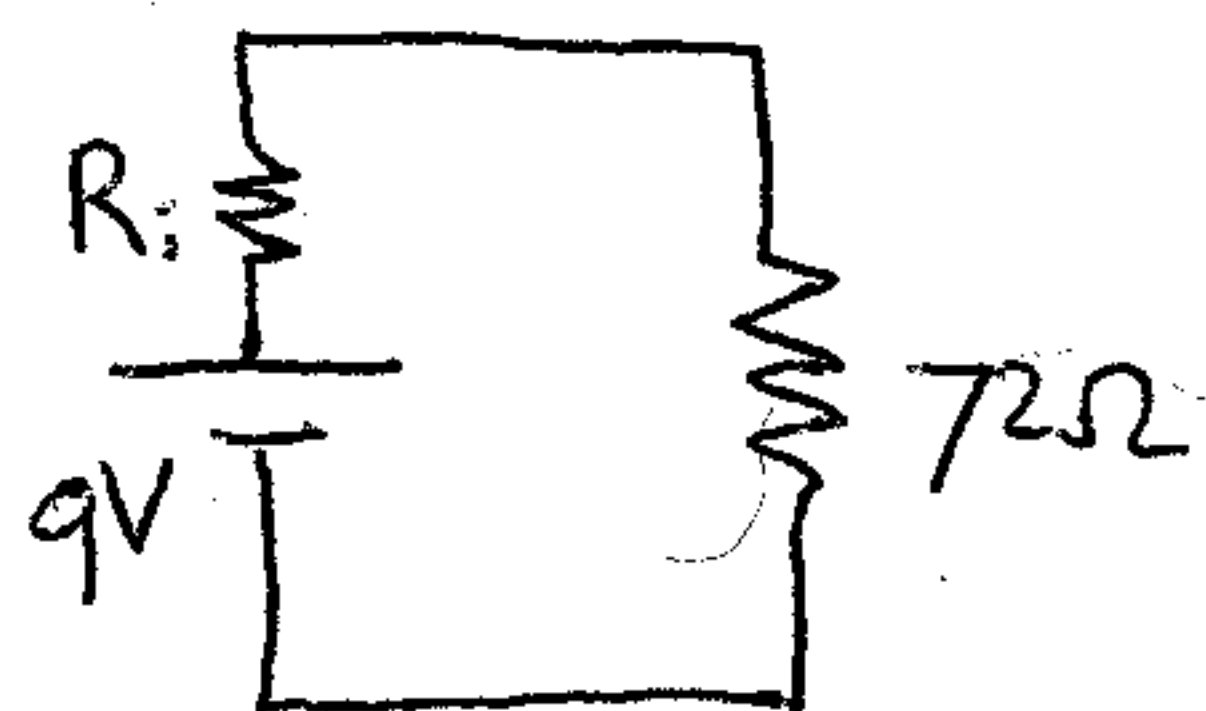


1)



$$\Delta V = \mathcal{E} - IR_i$$

$$\Delta V = I \cdot R$$

$$I = 117 \text{ mA}$$

$$R = 72 \Omega$$


$$\left. \begin{array}{l} \Delta V = I \cdot R \\ I = 117 \text{ mA} \\ R = 72 \Omega \end{array} \right\} \Delta V = 8.42 \text{ V}$$

$$\mathcal{E} = 9 \text{ V} \quad I = 117 \text{ mA} \quad \Delta V = 8.42 \text{ V} \quad \left. \vphantom{\mathcal{E}} \right\} R_i = (\mathcal{E} - \Delta V) / I = 4.92 \Omega$$

Note: This is one way of solving the problem using the formula given. Two (better) ways of solving this problem is:

- ① pretend R_i is just a regular resistor and add the two resistors up in series
- ② use Kirchhoff's 'voltage loop law/rule

2)

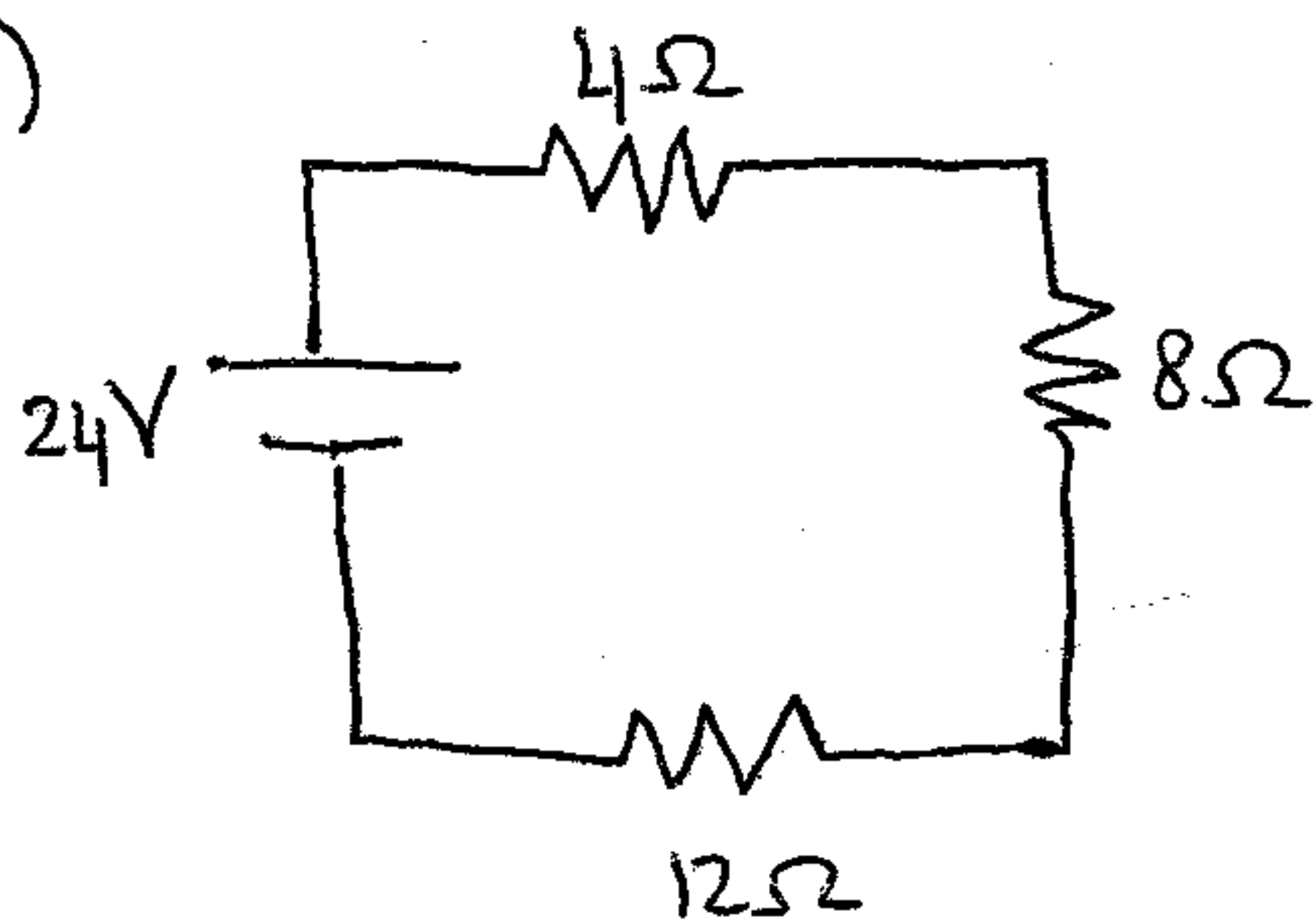


a) the resistors are connected in series:

$$R_{eq} = 4\Omega + 8\Omega + 12\Omega = 24\Omega$$

b) $I = V/R = 24\text{V}/24\Omega = 1.0\text{A}$ in each resistor because current is the same in series.

c)

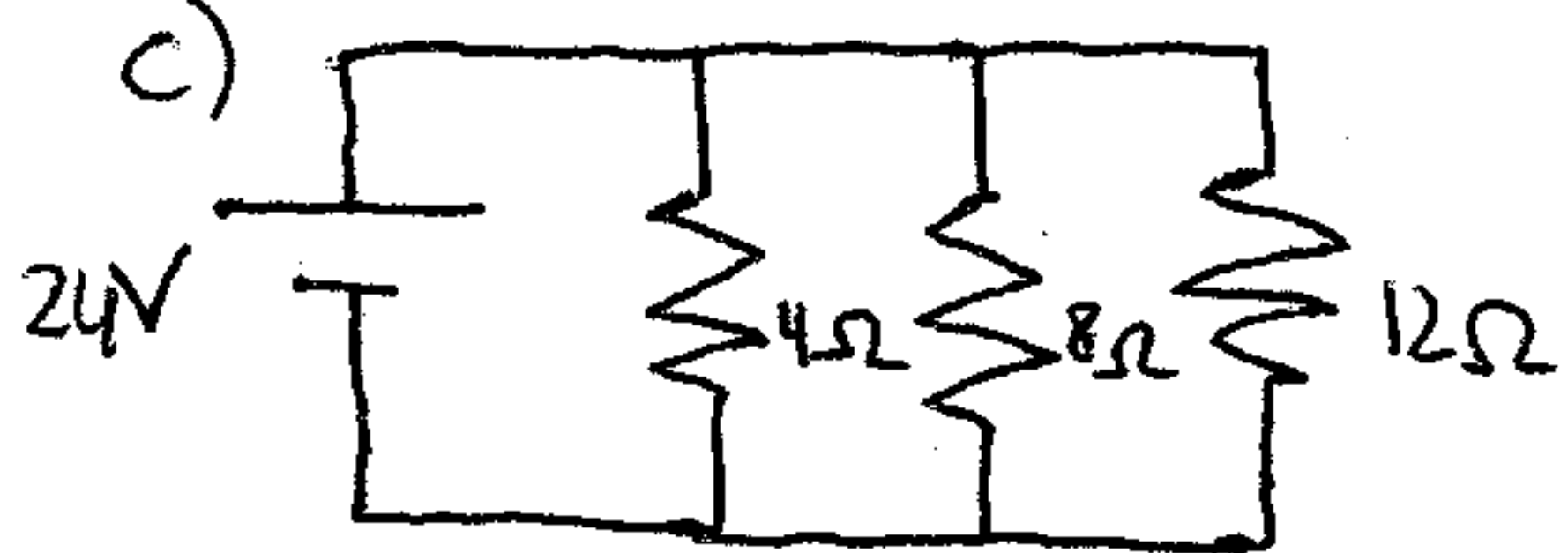

a) the resistors are in parallel:



$$R_{eq} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = 2.2 \Omega$$

b) $I = V/R$ the voltage is the same in parallel:

$$V = 24\text{V} \text{ for all resistors}$$

$$I_{4\Omega} = 6.0\text{A} \quad I_{8\Omega} = 3.0\text{A} \quad I_{12\Omega} = 2.0\text{A}$$

①

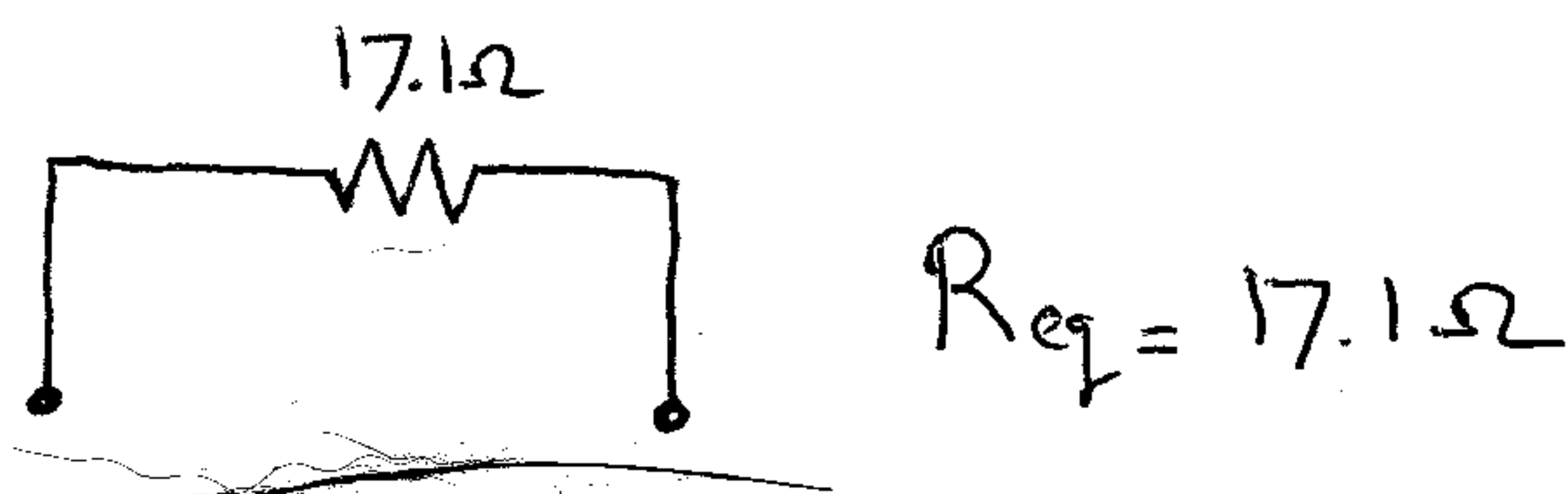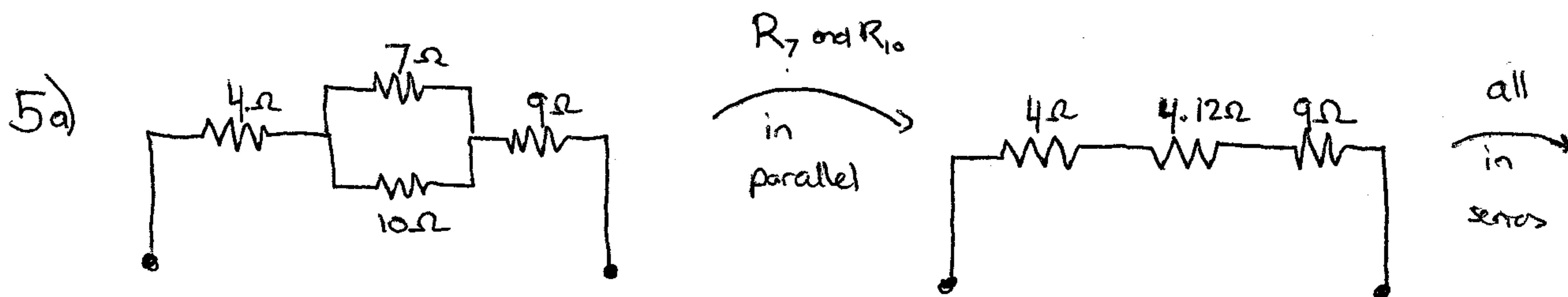

b) As with capacitors, work your way backwards:

$$R_{7\Omega} : V_7 = 34.0V \quad I_7 = 2.00A$$


$$R_{9\Omega} : \boxed{I_9 = 2.00A} \text{ because the current is equal for resistors in series, therefore } R_{4\Omega} : \boxed{I_4 = 2.00A} \text{ and } I_{4.12} = 2.00A \text{ also.}$$

The voltage drop across the 4.12Ω resistor is:


$V = I \cdot R = 8.24V$ we found this because voltage is the same for resistors in parallel:

$$R_{7\Omega} : V = 8.24V \Rightarrow \boxed{I_7 = V/R = 1.18A} \quad R_{10\Omega} : V = 8.24V \Rightarrow \boxed{I_{10\Omega} = V/R = 0.824A}$$

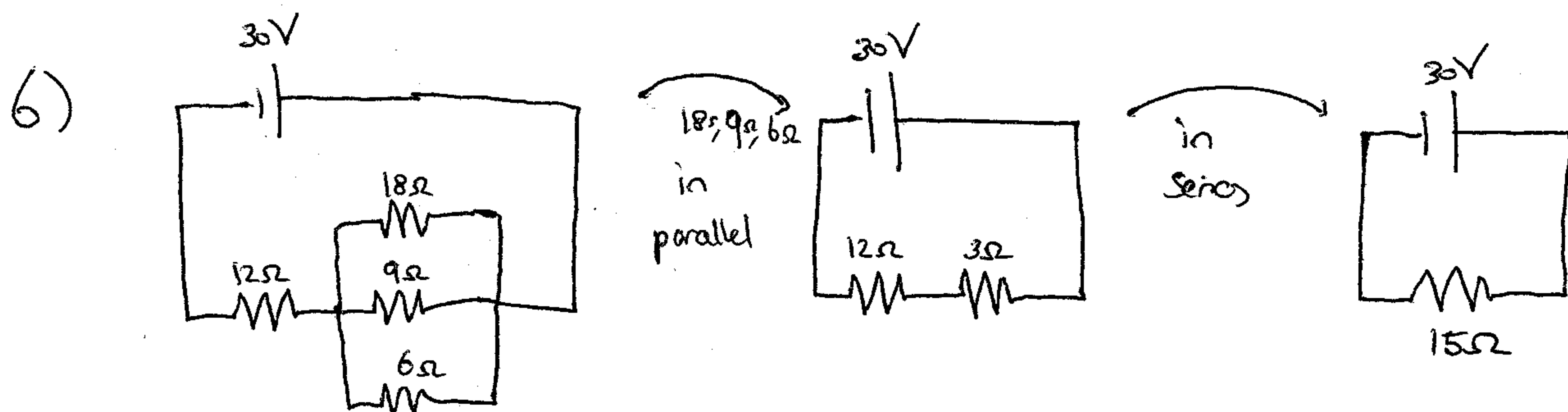
(Note the answers are slightly off because of rounding).



$$R_{eq} = 15\Omega$$

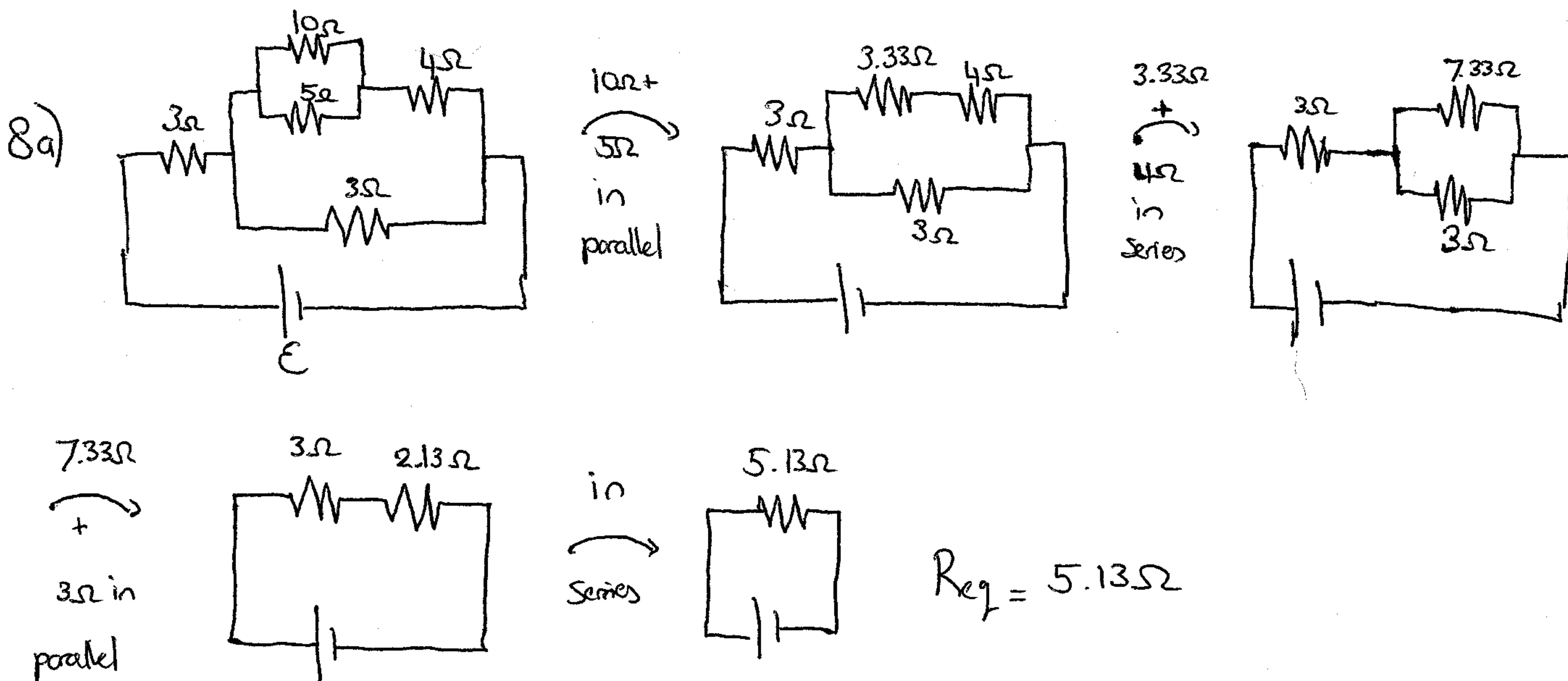

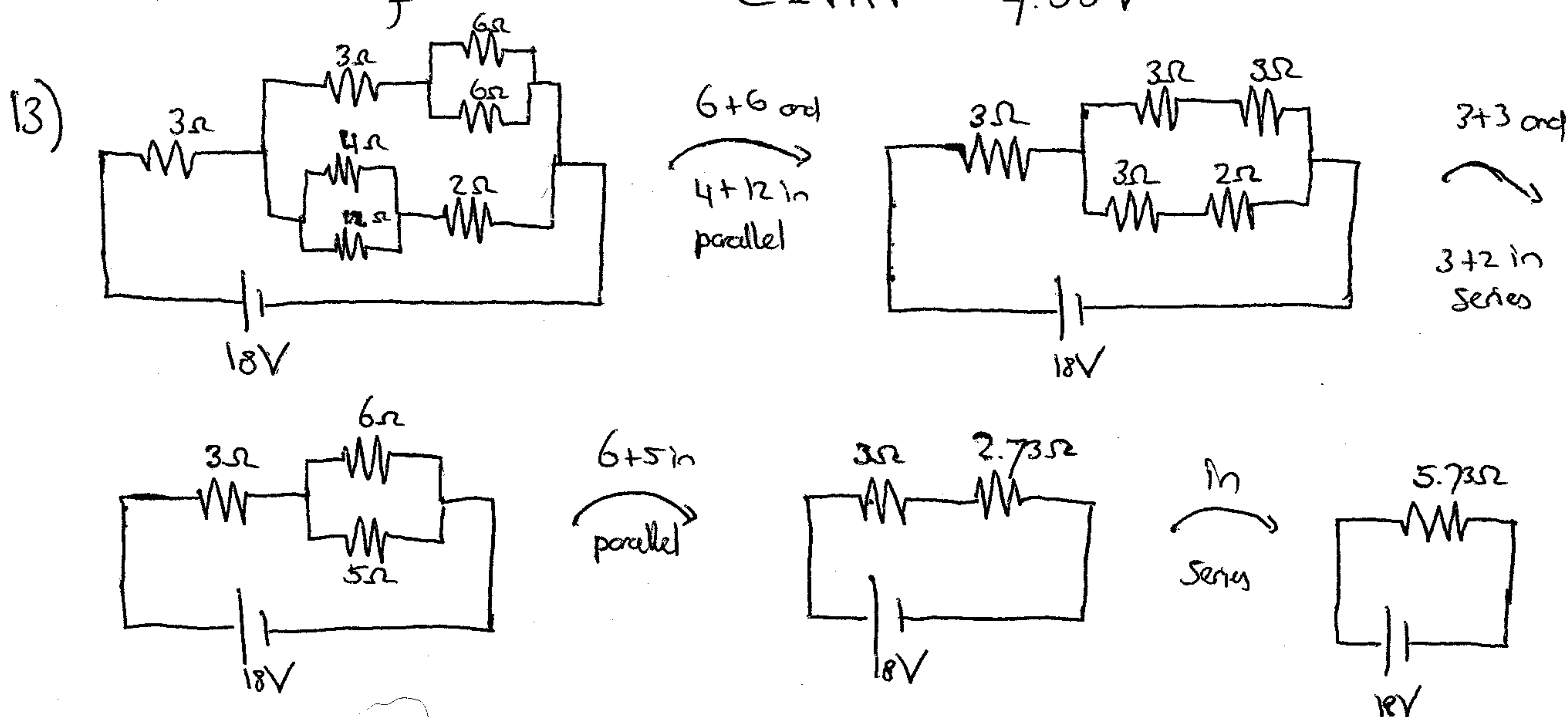b) Power = $P = V^2/R$ where $V = \text{Emf} = \mathcal{E}$ and $R = R_{eq}$ the equivalent resistance of the circuit $\mathcal{E} = \sqrt{R \cdot P} = 4.53\text{V}$




Again the trick is work your way backward remembering


- 1) Voltage is equal in parallel resistors
 - 2) Current is equal in series resistors
- The orderings to get the answer is:

$$I_{5\Omega} = 3.14\text{A} \Rightarrow V_{2.7\Omega} = 8.57\text{V} \Rightarrow I_{1.71\text{A}} \Rightarrow V_{3\Omega} = 5.14\text{V} \Rightarrow I_{12\Omega} = 0.428\text{A}$$



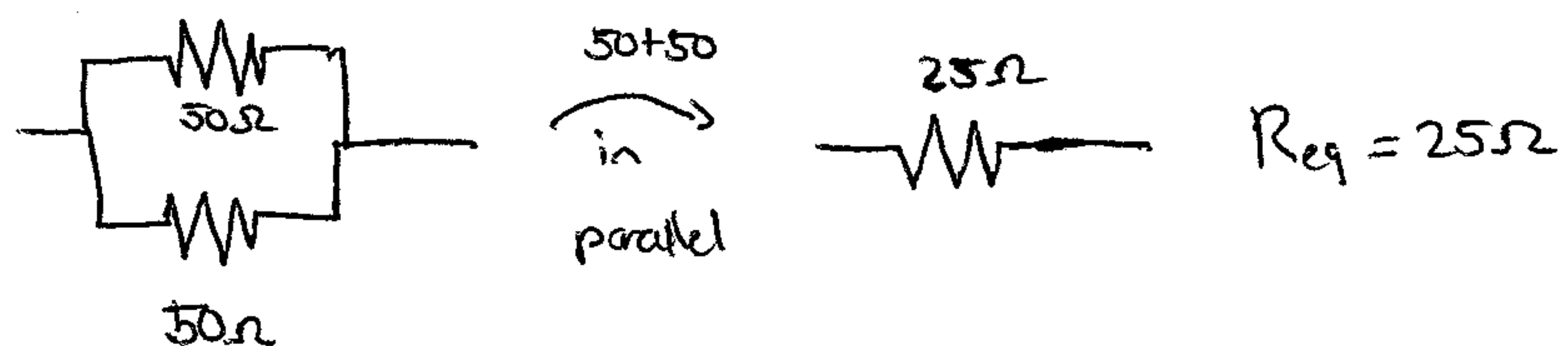
15) There is no clever way of doing this problem. Just play around until you get the right value. One helpful hint: two equal resistors in parallel will have an equivalent resistance of $\frac{1}{2}$ the resistance value:



a) to get 45Ω use the above + 20Ω :

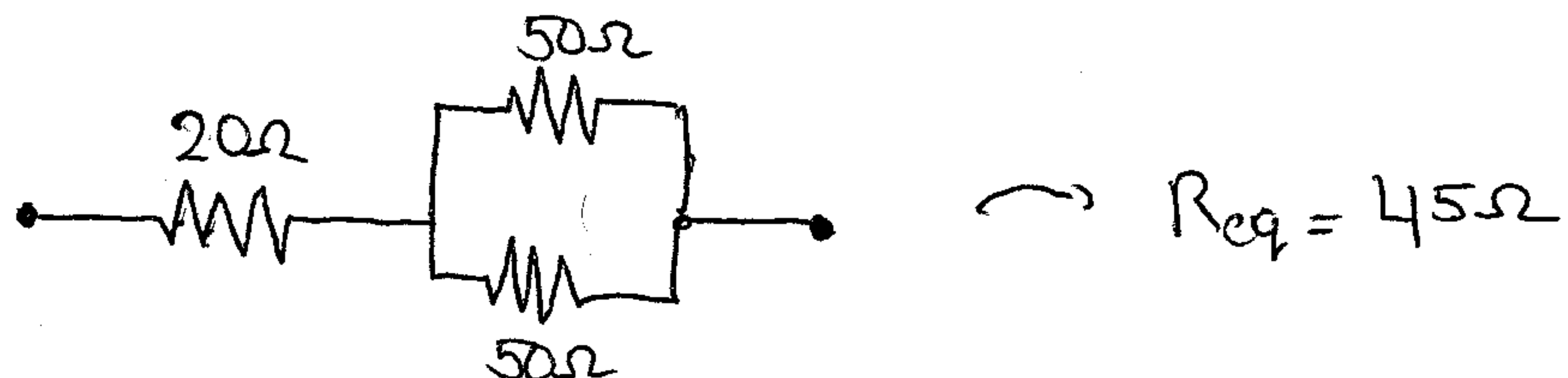


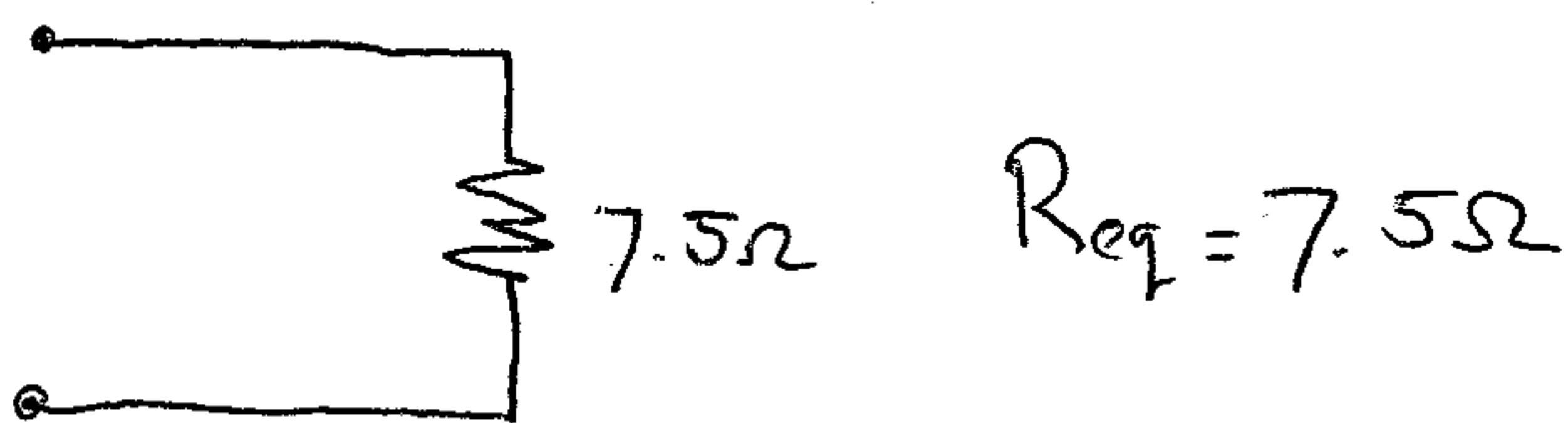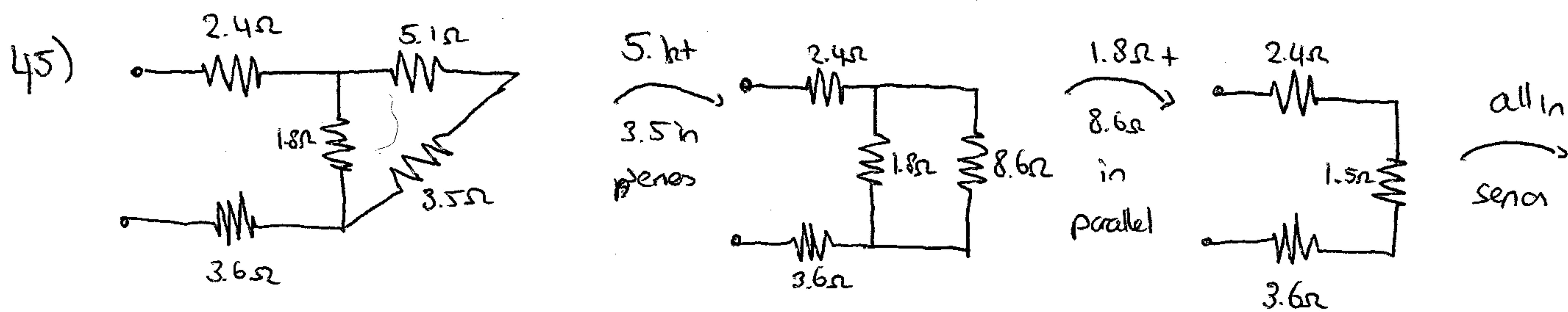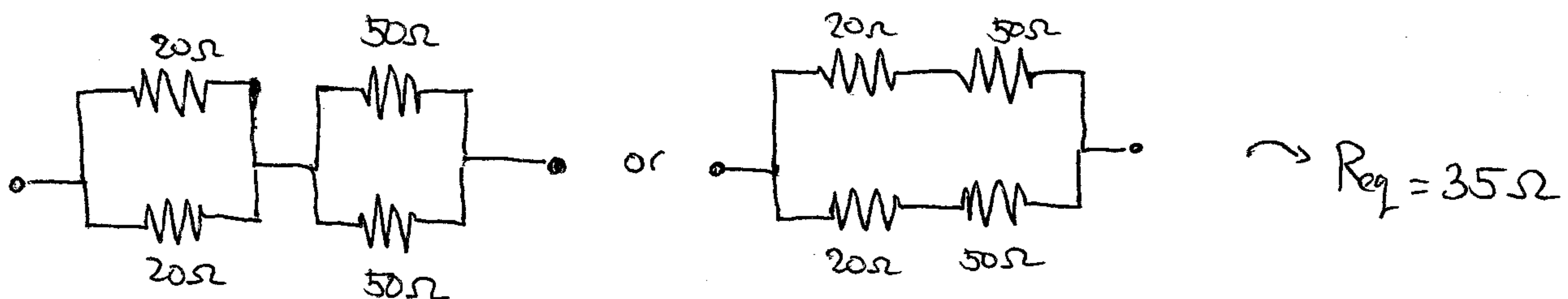b) to get 35Ω you need to get 10Ω i.e. 20Ω in parallel:



Don't let the beginning picture fool you they are still in ~~parallel~~ series

17)

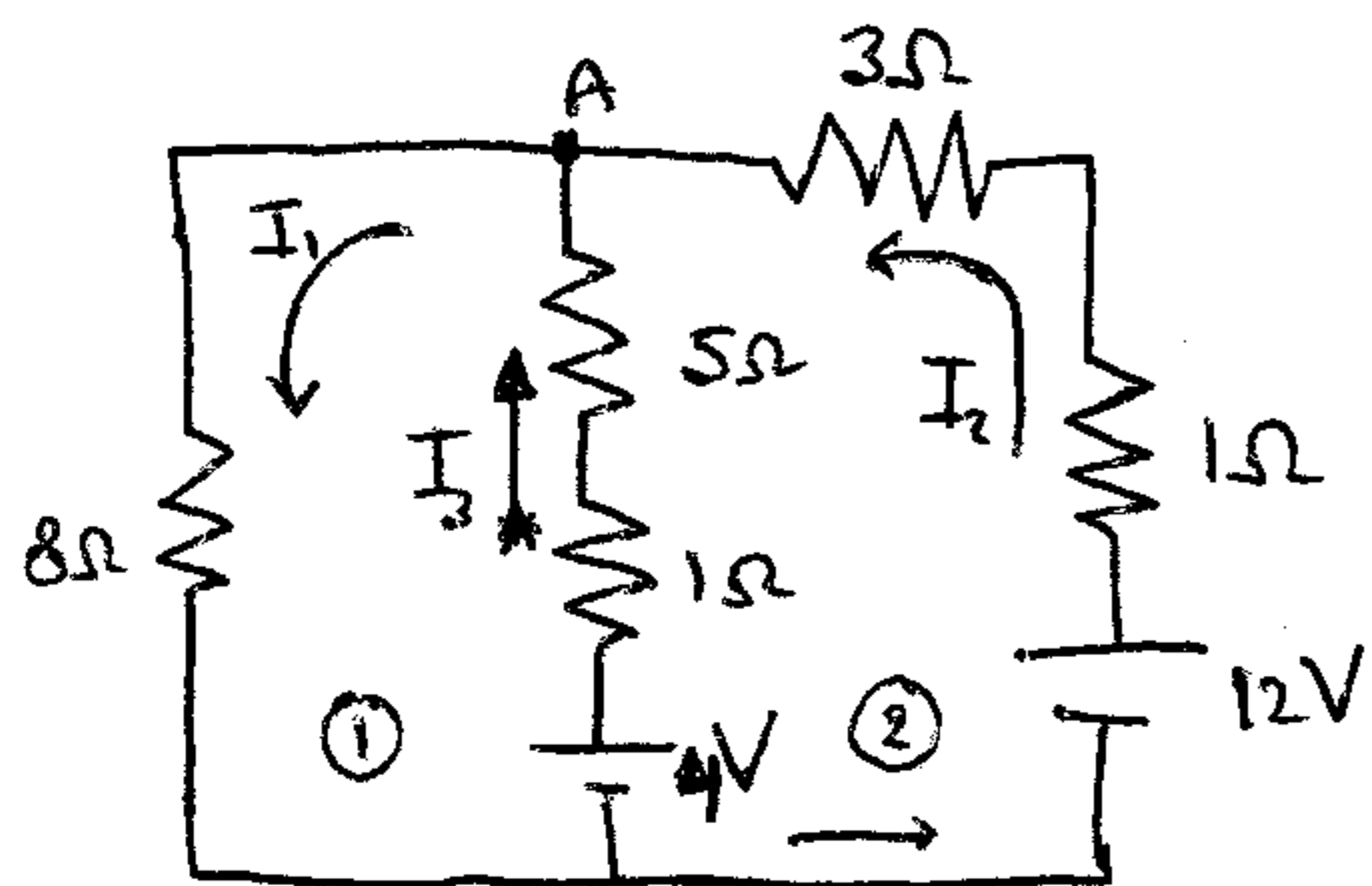

lets look at loop ① loop law gives:

$$4V - 1 \cdot I_3 - 5 \cdot I_3 - 8 I_1 = 0$$

Now loop ② will give:

$$12V - 1 \cdot I_2 - 3 \cdot I_2 + 5 I_3 + 1 \cdot I_3 - 4 = 0$$

* Note the + in front of the I_3 's if you

go against the current, it gives positive and with the current will

give a negative. The same for a voltage source, if you go

from - to + the voltage is positive, otherwise it is negative.

The last equation comes from the junction law: $I_2 + I_3 = I_1$

(from junction A) rewriting these gives:

$$-8 I_1 - 6 I_3 + 4 = 0 \Rightarrow I_1 = -\frac{3}{4} I_3 + \frac{1}{2}$$

$$-4 I_2 + 6 I_3 + 8 = 0 \Rightarrow I_2 = \frac{3}{2} I_3 + 2$$

$$I_1 - I_2 - I_3 = 0 \Rightarrow \left(-\frac{3}{4} I_3 + \frac{1}{2}\right) - \left(\frac{3}{2} I_3 + 2\right) - I_3 = 0$$

$$-\frac{13}{4} I_3 - \frac{3}{2} = 0 \quad I_3 = \frac{3}{2} \cdot \frac{-4}{13} = -\frac{6}{13} A \approx -0.462 A$$

$$I_1 = -\frac{3}{4} (-0.462) + \frac{1}{2} \approx 0.847 A$$


$$I_2 = \frac{3}{2} (-0.462) + 2 \approx 1.31 A$$

Note that I guessed the direction of I_3 wrong, I thought it would flow up, but since I_3 is negative it flows down.

$$I_{8\Omega} = 0.847 A \text{ downward}$$

$$I_{5\Omega} = 0.462 A \text{ downward}$$

$$I_{3\Omega} = 1.31 A \text{ left.}$$

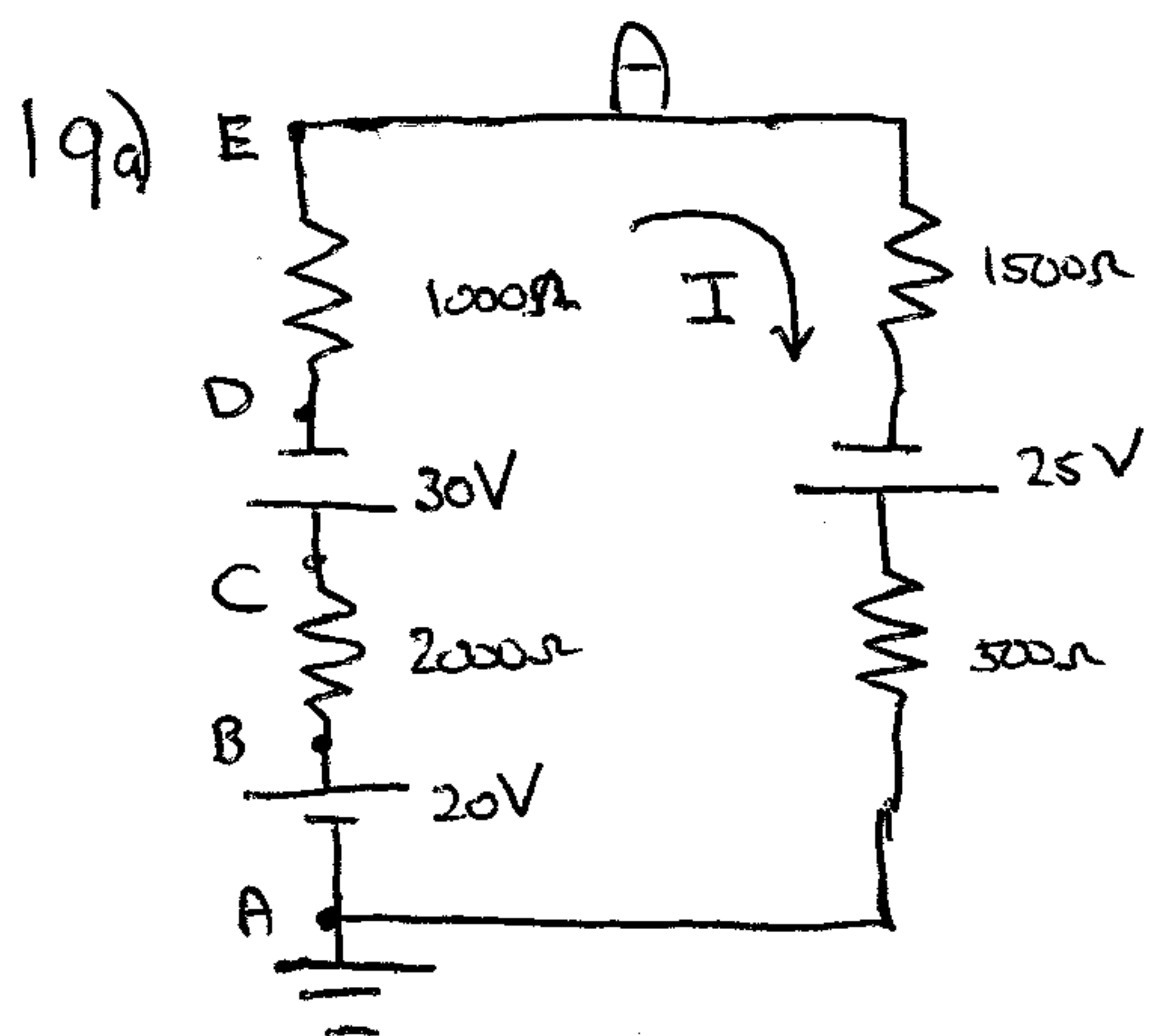

loop law gives:

$$20 - 2000 \cdot I - 30 - 1000 \cdot I - 1500 \cdot I + 25 - 500 \cdot I = 0$$

$$15 - 5000I = 0$$

$$a) I = \frac{15}{5000} = 3 \cdot 10^{-3} A = 3 \text{ mA}$$

$$b) \text{ point A} = 0V$$

$$\text{point B} = 20V$$

$$\text{point C} = 20 - 2000 \cdot 3 \text{ mA} = 14V$$


$$\text{point D} = 14 - 30 = -16V$$

$$\text{point E} = -19V$$

I.E the wire is at -19V.

$$c) \Delta V = I \cdot R = 3 \cdot 10^{-3} A \cdot 1500 \Omega = 4.5V$$

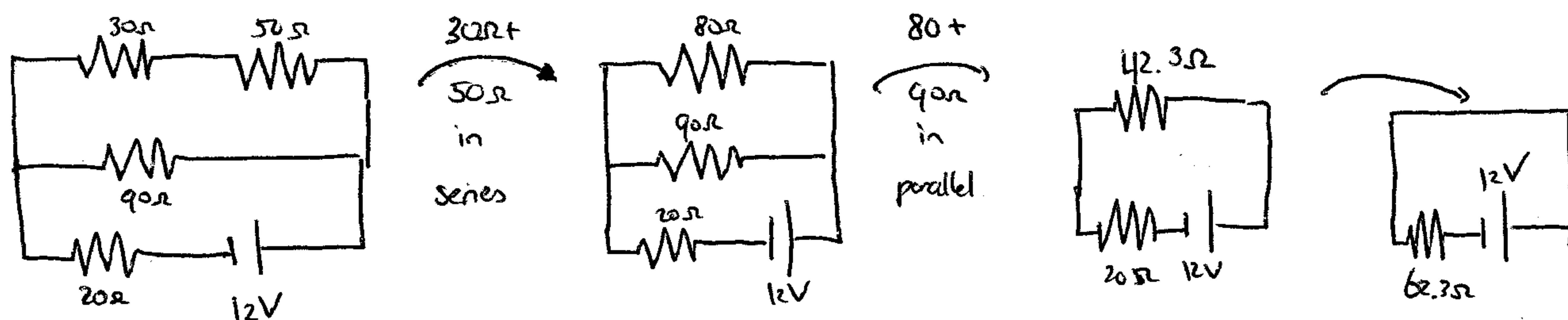22) The easiest way to do this is using equivalent resistors:




$$I_{62.3\Omega} = 0.193A \Rightarrow V_{42.3\Omega} = 8.16V \Rightarrow I_{80\Omega} = 0.102A \Rightarrow V_{50\Omega} = 5.1V$$

$$Power = V^2/R = (5.1)^2/50\Omega = 0.52W.$$

The other way of doing this problem is using Kirchhoff's laws, but then you get a mess like problem 17).

27)

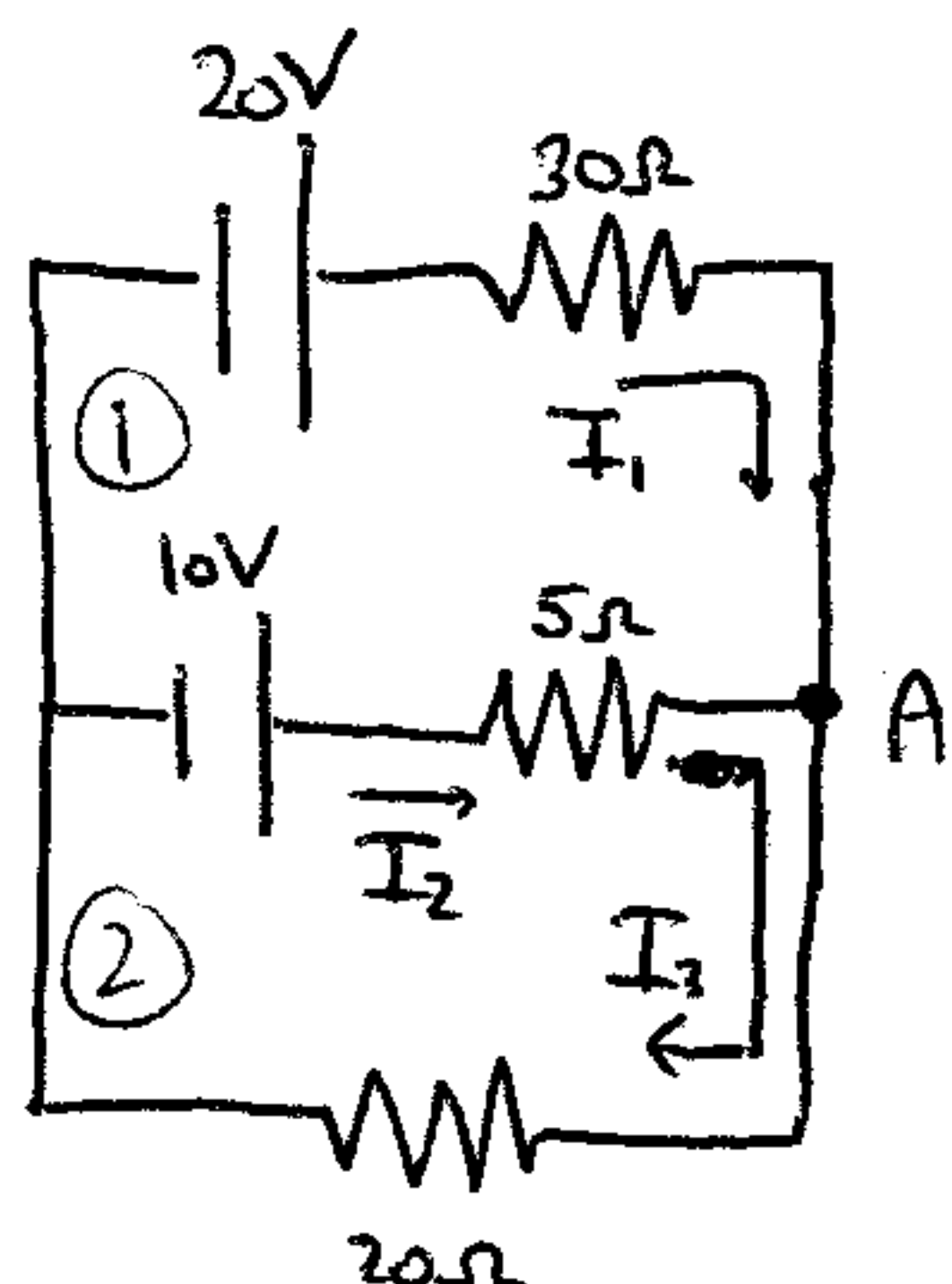

$$\text{loop ①: } 20V - 30 \cdot I_1 + 5 I_2 - 10 = 0$$

$$\text{loop ②: } 10V - 5 I_2 - 20 I_3 = 0$$

$$\text{Junction A: } I_1 + I_2 = I_3$$

$$\text{① } -30 I_1 + 5 I_2 + 10 = 0 \Rightarrow I_1 = \frac{1}{6} I_2 + \frac{1}{3}$$

$$\text{② } -5 I_2 - 20 I_3 + 10 = 0 \Rightarrow I_3 = -\frac{1}{4} I_2 + \frac{1}{2}$$


$$\text{③ } \left(\frac{1}{6} I_2 + \frac{1}{3}\right) + (I_2) = \left(-\frac{1}{4} I_2 + \frac{1}{2}\right)$$

$$\frac{17}{12} I_2 = \frac{1}{6} \quad I_2 = \frac{2}{17} A \approx 0.118 A \quad I_{5\Omega} = 0.118 A \text{ to the right}$$

$$I_3 = -\frac{1}{4} (0.118) + \frac{1}{2} \approx 0.471 A \quad I_{20\Omega} = 0.471 A \text{ to the left}$$

$$I_1 = \frac{1}{6} I_2 + \frac{1}{3} \approx 0.353 A \quad I_{30\Omega} = 0.353 A \text{ to the right}$$

49 a)

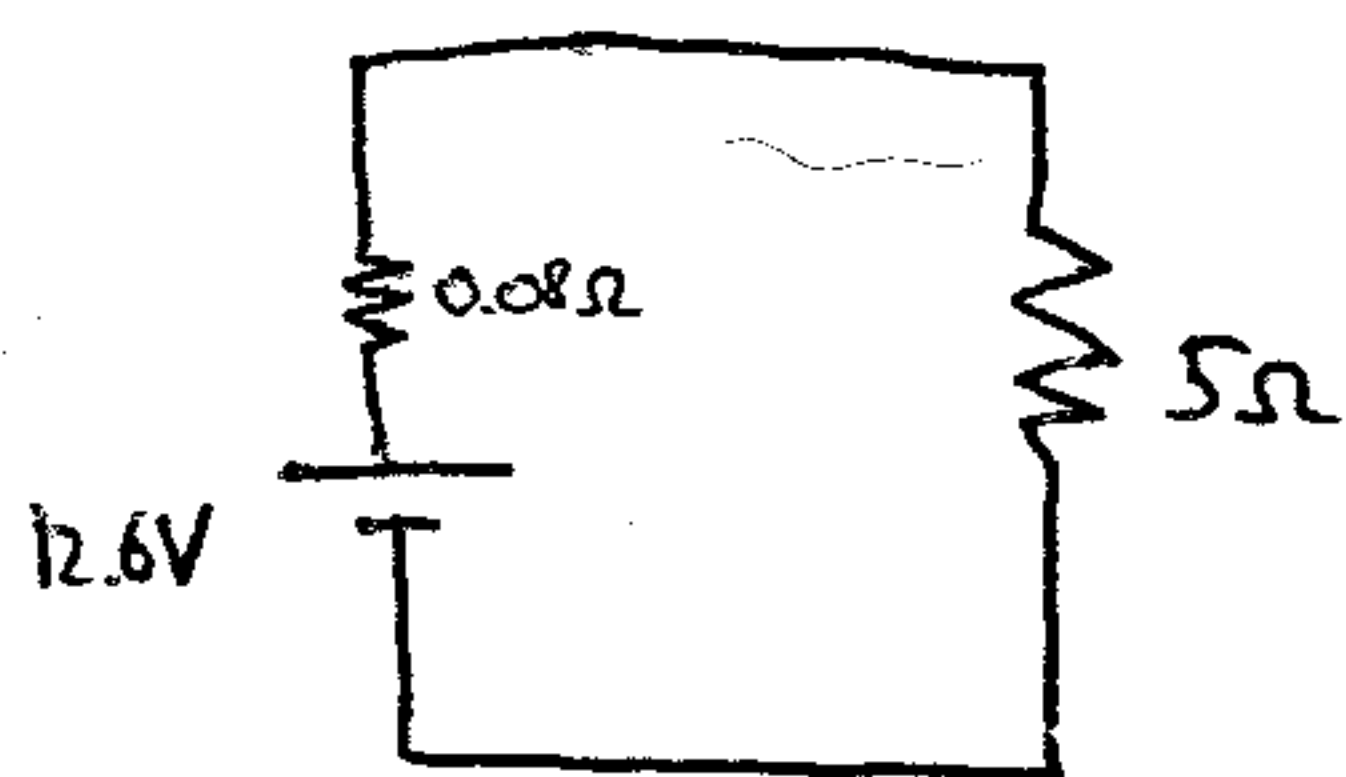


$$\text{Equivalent } R_{eq} = 5.08 \Omega$$

$$I = \frac{12.6V}{5.08 \Omega} = 2.48 A$$

$$V = I \cdot R = 2.48 \cdot 5 = 12.4 V$$

b)

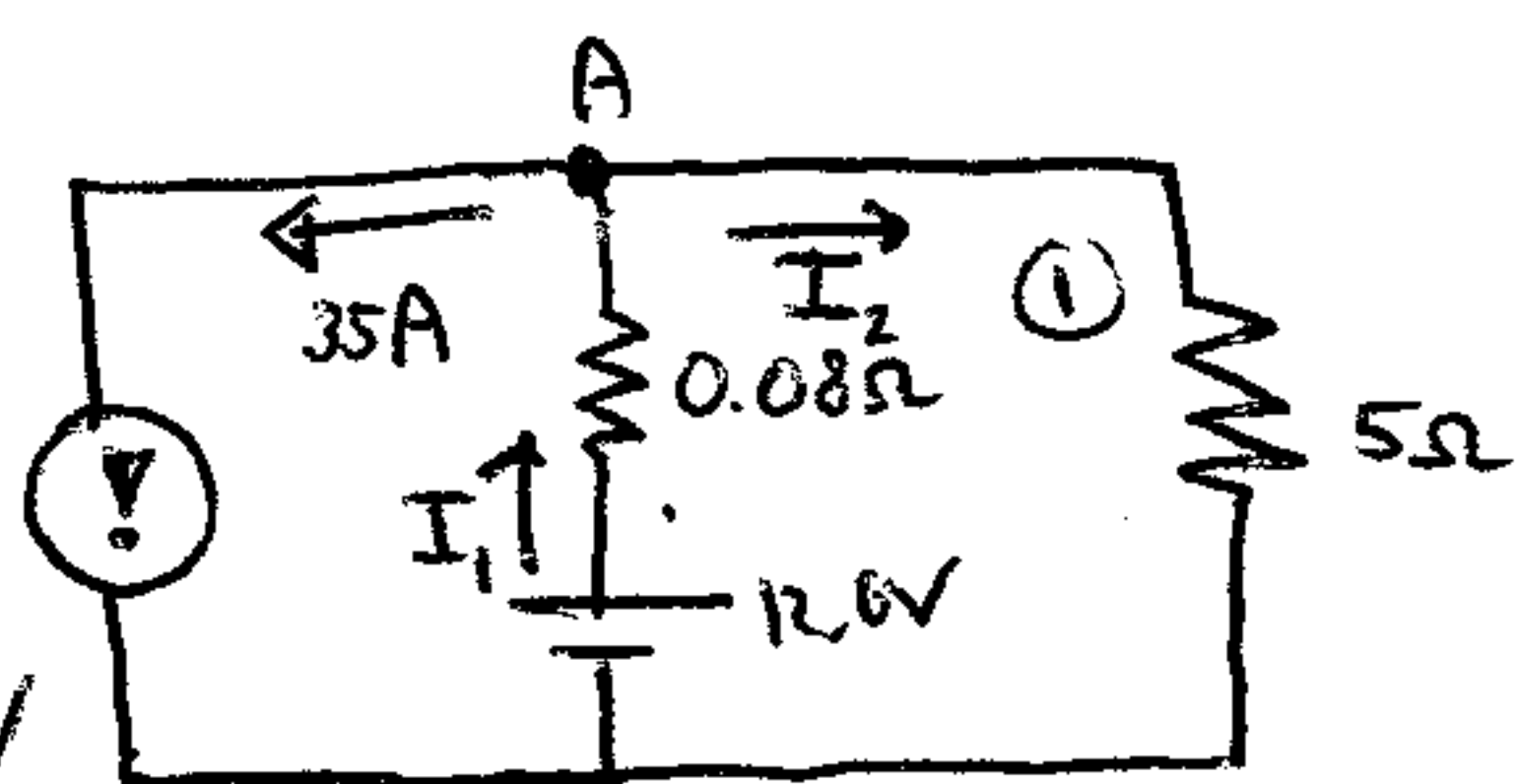

starter motor

Use Kirchhoff's loop law on loop ①

$$12.6 - 0.08 I_1 - 5 \cdot I_2 = 0$$

$$I_1 = 35 + I_2 \quad \leftarrow \text{junction law at A}$$

$$12.6 - 0.08(I_2 + 35) - 5 I_2 = 0 \quad \text{or } 5.08 I_2 = 9.8 \quad I_2 = 1.93 A$$

$$\text{Hence } V = I \cdot R = 1.93 A \cdot 5 \Omega = 9.65 V$$

⑦

$$31 \text{ a) } \tau = R \cdot C$$

$$\left. \begin{array}{l} R = 2 \cdot 10^6 \Omega \\ C = 6 \cdot 10^{-6} \text{ F} \end{array} \right\} \tau = 12 \text{ Sec is the time constant}$$

b) When the switch is closed a long time, the voltage over the capacitor will be equal to the $\mathcal{E}_{\text{mf}}$, because no charges are flowing:

$$\left. \begin{array}{l} Q = C \cdot V \\ C = 6 \cdot 10^{-6} \text{ F} \\ V = 20 \text{ V} \end{array} \right\} Q = 1.2 \cdot 10^{-4} \text{ C}$$

$$32 \text{ a) } \tau = R \cdot C$$

$$\left. \begin{array}{l} R = 100 \Omega \\ C = 2 \cdot 10^{-5} \text{ F} \end{array} \right\} \tau = 2 \text{ ms (millisecond)}$$

$$\text{b) } \left. \begin{array}{l} Q = C \cdot V \\ C = 2 \cdot 10^{-5} \text{ F} \\ V = 9 \text{ V} \end{array} \right\} Q = 1.8 \cdot 10^{-4} \text{ C}$$

$$\text{c) } \left. \begin{array}{l} Q = Q_0 (1 - e^{-t/RC}) \\ t = RC \text{ (one time constant)} \\ Q_0 = 1.8 \cdot 10^{-4} \text{ C} \end{array} \right\} Q = 1.8 \cdot 10^{-4} (1 - e^{-1}) = 1.14 \cdot 10^{-4} \text{ C}$$

33) first find the time constant: $\tau = R \cdot C = (1 \cdot 10^6 \Omega)(5 \cdot 10^{-6} \text{ F}) = 5 \text{ sec}$

then find the charge (maximum) on the capacitor:

$$Q = C \cdot V = (5 \cdot 10^{-6} \text{ F})(30 \text{ V}) = 1.50 \cdot 10^{-4} \text{ C} \quad \text{Hence}$$

$$\left. \begin{array}{l} Q = Q_0 (1 - e^{-t/RC}) \\ RC = 5 \text{ sec} \\ t = 10 \text{ sec} \\ Q_0 = 1.50 \cdot 10^{-4} \text{ C} \end{array} \right\} Q = 1.5 \cdot 10^{-4} (1 - e^{-2}) = 1.30 \cdot 10^{-4} \text{ C}$$


35) $Q = Q_0(1 - e^{-t/RC})$ dividing both sides by Q_0 will give
 $Q/Q_0 = (1 - e^{-t/RC})$ now $Q/Q_0 =$ the fraction charged i.e.
 in this problem $Q/Q_0 = 0.6$ at $t = 0.9$ sec Hence:

$$0.6 = (1 - e^{-0.900/\tau})$$

$$e^{-0.900/\tau} = 0.4 \Rightarrow -0.900/\tau = \ln(0.4) \Rightarrow \tau = -0.900/\ln(0.4)$$

$$\tau = 0.982 \text{ sec}$$

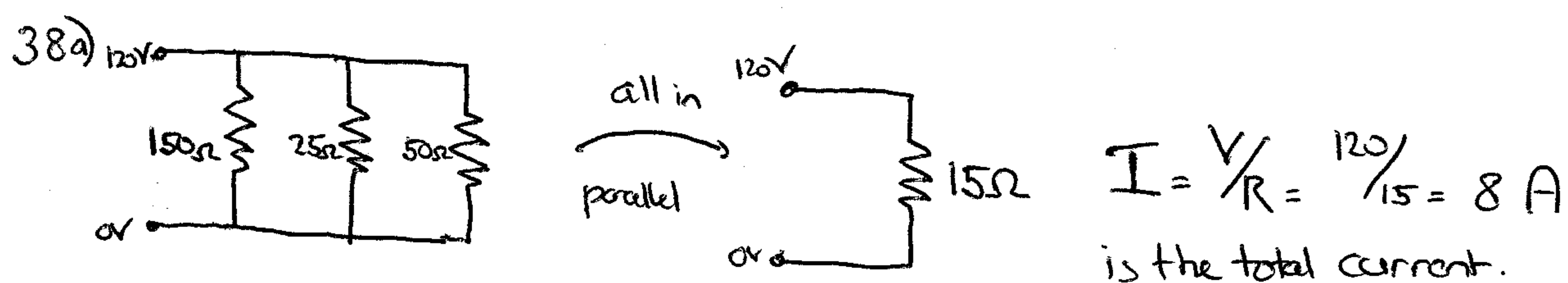44) from above: $Q/Q_0 = (1 - e^{-t/\tau})$ if $t = 2\tau$ (two time constants)
 then $Q/Q_0 = (1 - e^{-2\tau/\tau}) = (1 - e^{-2}) = 0.865 \Rightarrow 86.5\%$ is
 present on the capacitor after two time constants.



b) All have voltages of 120V

c) $R = 150\Omega$
 $V = 120V$ } $I = V/R = 0.800 \text{ A}$ is the current in the lamp

d) $P = V^2/R = (120V)^2/25\Omega = 576 \text{ W}$ is the power dissipated

39a) $P = V^2/R$ need to find the resistance

$$\left. \begin{array}{l} R = V^2/P \\ V = 240V \\ P = 3000W \end{array} \right\} R = 19.2 \Omega$$

b) $V = I \cdot R$

$$\left. \begin{array}{l} I = V/R \\ V = 120V \\ R = 19.2 \Omega \end{array} \right\} I = 6.25A \text{ is the current at } 120V$$

$$\left. \begin{array}{l} b) P = VI \\ V = 120V \\ I = 6.25A \end{array} \right\} P = 750W$$